

CO

Unit-2

Part-2

Combinational Logic

Introduction

- Logic circuits for digital systems may be combinational or sequential.
- Combinational circuits:
 - Consist of **logic gates only**
 - Outputs are determined from the present values of inputs
 - Operations can be specified by a set of Boolean functions
- Sequential circuits:
 - Consist of **logic gates and storage elements**
 - Outputs are a function of the inputs and the state of the storage elements
 - Depend not only on present inputs, but also on past values
 - Circuit behavior must be specified by a time sequence of inputs and internal states

COMBINATIONAL CIRCUITS

- A combinational circuit consists of
 - Input variables
 - Logic gates
 - Output variables

 


Fig. 4-1 Block Diagram of Combinational Circuit

COMBINATIONAL CIRCUITS

- Each input and output variable is a binary signal
 - Represent logic 1 and logic 0
- There are 2^n possible binary input combinations for n input variable
- Only one possible output value for each possible input combination
- Can be specified with a truth table
- Can also be described by m Boolean functions, one for each output variable
 - Each output function is expressed in terms of n input variables

ANALYSIS PROCEDURE

- The analysis of a combinational circuit requires that we determine the function that the circuit implements.
- This task starts with a given logic diagram and culminates with a set of Boolean functions, a truth table, or, possibly, an explanation of the circuit operation.
- The analysis can be performed manually by finding the Boolean functions or truth table or by using a computer simulation program.

ANALYSIS PROCEDURE

- The **first** step in the analysis is to make sure that the given circuit is **combinational and not sequential**.
- **The diagram of a combinational circuit has logic gates with no feedback paths or memory elements.**
- Once the logic diagram is verified to be that of a combinational circuit, one can proceed to **obtain the output Boolean functions or the truth table.**

ANALYSIS PROCEDURE

- To obtain the output Boolean functions from a logic diagram, proceed as follows:
 1. Label all gate outputs that are a function of input variables with arbitrary symbols. Determine the Boolean functions for each gate output.
 2. Label the gates that are a function of input variables and previously labeled gates with other arbitrary symbols. Find the Boolean functions for these gates.


ANALYSIS PROCEDURE

3. Repeat the process outlined in step 2 until the outputs of the circuit are obtained.
4. By repeated substitution of previously defined functions, obtain the output Boolean functions in terms of input variables.

ANALYSIS PROCEDURE

Step 1:

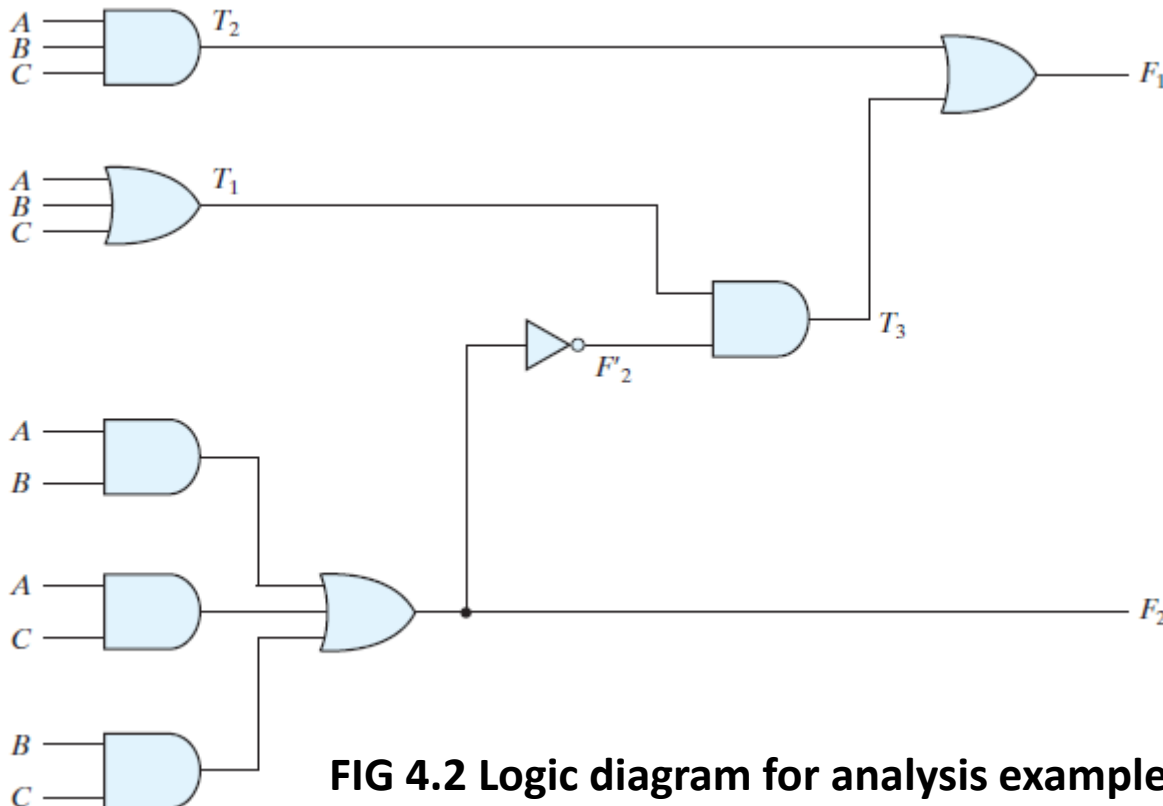- Label all gate outputs that are a function of input variables
- Determine Boolean functions for each gate output




$$\begin{aligned} F_2 &= AB + AC + BC \\ T_1 &= A + B + C \\ T_2 &= ABC \end{aligned}$$

FIG 4.2 Logic diagram for analysis example

ANALYSIS PROCEDURE

Step 2:

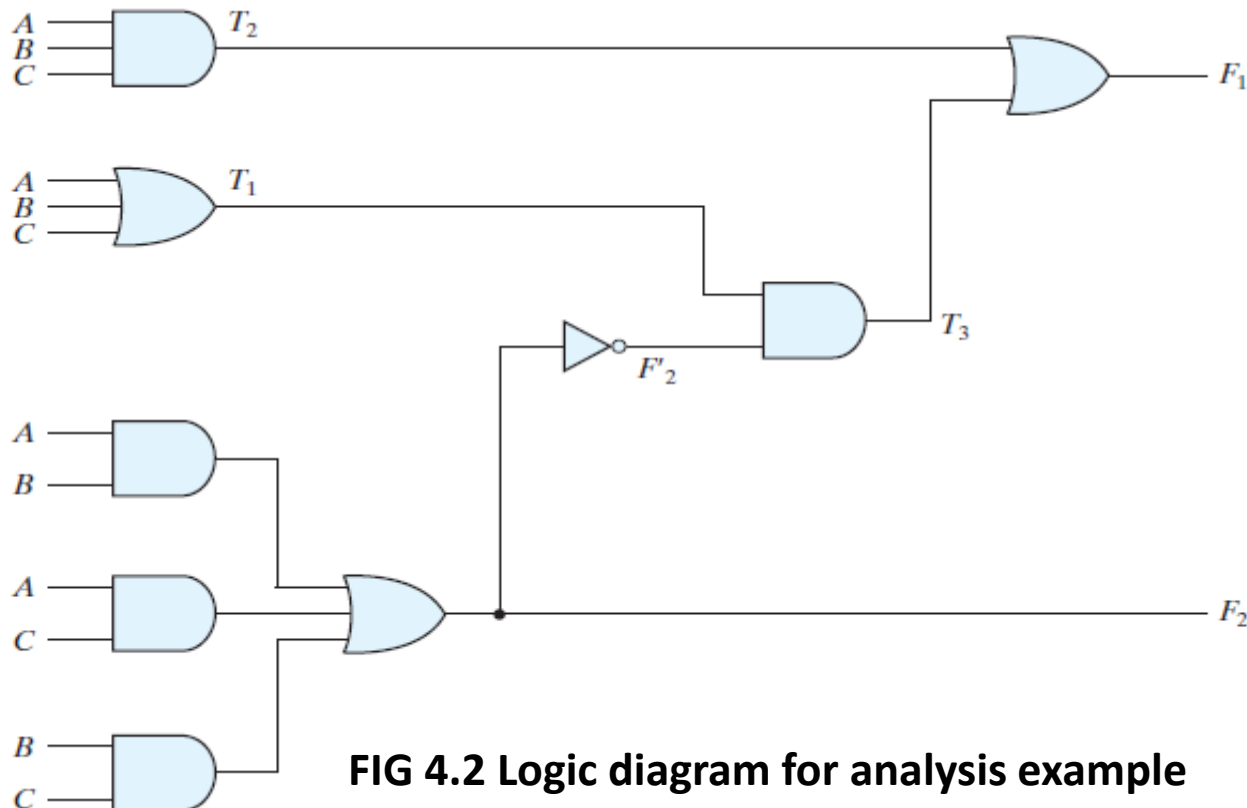- Label the gates that are a function of input variables a previously labeled gates
- Find the Boolean function for these gates



$$\begin{aligned} T_3 &= F_2' T_1 \\ F_1 &= T_3 + T_2 \end{aligned}$$

FIG 4.2 Logic diagram for analysis example

ANALYSIS PROCEDURE

Step 3:

- Obtain the output Boolean function in term of input variables
 - By repeated substitution of previously defined functions

$$\begin{aligned}F_1 &= T_3 + T_2 = F'_2 T_1 + ABC \\&= (AB + AC + BC)' (A + B + C) + ABC \\&= (A' + B')(A' + C')(B' + C')(A + B + C) + ABC \\&= (A' + B' C')(AB' + AC' + BC' + B' C) + ABC \\&= A' BC' + A' B' C + AB' C' + ABC\end{aligned}$$

ANALYSIS PROCEDURE

- To obtain the truth table from the logic diagram:
 1. Determine the number of input variables
 - For n inputs:
 - 2^n possible combinations
 - List the binary numbers from 0 to 2^n-1 in a table
 2. Label the outputs of selected gates
 3. Obtain the truth table for the outputs of those gates that are a function of the input variables only
 4. Obtain the truth table for those gates that are a function of previously defined variables at step 3
 - Repeatedly until all outputs are determined

ANALYSIS PROCEDURE

- We can derive the truth table in Table 4-1 by using the circuit of Fig.4-2.


Table 4.1

Truth Table for the Logic Diagram of Fig. 4.2

A	B	C	F₂	F'₂	T₁	T₂	T₃	F₁
0	0	0	0	1	0	0	0	0
0	0	1	0	1	1	0	1	1
0	1	0	0	1	1	0	1	1
0	1	1	1	0	1	0	0	0
1	0	0	0	1	1	0	1	1
1	0	1	1	0	1	0	0	0
1	1	0	1	0	1	0	0	0
1	1	1	1	0	1	1	0	1

ANALYSIS PROCEDURE

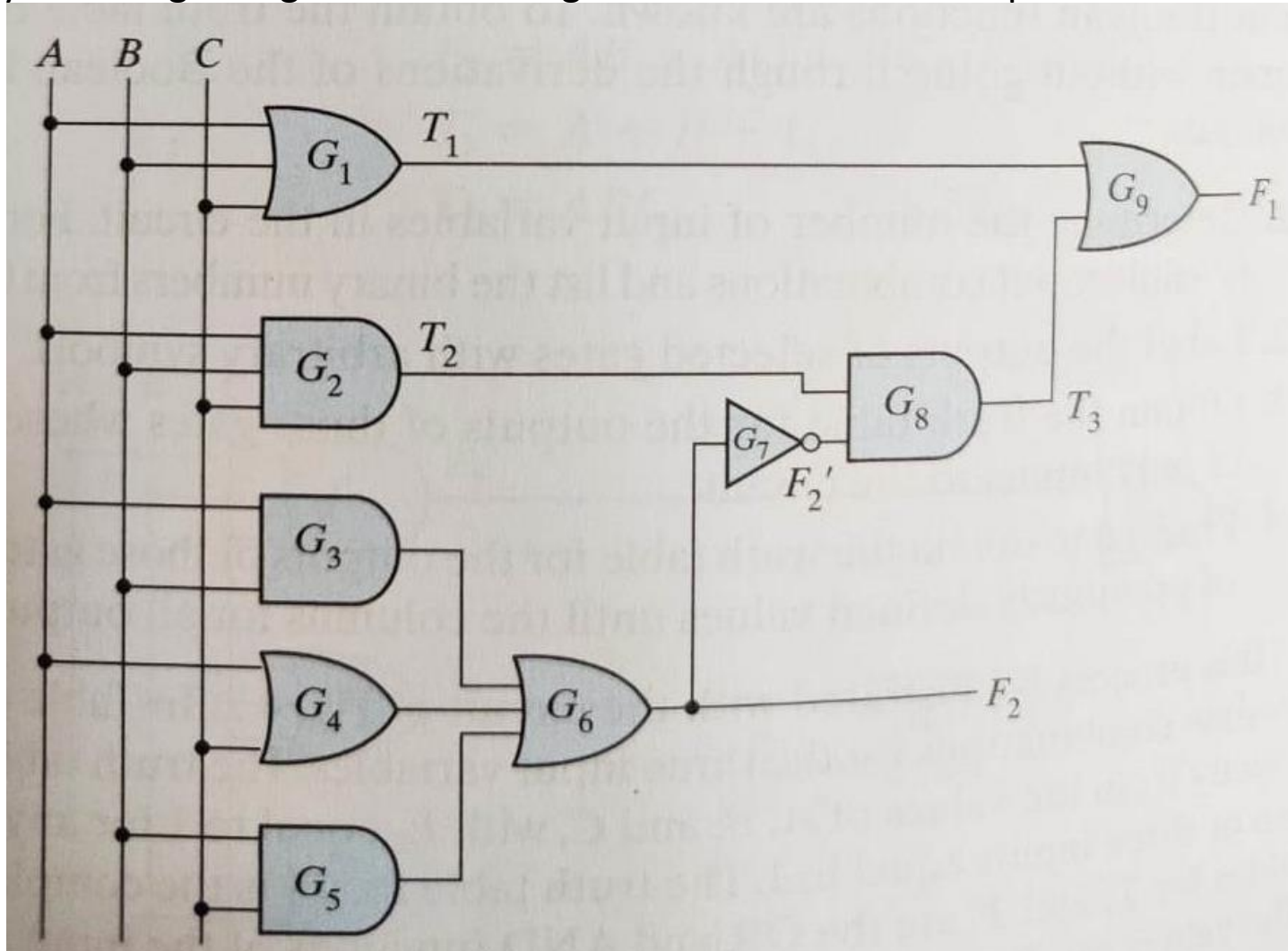Analyze the logic diagram in below fig and find the boolean expressions for F_1 and F_2



DESIGN PROCEDURE

- The design of combinational circuits starts from the specification of the design objective and culminates in a logic circuit diagram or a set of Boolean functions from which the logic diagram can be obtained.

(or)

- Design procedure:
 - Input: the specification of the problem
 - Output: the logic circuit diagram (or Boolean functions)

Design Procedure

- The procedure involves the following steps:
 1. From the specifications of the circuit, determine the required number of inputs and outputs and assign a symbol to each.
 2. Derive the truth table that defines the required relationship between inputs and outputs.
 3. Obtain the simplified Boolean functions for each output as a function of the input variables.
 4. Draw the logic diagram and verify the correctness of the design (manually or by simulation).

Code Conversion Example

- Convert from BCD code to Excess-3 code
- The 6 input combinations not listed are don't cares
- These values have no meaning in BCD
- We can arbitrary assign them to 1 or 0

Input BCD				Output Excess-3 Code			
A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

Table 4.2 Truth Table for Code Conversion Example

Maps for Code Converter (1/3)

- For each symbol of the Excess-3 code, we use 1's to draw the map for simplifying Boolean function.
- The six don't care minterms 10 through 15 are marked with X.

Maps for Code Converter (2/3)


		C			
		CD	00	01	11
A	AB	00	01	11	10
	00	m_0 1	m_1	m_3	m_2 1
	01	m_4 1	m_5	m_7	m_6 1
	11	m_{12} X	m_{13} X	m_{15} X	m_{14} X
10	m_8 1	m_9	m_{11} X	m_{10} X	

D
 $z = D'$


		C			
		CD	00	01	11
A	AB	00	01	11	10
	00	m_0 1	m_1	m_3 1	m_2
	01	m_4 1	m_5	m_7 1	m_6
	11	m_{12} X	m_{13} X	m_{15} X	m_{14} X
10	m_8 1	m_9	m_{11} X	m_{10} X	

D
 $y = CD + C'D'$

Maps for Code Converter (3/3)

 

$$x = B'C + B'D + BC'D'$$

 

$$w = A + BC + BD$$

Logic Diagram for the Converter

- There are various possibilities for a logic diagram that implements a circuit
- A two-level logic diagram may be obtained directly from the Boolean expressions derived by the maps
- The expressions may be manipulated algebraically to use common gates for two or more outputs
 - Reduce the number of gates used

$$z = D'$$

$$y = CD + C' D' = CD + (C + D)'$$

$$\begin{aligned}x &= B'C + B'D + BC' D' = B' (C + D) + BC' D' \\ &= B' (C + D) + B(C + D)'\end{aligned}$$

$$w = A + BC + BD = A + B(C + D)$$

Logic Diagram for the Converter

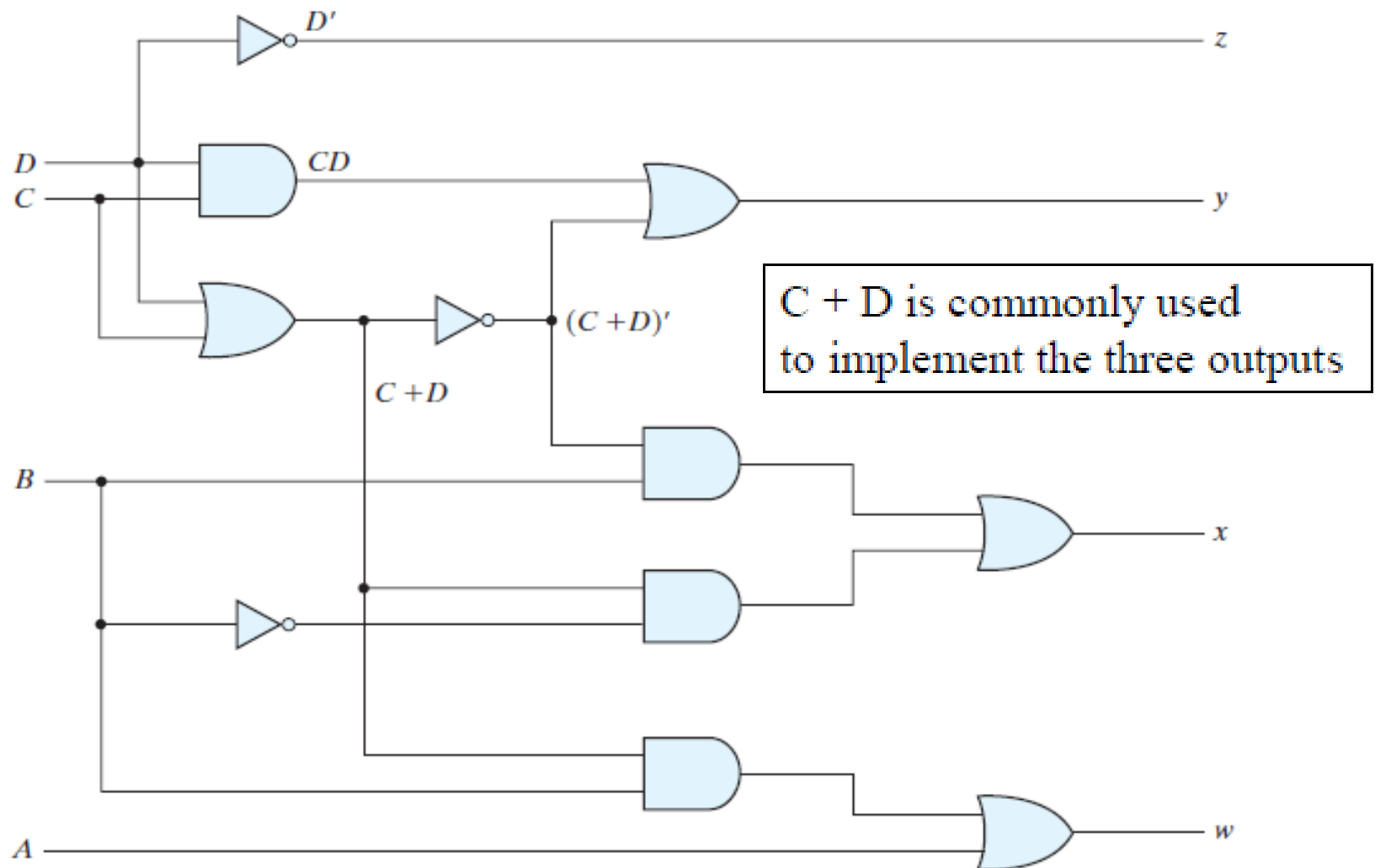


FIGURE 4.4
Logic diagram for BCD-to-excess-3 code converter

Home work

- Convert binary to grey code

Input Binary number				Output gray code			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	1
0	0	1	1	0	0	1	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	1	1
0	1	1	0	0	1	0	1
0	1	1	1	0	1	0	0
1	0	0	0	1	1	0	0
1	0	0	1	1	1	0	1
1	0	1	0	1	1	1	1
1	0	1	1	1	1	1	0
1	1	0	0	1	0	1	0
1	1	0	1	1	0	1	1
1	1	1	0	1	0	0	1
1	1	1	1	1	0	0	0

Binary Adder-Subtractor

- The most basic arithmetic operation is the addition of two binary digits.
- This simple addition consists of four possible elementary operations:
 - $0 + 0 = 0$
 - $0 + 1 = 1$
 - $1 + 0 = 1$
 - $1 + 1 = 10$
- The first three operations produce a sum of one digit, but when both augend and addend bits are equal to 1, the binary sum consists of two digits.
- The higher significant bit of this result is called a **carry**.


Binary Adder-Subtractor

- When the augend and addend numbers contain more significant digits, the carry obtained from the addition of two bits is added to the next higher order pair of significant bits.
- A combinational circuit that performs the addition of two bits is called a **half adder**.
- A adder performs the addition of three bits (two significant bits and a previous carry) is a **full adder**.

Half Adder

- Half adder
 - Inputs: x and y
 - Outputs: S (for sum) and C (for carry)

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 


Block Diagram of half adder


$$S = x'y + xy'$$

$$C = xy$$

Implementation of a Half Adder

 


$$(a) \ S = xy' + x'y$$
$$C = xy$$

 

$$(b) \ S = x \oplus y$$
$$C = xy$$

Full Adder

 - One that performs the addition of three bits (two significant bits and a previous carry) is a full adder.
- $0+0=0$, $0+1=1$, $1+0=1$, $1+1=10$, $10+1=11$, $11+1=100$



Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

x, y: the two significant bits to be added
z: the carry from the previous position

		y			
		yz	00	01	11
x	0	m_0	m_1 1	m_3	m_2 1
	1	m_4 1	m_5	m_7 1	m_6

(a) $S = x'y'z + x'yz' + xy'z' + xyz$

		y			
		yz	00	01	11
x	0	m_0	m_1	m_3 1	m_2
	1	m_4	m_5 1	m_7 1	m_6 1

(b) $C = xy + xz + yz$

Implementation of a Full Adder

 


FIGURE 4.7

Implementation of full adder in sum-of-products form

Another implementation

- Full-adder can also be implemented with two half adders and one OR gate (Carry Look-Ahead adder).

$$\begin{aligned}
 S &= z \oplus (x \oplus y) \\
 &= z'(xy' + x'y) + z(xy' + x'y)' \\
 &= xy'z' + x'yz' + xyz + x'y'z \\
 C &= z(xy' + x'y) + xy = xy'z + x'yz + xy = xy'z + x'yz + xyz + xyz'
 \end{aligned}$$

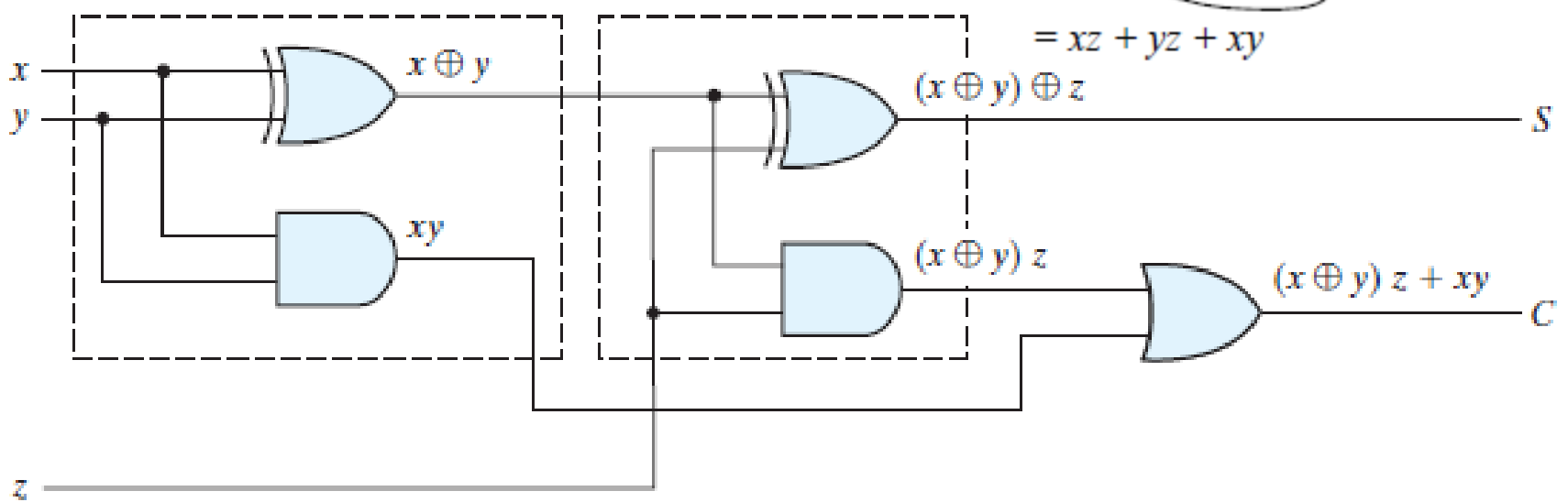


FIGURE 4.8
Implementation of full adder with two half adders and an OR gate

Binary Adder

- A binary adder is a digital circuit that produces the arithmetic sum of two binary numbers.
- It can be constructed with full adders connected in cascade, with the output carry from each full adder connected to the input carry of the next full adder in the chain.
- An n -bit adder requires n full adders, with each output carry connected to the input carry of the next higher order full adder.

Binary Adder

- Below figure shows the interconnection of four full-adder (FA) circuits to provide a **four-bit binary ripple carry adder**.

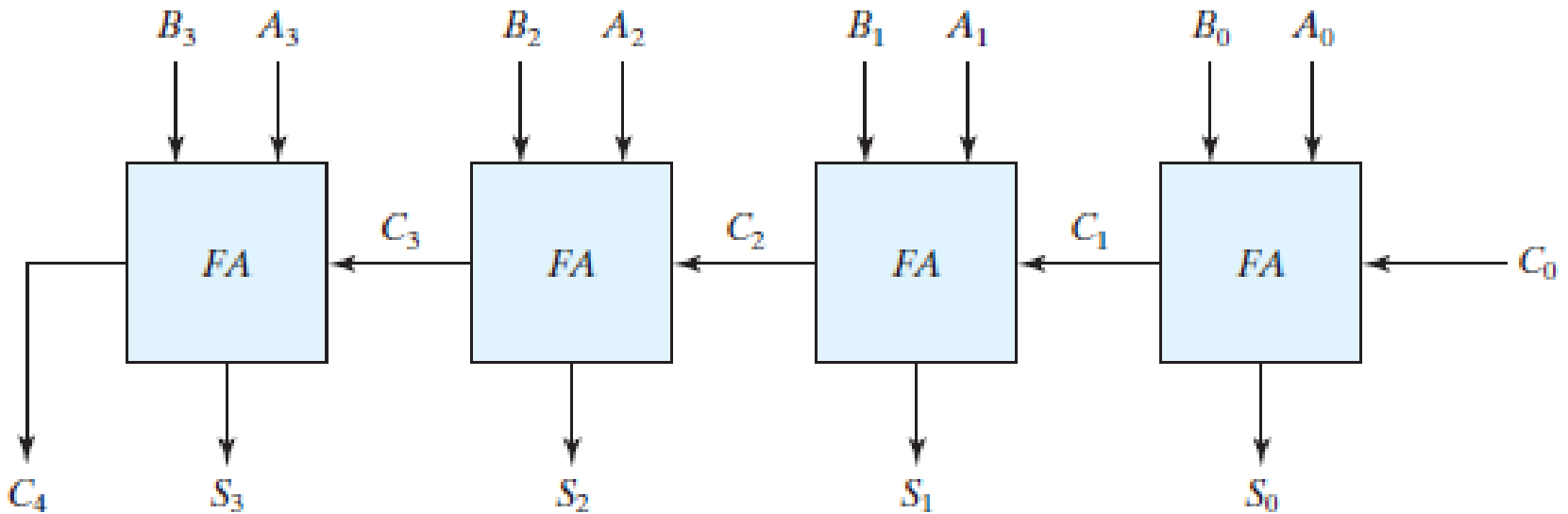


FIGURE 4.9
Four-bit adder

4-bit Adder Example

- Consider two binary number $A = 1011$ and $B = 0011$

Subscript i :	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

4-bit Adder Example

- To demonstrate with a specific example, consider the two binary numbers $A=1011$ and $B=0011$. Their sum $S=1110$ is formed with the four-bit adder as follows:


Subscript i :	3	2	1	0	
Input carry	0	1	1	0	C_i
Augend	1	0	1	1	A_i
Addend	0	0	1	1	B_i
Sum	1	1	1	0	S_i
Output carry	0	0	1	1	C_{i+1}

Carry Propagation

- As in any combinational circuit, the signal must propagate through the gates before the correct output sum is available in the output terminals.
- The total propagation time is equal to the propagation delay of a typical gate, times the number of gate levels in the circuit.
- The longest propagation delay time in an adder is the time it takes the carry to propagate through the full adders.
- Since each bit of the sum output depends on the value of the input carry, the value of S_i at any given stage in the adder will be in its steady-state final value only after the input carry to that stage has been propagated.

Full Adder with P and G

 
- The full adder can be redrawn with two internal signals P (propagation) and G (generation)
- The signal from input carry C_i to output carry C_{i+1} propagates through an AND and a OR gate (2 gate levels)
 - For n-bit adder, there are $2n$ gate levels for the carry to propagate from input to output



Carry Propagation

- The ***carry propagation time*** is a limiting factor on the speed with which two numbers are added
- All other arithmetic operations are implemented by successive additions
 - The time consumed during the addition is very critical
- To reduce the carry propagation delay
 - Employ faster gates with reduced delays
 - Increase the equipment complexity
- Several techniques for reducing the carry propagation time in a parallel adder
 - The most widely used technique employs the principle of ***carry lookahead***

Carry Propagation & Generation

 


carry propagate : $P_i = A_i \oplus B_i$

carry generate : $G_i = A_i B_i$

$S_i = P_i \oplus C_i$

$C_{i+1} = G_i + P_i C_i$

Carry Lookahead Generator

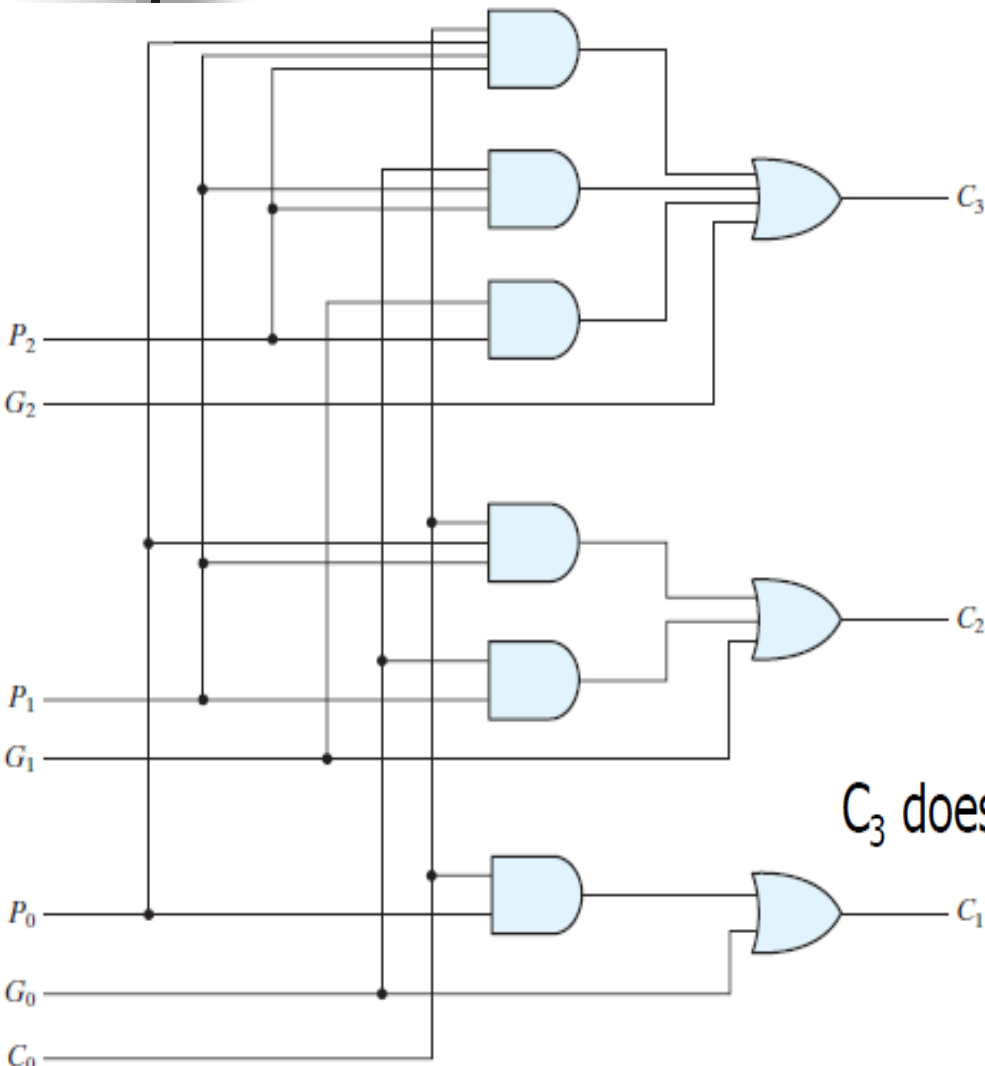

C_0 = input carry

$$C_1 = G_0 + P_0C_0$$

$$C_2 = G_1 + P_1C_1$$

$$= G_1 + P_1(G_0 + P_0C_0)$$

$$= G_1 + P_1G_0 + P_1P_0C_0$$


$$C_3 = G_2 + P_2C_2$$

$$= G_2 + P_2G_1 + P_2P_1G_0 + P_2P_1P_0C_0$$

C_3 does not have to wait for C_2 and C_1 to propagate

C_3 is propagated at the same time as C_2 and C_1 .

Carry Lookahead Adder

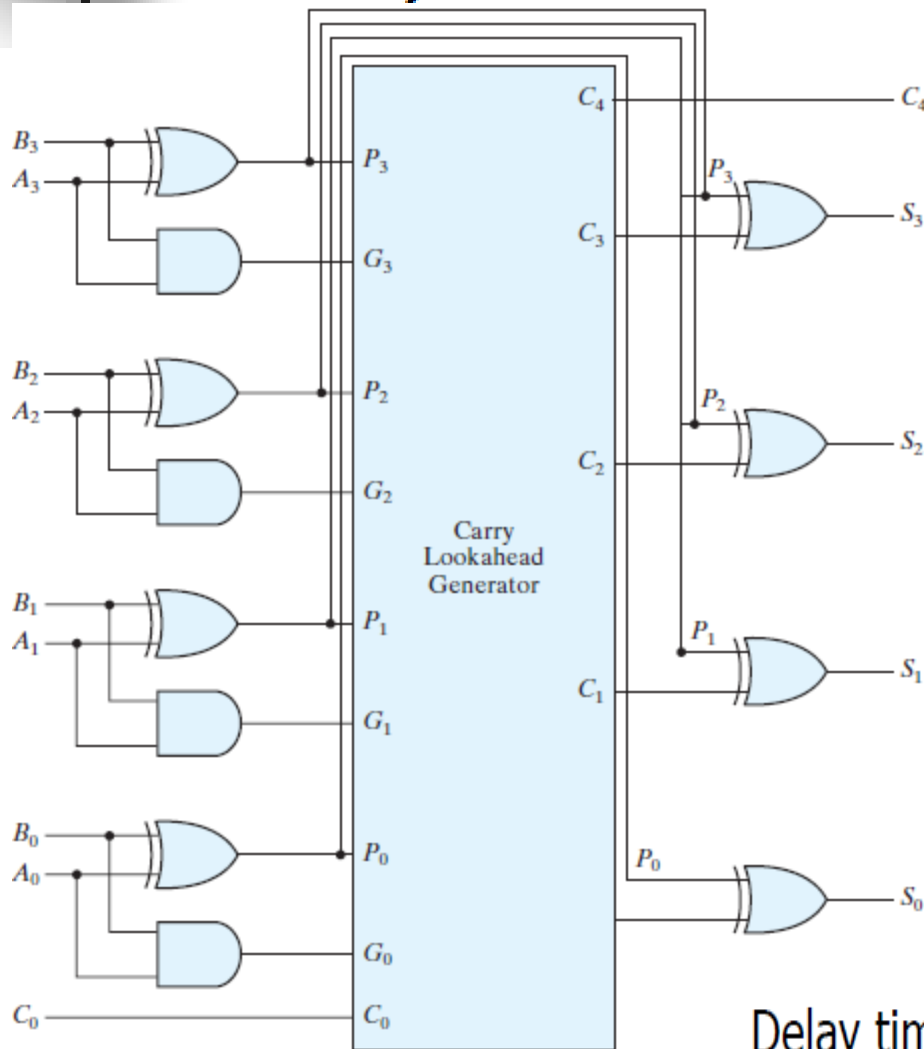

- All output carries are generated after a delay through two levels of gates
- Output S1 to S3 can have equal propagation delay times

Delay time of n-bit CLAA = XOR + (AND + OR) + XOR

Binary Subtractor

- $A - B$ can be done by taking the 2's complement of B and adding it to A ---> $A - B = A + (-B)$
 - 2's complement can be obtained by taking the 1's complement and adding on to the least significant pair of bits
 - $A - B = A + (B' + 1)$
- The circuit for subtraction $A - B$ consists of an adder with inverter placed between each data input B and the corresponding input of the full adder
- The input carry C_0 must be equal to 1

Binary Subtractor


- It is worth noting that binary numbers in the signed-complement system are added and subtracted by the same basic addition and subtraction rules as are unsigned numbers.
- Therefore, computers need only one common hardware circuit to handle both types of arithmetic.
- The user or programmer must interpret the results of such addition or subtraction differently, depending on whether it is assumed that the numbers are signed or unsigned.

4-bit Adder-Subtractor

- $M=0$ (Adder)
 - Input of FA is A and B ($B \oplus 0 = B$), and C_0 is 0
- $M=1$ (Subtractor)
 - Input of FA is A and B' ($B \oplus 1 = B'$), and C_0 is 1

x	y	$x \oplus y$
0	0	0
0	1	1
<hr/>		
1	0	1
1	1	0

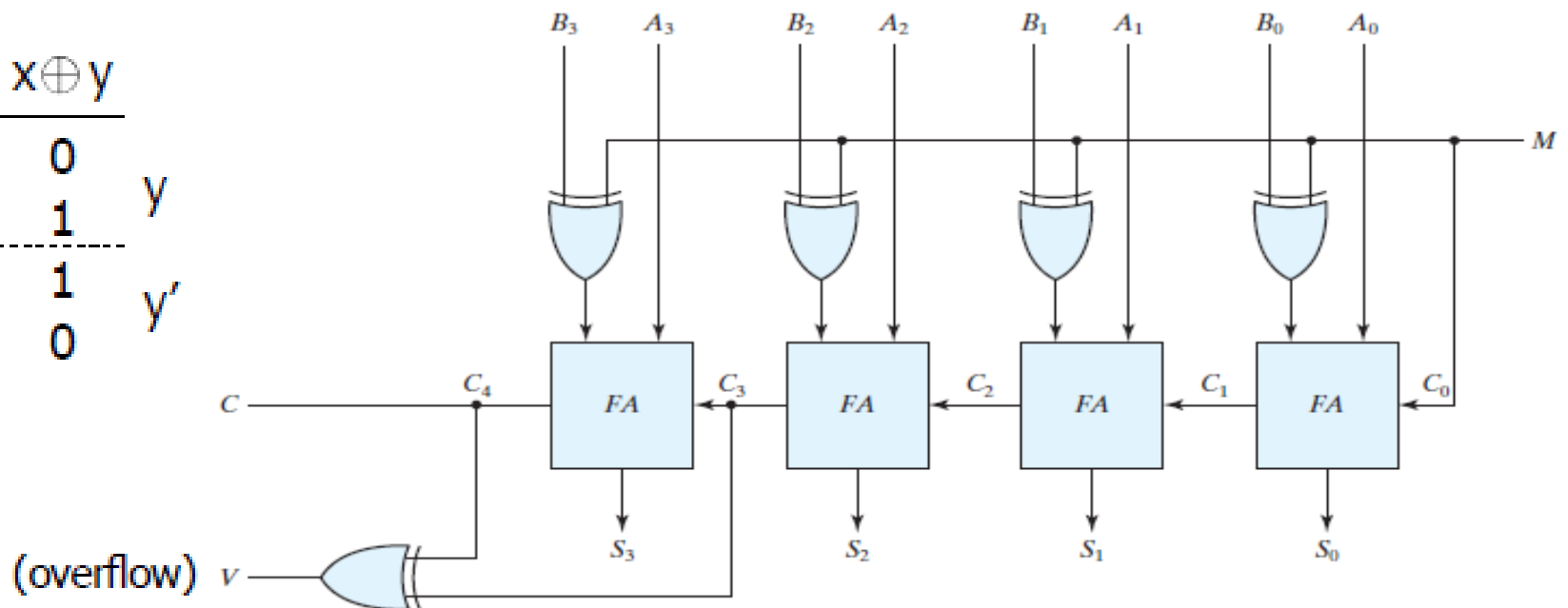y (next to 0 1 and 1 0 rows)
 y' (next to 1 0 and 1 1 rows)



Overflow

- When two numbers with n digits each are added and the sum is a number occupying $n+1$ digits, we say that an overflow occurred.
- Overflow is a problem in digital computers because the number of bits that hold the number is finite and a result that contains $n+1$ bits cannot be accommodated by an n -bit word.
- For this reason, many computers detect the occurrence of an overflow, and when it occurs, a corresponding flip-flop is set that can then be checked by the user.

Overflow

- The detection of an overflow after the addition of two binary numbers depends on whether the numbers are considered to be signed or unsigned.
- When two unsigned numbers are added, an overflow is detected from the end carry out of the most significant position.
- When two signed numbers are added, the sign bit is treated as part of the number and the end carry does not indicate an overflow.
 - Extra overflow detection circuits are required

Overflow

- An overflow cannot occur after an addition if one number is positive and the other is negative
- An overflow may occur if the two numbers added are both positive or both negative.

Overflow Example

The two carry bits are different !!

Carries : 0 1

+70 0 1000110

+80 0 1010000

+150 1 0010110 (-106)
(010010110)

Carries : 1 0

-70 1 0111010


-80 1 0110000

-150 0 1101010 (+106)
(101101010)

Overflow


Overflow Detection

 - An overflow condition can be detected by observing the carry into the sign bit position and the carry out of the sign bit position
 - If these two carries are not equal, and overflow has occurred
 - If the output V is equal to 1, an overflow is detected



Adder-Subtractor Circuit

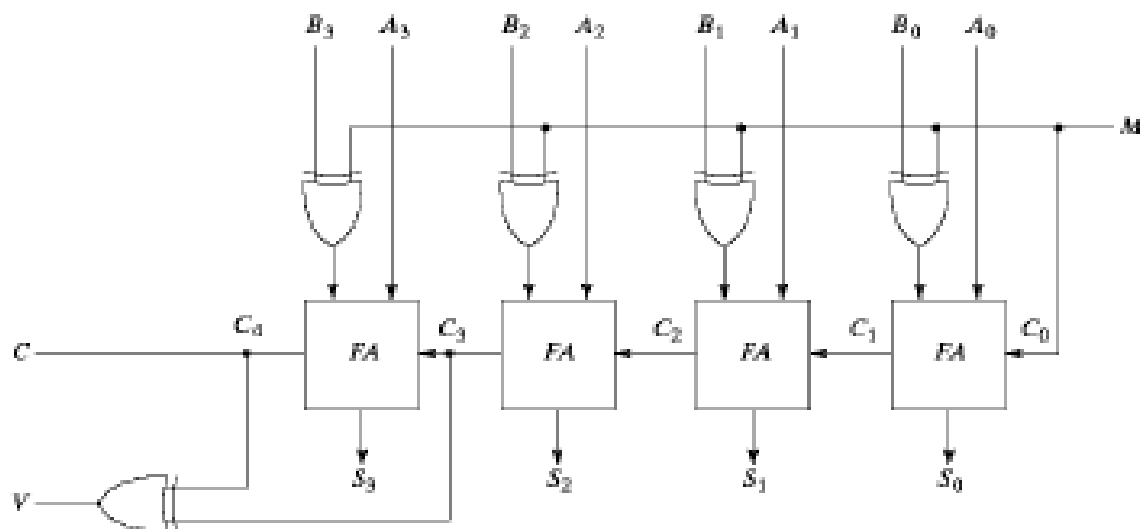- Unsigned
 - C bit detects a *carry* after addition or a *borrow* after subtraction
- Signed
 - V bit detects an overflow
0: no overflow; 1: overflow



Binary Multiplier

- Multiplication of binary numbers is performed in the same way as multiplication of decimal numbers.
- The multiplicand is multiplied by each bit of the multiplier, starting from the least significant bit.
- Each such multiplication forms a partial product. Successive partial products are shifted one position to the left.
- The final product is obtained from the sum of the partial products.


Two-bit by two-bit binary multiplier

$$\begin{array}{r}
 B_1 \quad B_0 \\
 A_1 \quad A_0 \\
 \hline
 A_0 B_1 \quad A_0 B_0
 \end{array}$$

$$\begin{array}{r}
 A_1 B_1 \quad A_1 B_0 \\
 \hline
 C_3 \quad C_2 \quad C_1 \quad C_0
 \end{array}$$

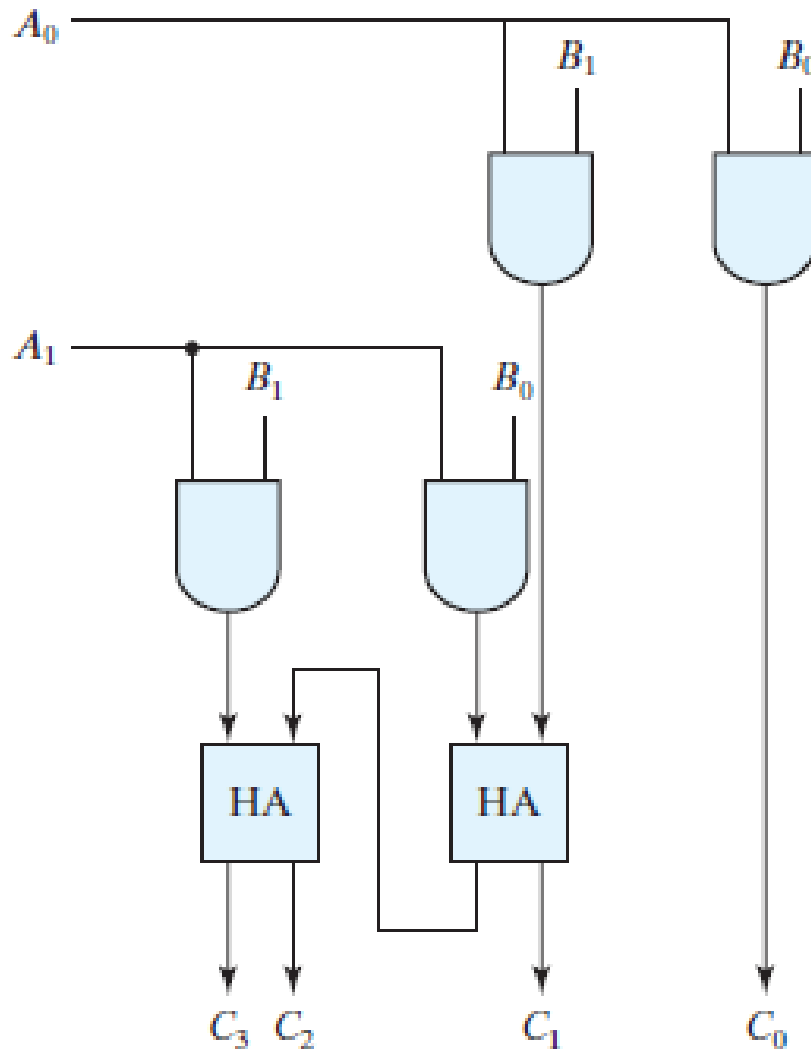Example:-

$$\begin{array}{r}
 10 \\
 11 \quad \times \\
 \hline
 10 \\
 10 \\
 \hline
 110
 \end{array}$$



Binary Multiplier

- Usually, there are more bits in the partial products and it is necessary to use full adders to produce the sum of the partial products.
- **Note:-** The least significant bit of the product does not have to go through an adder, since it is formed by the output of the first AND gate.



J-bit by K-bit binary multiplier

- A combinational circuit binary multiplier with more bits can be constructed in a similar fashion.
- A bit of the multiplier is ANDed with each bit of the multiplicand in as many levels as there are bits in the multiplier.
- The binary output in each level of AND gates is added with the partial product of the previous level to form a new partial product.
- The last level produces the product.
- For J multiplier bits and K multiplicand bits, we need $(J \cdot K)$ AND gates and $(J - 1)$ K-bit adders to produce a product of $(J + K)$ bits.

4-bit by 3-bit binary multiplier

- **Second example** - Consider a multiplier circuit that multiplies a binary number represented by four bits by a number represented by three bits.
- Let the multiplicand be represented by $B_3 B_2 B_1 B_0$ and the multiplier by $A_2 A_1 A_0$.
- Since $K=4$ and $J=3$, we need 12 AND gates and two 4-bit adders to produce a product of seven bits.
- The logic diagram of the multiplier is shown in below figure.

4-bit by 3-bit binary multiplier

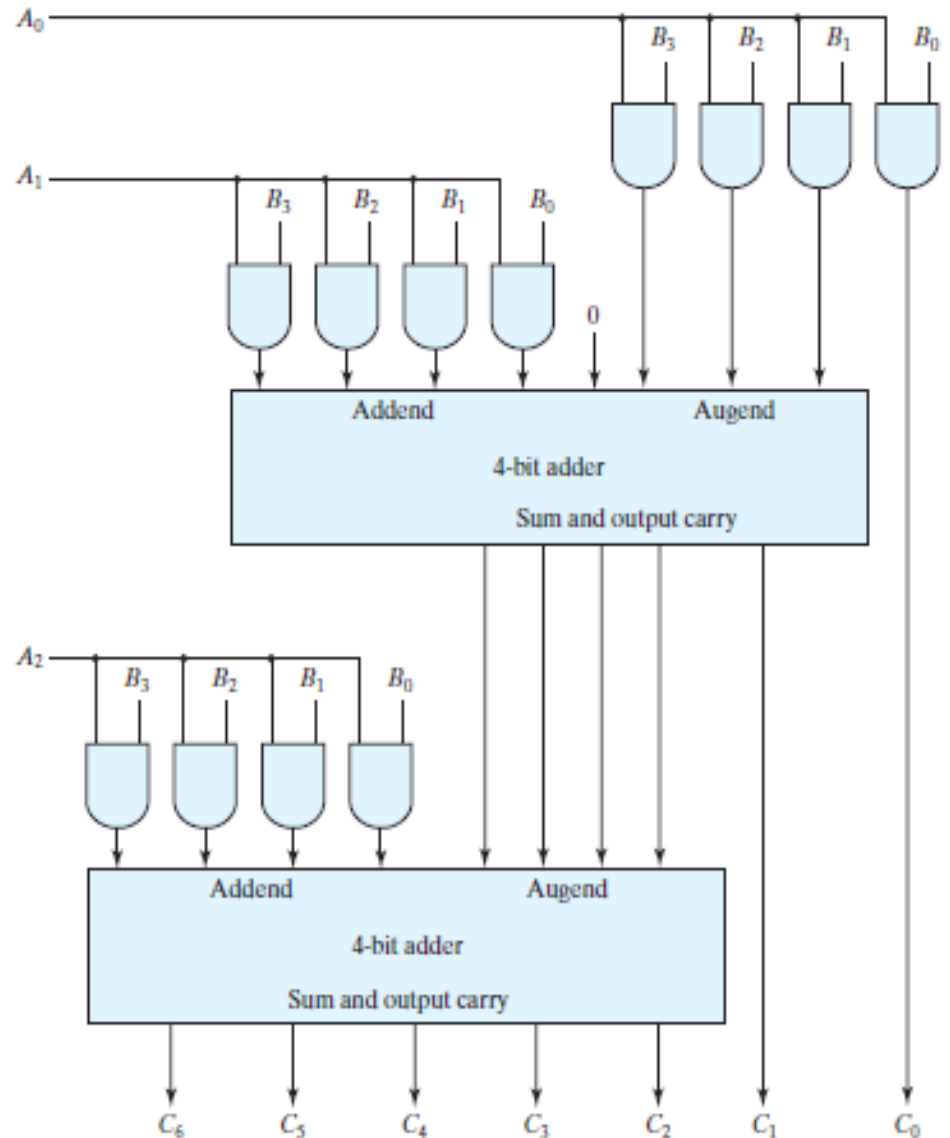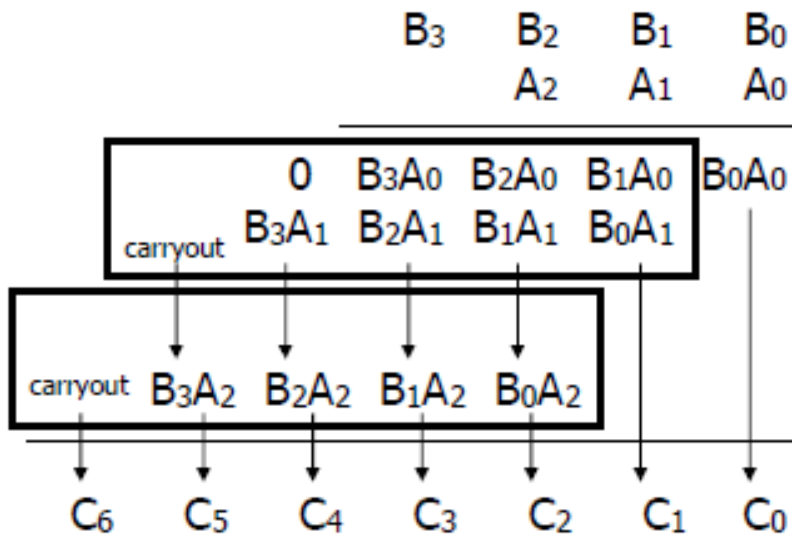


Magnitude Comparator

- The comparison of two numbers is an operation that determines whether one number is greater than, less than, or equal to the other number.
- A magnitude comparator is a combinational circuit that compares two numbers A and B and determines their relative magnitudes.
- The outcome of the comparison is specified by three binary variables that indicate whether $A > B$, $A = B$, or $A < B$.

Magnitude Comparator

- The algorithm is a direct application of the procedure a person uses to compare the relative magnitudes of two numbers.
- Consider two numbers, A and B, with four digits each. Write the coefficients of the numbers in descending order of significance:
- $A=A_3A_2A_1A_0$ $B=B_3B_2B_1B_0$
- Each subscripted letter represents one of the digits in the number. The two numbers are equal if all pairs of significant digits are equal: $A_3=B_3$, $A_2=B_2$, $A_1=B_1$, and $A_0=B_0$. When the numbers are binary, the digits are either 1 or 0, and the equality of each pair of bits can be expressed logically with an exclusive-NOR function as
$$x_i=A_iB_i + A_i'B_i'$$
 for $i = 0, 1, 2, 3$
- where $x_i = 1$ only if the pair of bits in position i are equal (i.e., if both are 1 or both are 0).

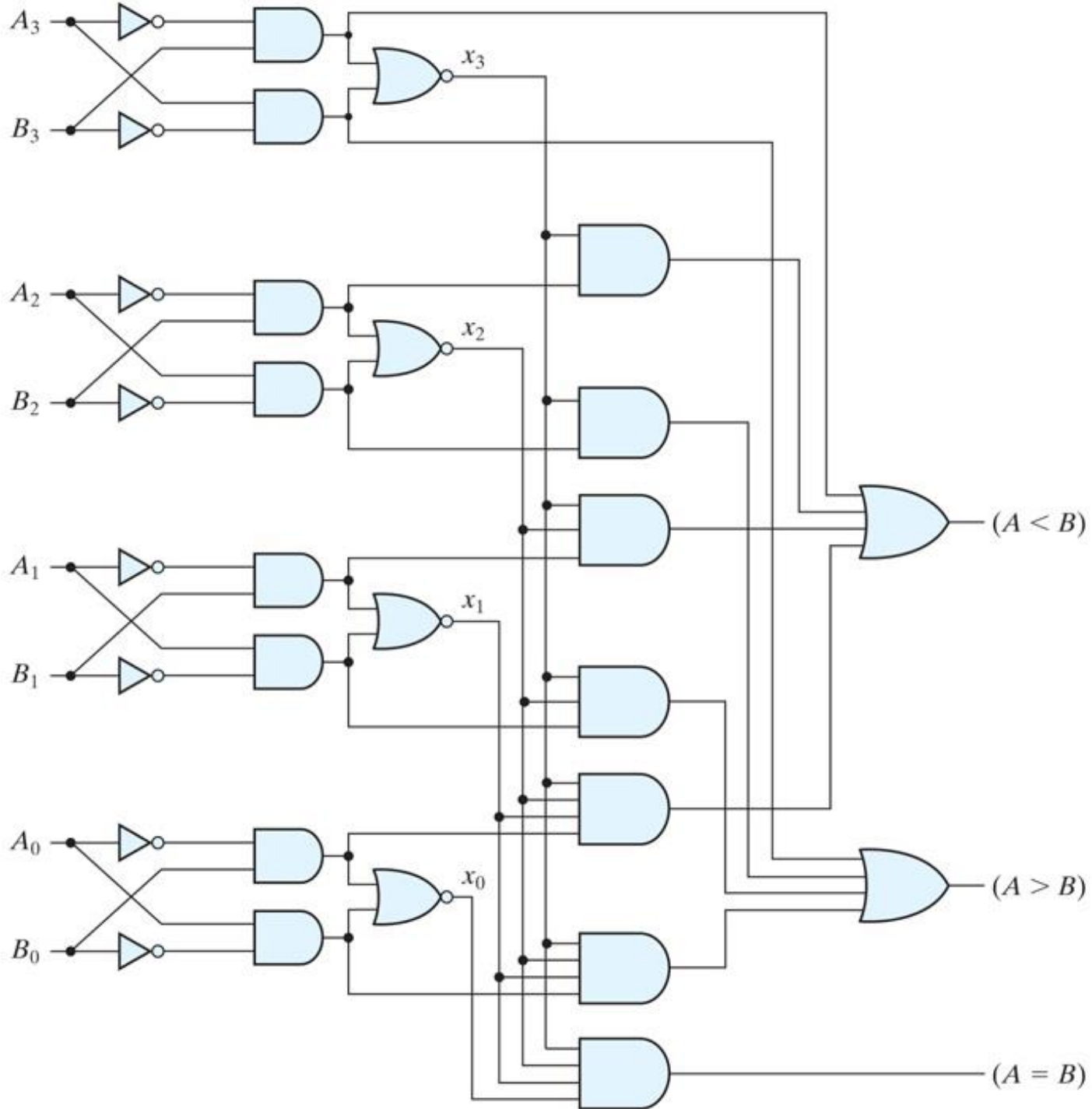

Decoders

- A decoder is a combinational circuit that converts binary information from n input lines to a maximum of 2^n unique output lines.
- If the n -bit coded information has unused combinations, the decoder may have fewer than 2^n outputs.


Decoders

- The decoders presented here are called n-to m-line decoders, where $m \leq 2^n$.
- Their purpose is to generate the 2^n (or fewer) minterms of n input variables.
- Each combination of inputs will assert a unique output.
- The name decoder is also used in conjunction with other code converters, such as a BCD-to-seven-segment decoder.

3-to-8-Line Decoder

- As an example, consider the three-to-eight-line decoder circuit of below Fig.
- The three inputs are decoded into eight outputs, each representing one of the minterms of the three input variables.
- The operation of the decoder may be clarified by the truth table listed in below Table.
- For each possible input combination, there are seven outputs that are equal to 0 and only one that is equal to 1.
- The output whose value is equal to 1 represents the minterm equivalent of the binary number currently available in the input lines.


3-to-8-Line Decoder

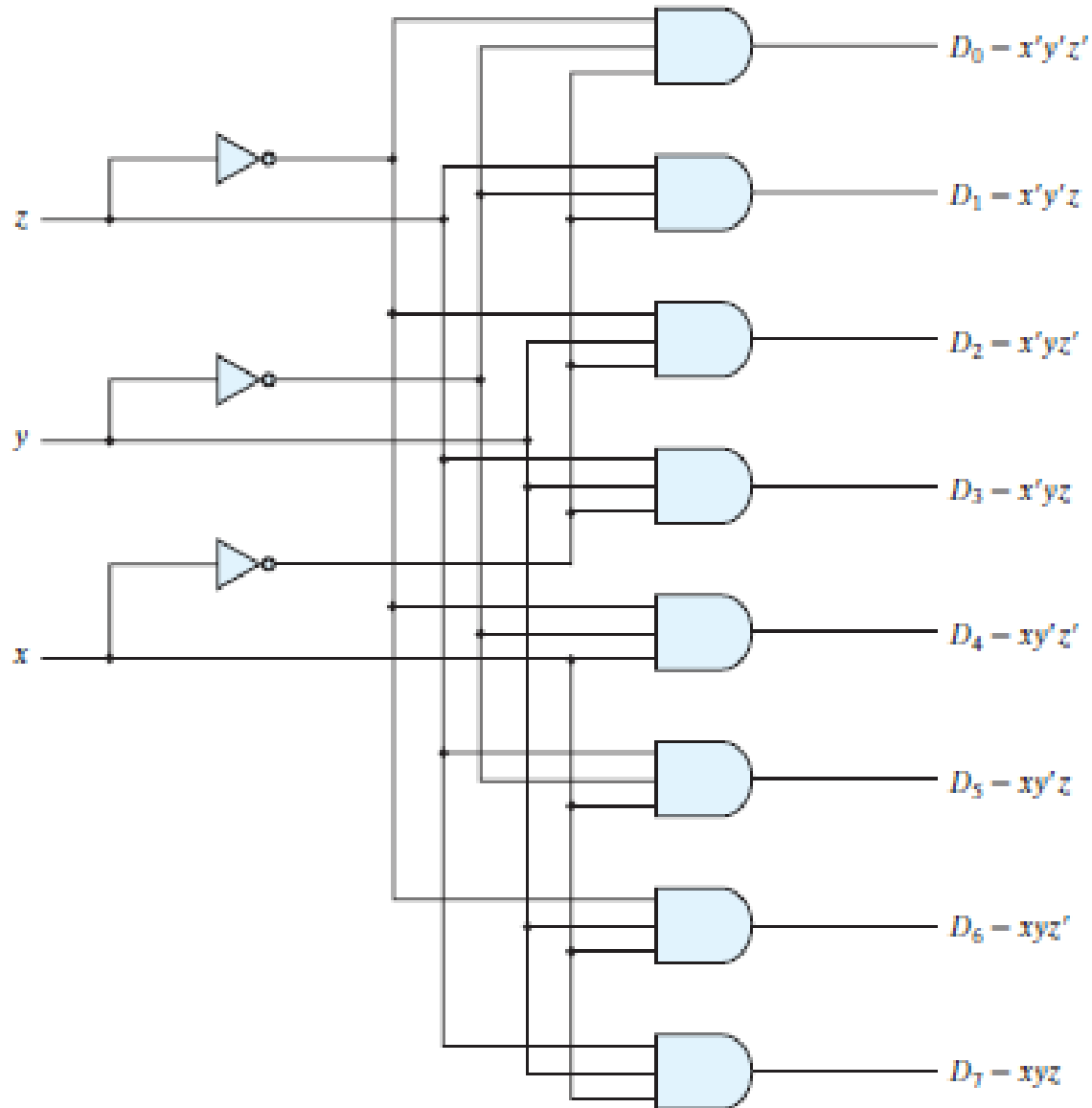

2-to-4-line decoder with enable input

- Some decoders are constructed with NAND gates. Since a NAND gate produces the AND operation with an inverted output, it becomes more economical to generate the decoder minterms in their complemented form.
- An ***enable*** input can be added to control the operation
 - $E=1$: disabled
 - None of the outputs are equal to 0

2-to-4-line decoder with enable input

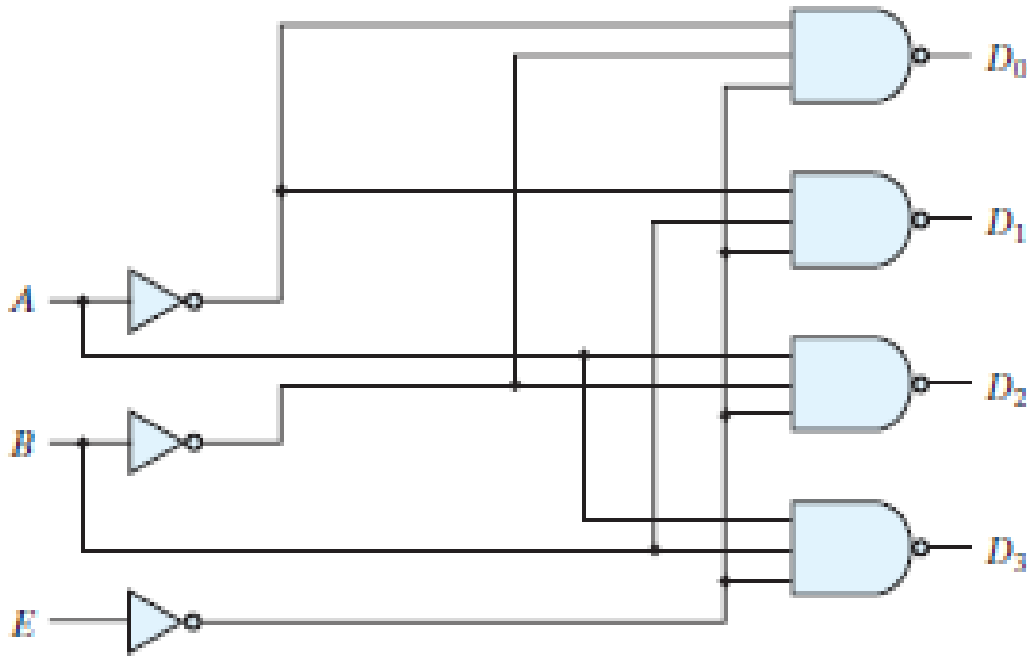

(a) Logic diagram

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> ₀	<i>D</i> ₁	<i>D</i> ₂	<i>D</i> ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

(b) Truth table


As indicated by the truth table , only one output can be equal to 0 at any given time, all other outputs are equal to 1

Demultiplexer

- A decoder with enable input can function as a demultiplexer — a circuit that receives information from a single line and directs it to one of 2^n possible output lines.
- The selection of a specific output is controlled by the bit combination of n selection lines.
- A decoder with an enable input is referred to as a decoder/demultiplexer.
- Below Figure shows two 3-to-8-line decoders with enable inputs connected to form a 4-to-16-line decoder.

Construct Larger Decoders

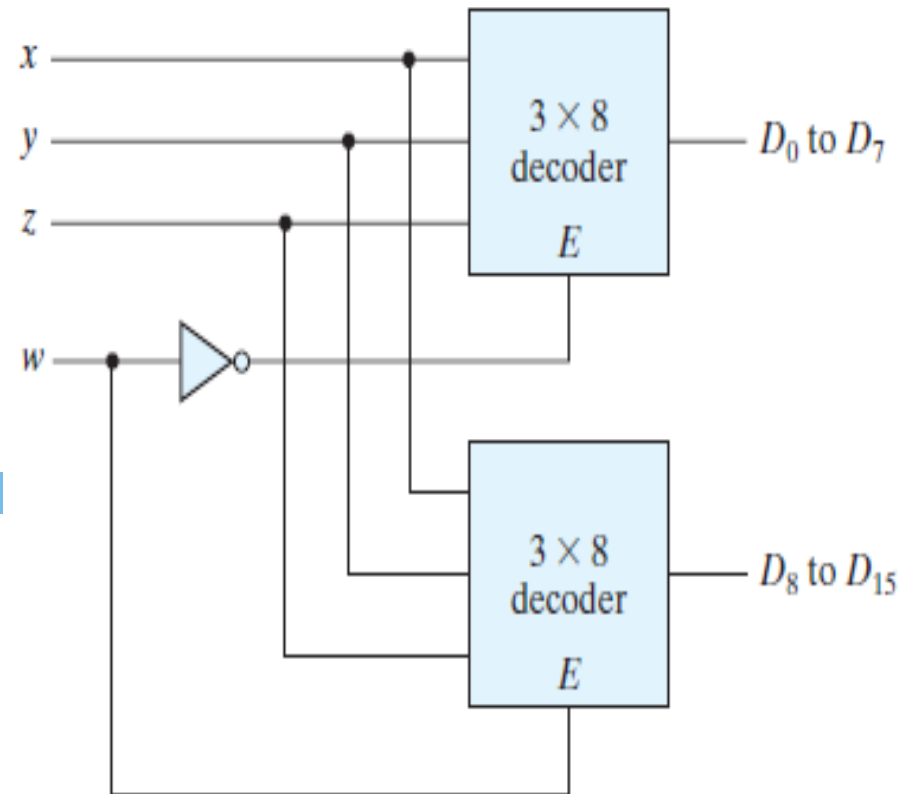- Decoders with enable inputs can be connected together to form a larger decoder
- The enable input is used as the most significant bit of the selection signal
 - $w=0$: the top decoder is enabled
 - $w=1$: the bottom one is enabled
- In general, enable inputs are a convenient feature for standard components to expand their numbers of inputs and outputs




4 × 16 decoder constructed with two 3 × 8 decoders

Combinational Logic Implementation

- A decoder provides the 2^n minterms of n input variables
 - Can be used to form any combinational circuits with extra OR gates (sum of minterms)
 - A function having a list of k minterms can be expressed in its complemented form F' with $2^n - k$ minterms
 - If $k > 2^n/2$, F' will have fewer minterms (fewer OR gates)
 - NOR gates are used instead for implementing F'
-

Combinational Logic Implementation

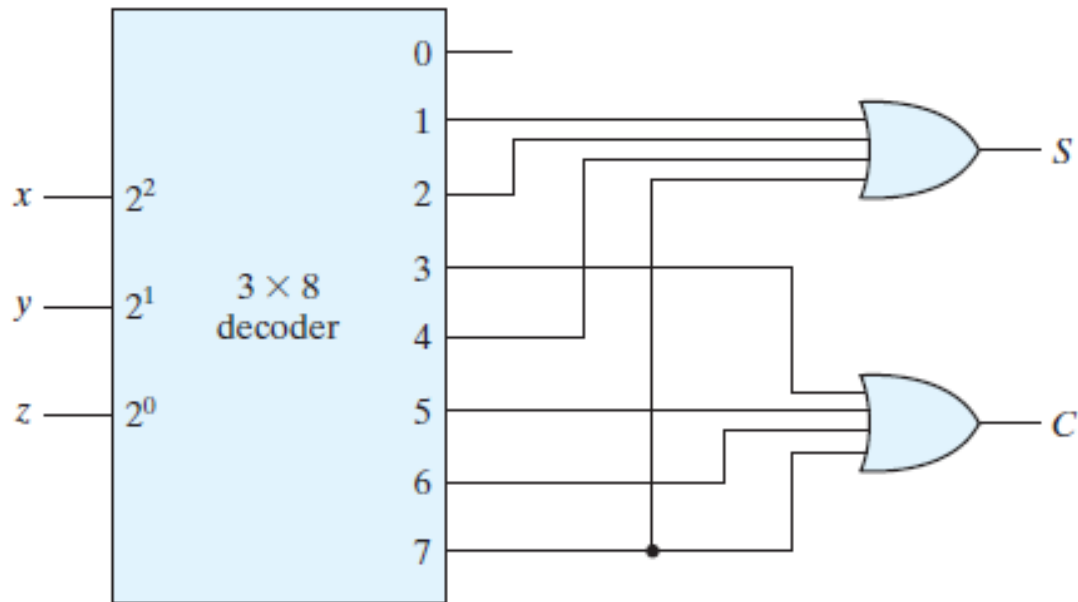

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Implementation of a full adder with a decoder

$$S(x,y,z) = \Sigma (1,2,4,7)$$

$$C(x,y,z) = \Sigma (3,5,6,7)$$

Encoder

- A circuit that performs the inverse operation of a decoder
 - Have 2^n (or fewer) input lines and n output lines
 - The output lines generate the binary code of the input positions
- Only one input can be active at any given time
- An extra output may be required to distinguish the cases that $D_0 = 1$ and all inputs are 0

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

$$\begin{aligned}z &= D_1 + D_3 + D_5 + D_7 \\y &= D_2 + D_3 + D_6 + D_7 \\x &= D_4 + D_5 + D_6 + D_7\end{aligned}$$

Truth Table of an Octal-to-Binary Encoder



Priority Encoder

- A priority encoder is an encoder circuit that includes the priority function.
- The operation of the priority encoder is such that if two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence.
 - In the following truth table:
 - $D_3 > D_2 > D_1 > D_0$
 - The X's in output columns represent don't-care conditions
 - The X's in input columns are useful for representing a truth table in condensed form

Inputs				Outputs		
D_0	D_1	D_2	D_3	x	y	V
0	0	0	0	X	X	0
1	0	0	0	0	0	1
X	1	0	0	0	1	1
X	X	1	0	1	0	1
X	X	X	1	1	1	1

V = 0 :
no valid inputs

Priority Encoder

  


Priority Encoder

$$x = D_2 + D_3$$

$$y = D_3 + D_1 D_2'$$

$$V = D_0 + D_1 + D_2 + D_3$$

 

Four-input priority encoder


MULTIPLEXERS

- A multiplexer is a combinational circuit that selects binary information from one of many input lines and directs it to a single output line.
- The selection of a particular input line is controlled by a set of selection lines.
- Normally, there are 2^n input lines and n selection lines whose bit combinations determine which input is selected.


Two-to-one-line multiplexer

- A two-to-one-line multiplexer connects one of two 1-bit sources to a common destination, as shown in below Fig(a).
- The circuit has two data input lines, one output line, and one selection line S.
- When $S=0$, the upper AND gate is enabled and I_0 has a path to the output.
- When $S=1$, the lower AND gate is enabled and I_1 has a path to the output.
- The multiplexer acts like an **electronic switch** that selects one of two sources.
- The block diagram of a multiplexer is sometimes depicted by a **wedge-shaped symbol**, as shown in Fig (b).
- **It suggests visually how a selected one of multiple data sources is directed into a single destination.**
- The multiplexer is often labeled **“MUX”** in block diagrams.

Two-to-one-line multiplexer

 

(a) Logic diagram

 

(b) Block diagram


FIGURE 4.24
Two-to-one-line multiplexer

Four-to-one-line multiplexer

- A four-to-one-line multiplexer is shown in below Fig.
- Each of the four inputs, I_0 through I_3 , is applied to one input of an AND gate.
- Selection lines S_1 and S_0 are decoded to select a particular AND gate.
- The outputs of the AND gates are applied to a single OR gate that provides the one-line output.
- The function table lists the input that is passed to the output for each combination of the binary selection values.
- A multiplexer is also called a **data selector** , since it selects one of many inputs and steers the binary information to the output line.

4-to-1-Line Multiplexer

 - The combinations of S_0 and S_1 control each AND gates
- Part of the multiplexer resembles a decoder
- To construct a multiplexer:
 - Start with an n -to- 2^n decoder
 - Add 2^n input lines, one to each AND gate
 - The outputs of the AND gates are applied to a single OR gate




(a) Logic diagram

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

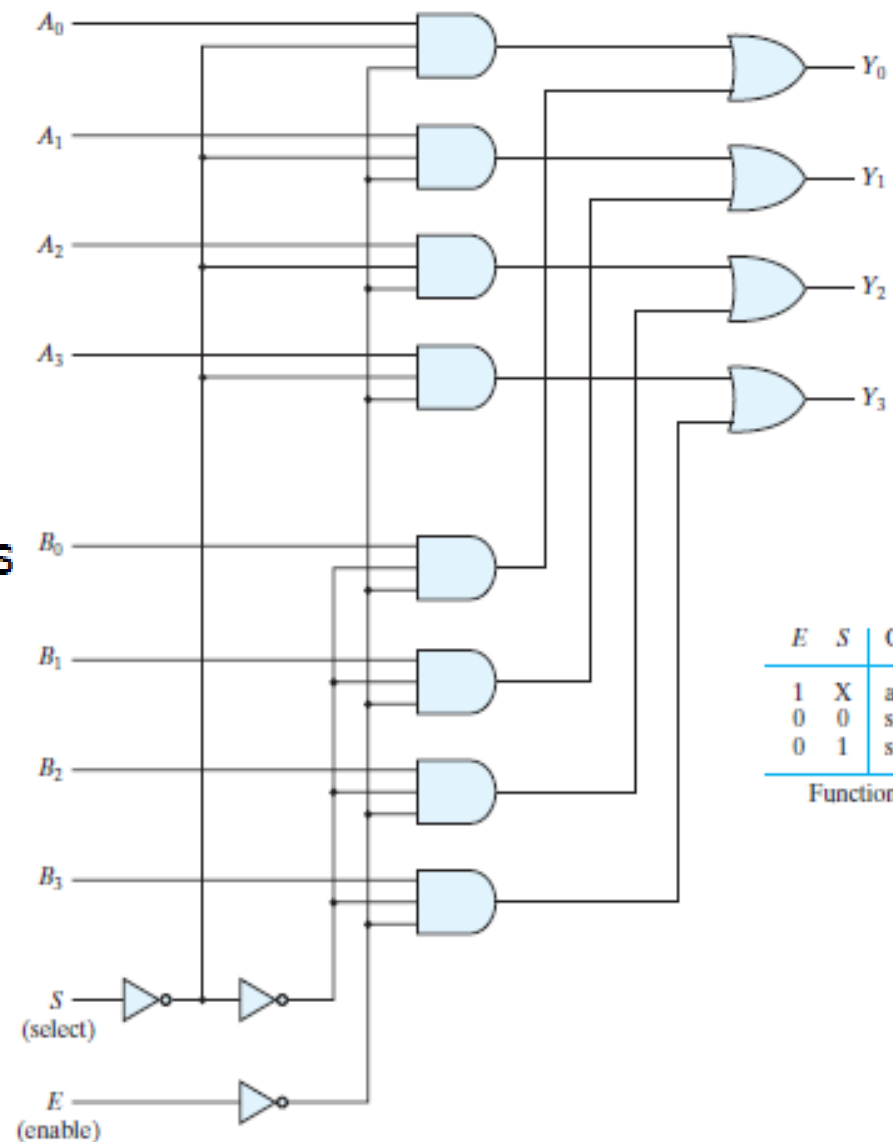(b) Function table

Quadruple 2-to-1-Line Multiplexer

- Multiplexers can be combined with **common selection inputs** to provide multiple-bit selection logic
- Quadruple 2-to-1-line multiplexer:
 - Four 2-to-1-line multiplexers
 - Each capable of selecting one bit of the 2 4-bit inputs
 - E: enable input
E=1: disable the circuit
(all outputs are 0)



E	S	Output Y
1	X	all 0's
0	0	select A
0	1	select B

Function table


Boolean Function Implementation

- A multiplexer is essentially a decoder with an external OR gate
 - Can be used to implement Boolean functions without extra logic
- To implement a Boolean function of n variables:
 - Use a multiplexer with $n - 1$ selection inputs
 - The first $n - 1$ variables are connected to the selection inputs
 - The remaining variable is used for the data inputs

$$F(x,y,z) = \Sigma(1,2,6,7)$$

x	y	z	F	
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = z'$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

(a) Truth table

 


(b) Multiplexer implementation

Implementing a 4-Input Function

$$F(A,B,C,D) = \Sigma(1,3,4,11,12,13,14,15)$$

logic 0: connected to ground
logic 1: connected to Vdd (5V)

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>F</i>	
0	0	0	0	0	
0	0	0	1	1	$F = D$
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = D'$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	$F = 0$
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	$F = D$
1	1	0	0	1	$F = 1$
1	1	0	1	1	$F = 1$
1	1	1	0	1	$F = 1$
1	1	1	1	1	$F = 1$

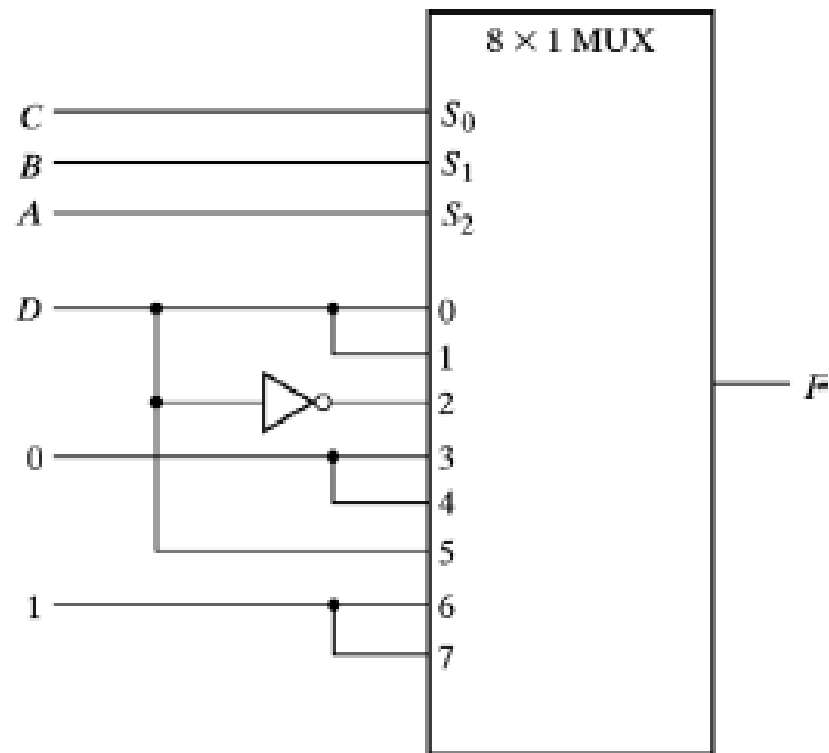

can be 0, 1, the variable, or its complement

Three-State Gate

- A circuit that exhibits three states
 - logic 1, logic 0, and *high-impedance (z)*
- The high-impedance state acts like an open circuit (disconnected)
- The most commonly used three-state gate is the buffer gate
 - $C=0 \rightarrow$ disabled (high-impedance) ; $C=1 \rightarrow$ enabled (pass)
 - Can be used at the output of a function without altering the internal implementation


 



Fig. 4-29 Graphic Symbol for a Three-State Buffer

Implementation with 3-State Gates

 - A large number of three-state gate outputs can be connected with wires to form a common line (bus) without logic conflicts
 - Very convenient for implementing some circuits (ex: multiplexer)
 - Only one buffer can be in the active state at any given time
- One way to ensure that no more than one control input is active at any given time is to use a decoder



(a) 2-to-1- line mux

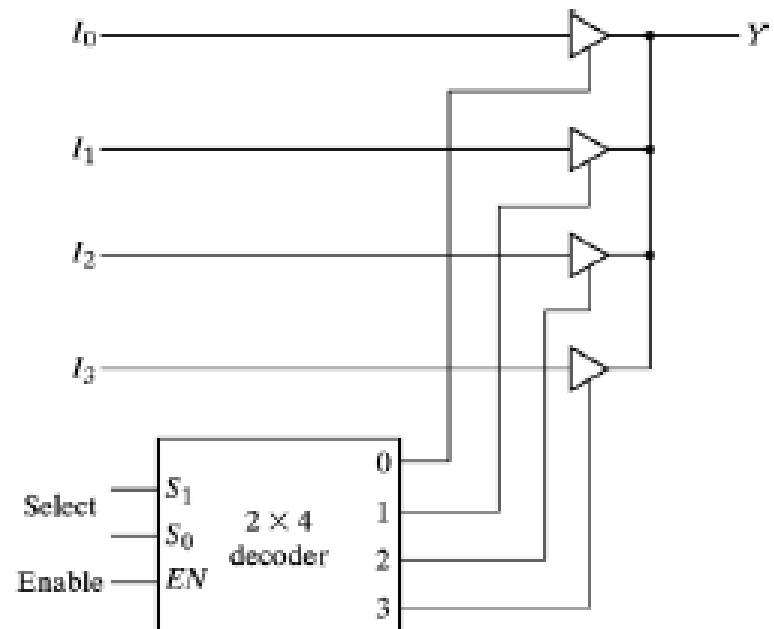

(b) 4 - to - 1 line mux