

REGULATED D.C. POWER SUPPLY Questions and Answers pdf :-

1. In an unregulated power supply, if load current increases, the output voltage

- Remains the same
 - Decreases
 - Increases
 - None of the above
- Ans : 2

2. In an unregulated power supply, if input a.c. voltage increases, the output voltage

- Increases
 - Decreases
 - Remains the same
 - None of the above
- Ans : 1

3. A power supply which has voltage regulation of is unregulated power supply

- 0 %
 - 5 %
 - 10 %
 - 8%
- Ans : 3

4. Commercial power supplies have voltage regulation

- of 10%
 - of 15%
 - of 25%
 - within 1%
- Ans : 4

5. An ideal regulated power supply is one which has voltage regulation of

- 0%
 - 5%
 - 10%
 - 1%
- Ans : 1

6. A Zener diode utilises characteristic for voltage regulation

- Forward
- Reverse
- Both forward and reverse
- None of the above

Ans : 2

7. Zener diode can be used as

- c. voltage regulator only
- c. voltage regulator only
- both d.c. and a.c. voltage regulator
- none of the above

Ans : 3

8. A Zener diode is used as a voltage regulating device

- Shunt
- Series
- Series-shunt
- None of the above

Ans : 1

9. As the junction temperature increases, the voltage breakdown point for Zener mechanism

- Is increased
- Is decreased
- Remains the same
- None of the above

Ans : 2

10. The rupture of co-valent bonds will occur when the electric field is

- 100 V/cm
- 6 V/cm
- 1000 V/cm
- More than 105 V/cm

Ans : 4

11. In a 15 V Zener diode , the breakdown mechanism will occur by

- Avalanche mechanism
- Zener mechanism
- Both Zener and avalanche mechanism

None of the above

Ans : 1

12. A Zener diode that has very narrow depletion layer will breakdown by mechanism

Avalanche

Zener

Both avalanche and Zener

None of the above

Ans : 2

13. As the junction temperature increases, the voltage breakdown point for avalanche mechanism

Remains the same

Decrease

Increases

None of the above

Ans : 3

14. Another name for Zener diode is diode

Breakdown

Voltage

Power

Current

Ans : 1

15. Zener diode are generally made of

Germanium

Silicon

Carbon

None of the above

Ans : 2

16. For increasing the voltage rating, zeners are connected in

Parallel

Series-parallel

Series

None of the above

Ans : 3

17. In a Zener voltage regulator, the changes in load current produce changes in

- Zener current
 - Zener voltage
 - Zener voltage as well as Zener current
 - None of the above
- Ans : 1

18. A Zener voltage regulator is used for load currents

- High
 - Very high
 - Moderate
 - Small
- Ans : 4

19. A Zener voltage regulator will cease to act as a voltage regulator if Zener current becomes

- Less than load current
 - Zero
 - More than load current
 - None of the above
- Ans : 2

20. If the doping level is increased, the breakdown voltage of the Zener

- Remains the same
 - Is increased
 - Is decreased
 - None of the above
- Ans : 3

21. A 30 V Zener will have depletion layer width that of 10 V Zener

- More than
 - Less than
 - Equal to
 - None of the above
- Ans : 1

22. The current in a Zener diode is limited by

- External resistance
- Power dissipation

Both (1) and (2)
None of the above
Ans : 3

23. A 5 mA changes in Zener current produces a 50 mA change in Zener voltage.
What is the Zener impedance?

1
1
100
10
Ans : 4

24. A certain regulator has a no-load voltage of 6 V and a full-load output of 5.82 V. What is the load regulation?

09%
87 %
72 %
None of the above
Ans : 1

25. What is true about the breakdown voltage in a Zener diode?

It decreases when load current increases
It destroys the diode
It equals current times the resistance
It is approximately constant
Ans : 4

26. Which of these is the best description for a Zener diode?

It is a diode
It is a constant current device
It is a constant-voltage device
It works in the forward region
Ans : 3

27. A Zener diode

Is a battery
Acts like a battery in the breakdown region
Has a barrier potential of 1 V
Is forward biased
Ans : 2

28. The load voltage is approximately constant when a Zener diode is

- Forward biased
- Unbiased
- Reverse biased
- Operating in the breakdown region

Ans : 4

29. In a loaded Zener regulator, which is the largest Zener current?

- Series current
- Zener current
- Load current
- None of the above

Ans : 1

30. If the load resistance decreases in a Zener regulator, then Zener current

- Decreases
- Stays the same
- Increases
- None of the above

Ans : 1

31. If the input a.c. voltage to regulated or ordinary power supply increases by 5% what will be the approximate change in d.c. output voltage?

- 10%
- 20%
- 15%
- 5%

Ans : 4

32. If the load current drawn by unregulated power supply increases, the d.c. output voltage

- Increases
- Decreases
- Stays the same
- None of the above

Ans : 2

33. If the load current drawn by unregulated power supply increases, the d.c. output voltage

Increases
Decreases
Stays the same
None of the above

Ans : 2

34. A power supply has a voltage regulation of 1%. If the no-load voltage is 20 V, what is the full-load voltage?

8 V
7 V
6 V
2 V

Ans : 1

35. Two similar 15 V Zeners are connected in series. What is the regulated output voltage?

15 V
5 V
30 V
45 V

Ans : 3

36. A power supply can deliver a maximum rated current of 0.5 A at full-load output voltage of 20 V. What is the minimum load resistance that you can connect across the supply?

10 O
20 O
15 O
40 O

Ans : 4

37. In a regulated power supply, two similar 15 V zeners are connected in series. The input voltage is 45 V d.c. If each Zener has a maximum current rating of 300 mA, what should be the value of the series resistance?

10 O
50 O
25 O
40 O

Ans : 2

38. A Zener regulator in the power supply

Increases the ripple
Decreases the ripple
Neither increases nor decreases the ripple
Data insufficient

Ans : 2

39. When load current is zero, the Zener current will be

Zero
Minimum
Maximum
None of the above

Ans : 3

40. The Zener current will be minimum when

Load current is maximum
Load current is minimum
Load current is zero
None of the above

Ans : 1