

GATE ECE - 2005

Explanations:

1. (A) For the given equation,
auxiliary equation is

$$m^2 - 5m + 6 = 0$$

$$(m-3)(m-2) = 0$$

$$m = 3, 2$$


$$y = e^{2x} + e^{3x}$$

2. (C) Fourier series is defined for a periodic function.

Here $e^{-|t|}$ is not a periodic function.

3. (D)
4. (B)

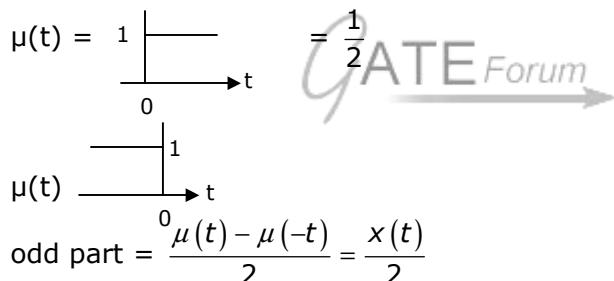5. (A) Even part = $\frac{\mu(t) + \mu(-t)}{2}$



Answer is (A)

6. (C) The given sequence is a 2 sided sequence
so its ROC is a circle
answer is C;

$$\text{ROC for } \left(\frac{5}{6}\right)^n \mu(n) \text{ is } |z| > \frac{5}{6}$$

$$\text{ROC for } \left(\frac{6}{5}\right)^n \mu(-n-1) \text{ is } |z| > \frac{6}{5}$$

$$\frac{5}{6} < |z| < \frac{6}{5}$$

7. (C)

$$u(t) = Ri + \frac{Ldi}{dt} + \frac{1}{C} \int cdt$$

$$\text{By differentiating, } 0 = \frac{Rdi}{dt} + \frac{Ldi^2}{dt^2} + \frac{1}{C} C$$

$$\frac{di^2}{dt^2} + \left(\frac{R}{L}\right) \frac{di}{dt} + \left(\frac{1}{LC}\right) i = 0$$

Roots are,

$$\frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\text{For no oscillations, } \left(\frac{R}{2L}\right)^2 \geq \frac{1}{LC}$$

$$\text{Answer (C). } R \geq 2\sqrt{\frac{L}{C}}$$

8. (B) For an ideal transformer,

$$V_1 = nV_2$$

$$V_2 = nV_1$$

$$I_1 = -\frac{1}{n} I_2$$

$$I_2 = -nI_1$$

$$A = \frac{V_1}{V_2} = n$$

$$B = -\frac{V_1}{I_2} = 0$$

$$C = 0$$

$$D = \frac{-I_1}{I_2} = -\left[\frac{-1}{n}\right] = \frac{1}{n}$$

$$D = \frac{1}{n}$$

9. (B)

10. (C)

11. (C)

12. (B) Reverse saturation current doubles for every 10 degree rise in temperature.

$$I_S = 10 \text{ PA} @ 20^\circ\text{C}$$

$$I_S = 20 \text{ PA} @ 30^\circ\text{C}$$

$$I_S = 40 \text{ PA} @ 40^\circ\text{C}$$

13. (C)

14. (D)

15. (A)

16. ()

17. (B)

18. (B)



19. (A) No Answer ε^1 Data not sufficient

20. (B) For causal system,

$$h(t) = 0, \text{ for } t < 0$$

\therefore Answer is (B).

21. (D)

$$x(n) = \left(\frac{1}{2}\right)^n u(n); x^2(n) = \left(\frac{1}{2}\right)^{2n} u^2(n)$$

$$y(n) = \left(\frac{1}{4}\right)^n u(n); x^2(n) = \left(\frac{1}{4}\right)^n u(n)$$

$$Y(e^{j\omega}) = \frac{1}{1 - \frac{1}{4}e^{-j\omega}} \Rightarrow Y(e^{j\omega}) = \frac{1}{1 - \frac{1}{4}}$$

$$Y(e^{j\omega}) = \frac{4}{3}$$

22. (D)

$$\begin{aligned} 23. (A) S(t) &= 8\cos(20\pi t - \frac{\pi}{2}) + 4\sin(15\pi t) \\ &= 8\sin(20\pi t) + 4\sin(15\pi t) \end{aligned}$$

$$\text{Power in the signal} = \left(\frac{8}{\sqrt{2}}\right)^2 + \left(\frac{4}{\sqrt{2}}\right)^2 = 40$$

24. (C)

25. (B)

26. (D) Lag network is an RC network

$$G(s) = \frac{1}{s + sT}$$

$$\begin{aligned} G(j\omega) &= \frac{1}{1 + j\omega T} = \frac{1}{\sqrt{1 + \omega^2 T^2}} \angle -\tan^{-1} \omega T \\ &= M \angle \phi \end{aligned}$$

when $\omega = 0, M = 1$ and $\phi = 0$


the phasor at $\omega = 0$ has unit length ε^1 lies along the positive real axis.

As ω increases M decreases ε^1 phase angle increases negatively.

$$\text{When } \omega = \frac{1}{T}, M = \frac{1}{\sqrt{2}}, \phi = -45^\circ$$

$$\omega \rightarrow \infty, M \rightarrow 0, \phi = -90^\circ$$

Answer is (D)

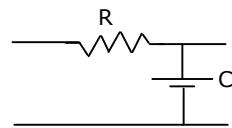

27. ()

28. (C)

29. (B) From wave equation,

$$\omega t = 50000t$$

$$\frac{2\pi}{\lambda} = 0.04$$

$$f = \frac{5 \times 10^4}{2\pi}$$

$$\lambda = \frac{2\pi}{0.004}$$

$$v = f\lambda = -1.25 \times 10^7 \text{ m/sec.}$$

30. (C)

31. (A)

32. (C)

33. (A)

$$A = \begin{bmatrix} 2 & -1 \\ 10 & 0 \\ 0 & 3 \end{bmatrix}; A^{-1} = \frac{1}{6} \begin{bmatrix} 3 & 1 \\ 10 & 2 \end{bmatrix} = \begin{bmatrix} 0.5 & \frac{1}{60} \\ 0 & \frac{1}{3} \end{bmatrix}$$

$$a = \frac{1}{60}, b = \frac{1}{3}$$

$$a + b = \frac{1}{60} + \frac{20}{60} = \frac{21}{60}$$



34. (A)

$$\int_0^{\infty} e^{-\frac{x^2}{8}} dx = \int_0^{\infty} e^{-bx^2} dx$$

$$b = \frac{1}{8}, bx^2 = t, dx = \frac{dt}{2\sqrt{b}}$$

$$= \frac{1}{2\sqrt{b}} \int_0^{\infty} e^{-t} t^{-\frac{1}{2}} dt = \frac{\Gamma\left(\frac{1}{2}\right)}{2\sqrt{b}}$$

$\Gamma\left(\frac{1}{2}\right)$ Gamma function

$$\therefore I = \frac{1}{\sqrt{2\pi}} \times \frac{\sqrt{\pi}\sqrt{8}}{2} = \frac{(2\sqrt{2})\sqrt{\pi}}{(2\sqrt{2}\sqrt{\pi})} = 1$$

$$I = 1$$

35. (C) The symmetric function equation is e^{-t^2} (Simple Gaussian equation)

$$y(t) = \frac{d}{dt} (e^{-t^2}) = -2t [e^{-t^2}]$$

when t is +ve, y(t) is negative

when t is -ve, y(t) is positive.

Answer is (C).

36. (C)

37. (A) By trial ϵ^1 error (A) is correct

38. (A)


By KCL,

$$5\angle 0 = -I_1 + 10\angle 60$$

$$I_1 = 10\angle 60 - 5$$

$$= 10 \left(\frac{1}{2} + \frac{j\sqrt{3}}{2} \right) - 5$$
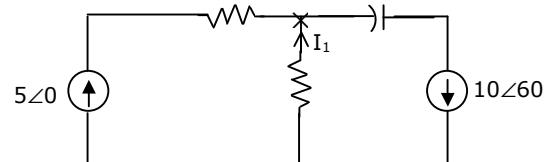
$$I_1 = \frac{10\sqrt{3}}{2} \angle 90^\circ$$



39. (B)


40. () By KVL,

$$10 = -5I_1 + 5(1 - I_1)$$

$$I_1 = -\frac{1}{2}$$

$$V_{ab} = 5(1 - I_1)$$

$$V_{ab} = 7.5$$

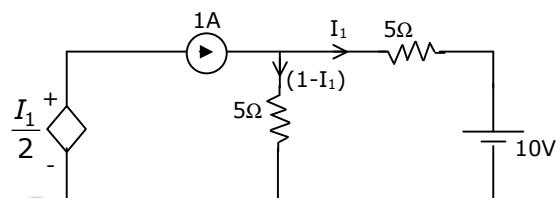

GATE Forum

41. (C)

$$I_1 = \frac{10}{2R} = \frac{5}{R}$$


$$I_2 = \frac{10}{2.1R} = 4.76/R$$

$$V_{ab} = -RI_1 + I_2 R$$

$$= R[I_2 - I_1]$$

$$= \frac{R}{R}[4.76 - 5]$$

$$V_{ab} = -0.238$$

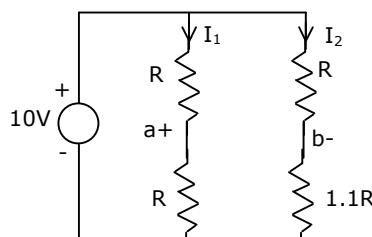


42. (D)

43. (B) Time constant = $RC = 100\mu\text{sec}$.

$$T = 2 \text{ sec} \gg 100\mu\text{sec}$$

So, C is fully charged (opposite polarity)

$$V_{out} = -3$$

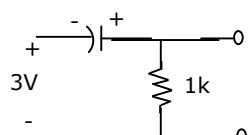

44. (B) Conductivity is proportional to doping concentration

$$NA = 10^{18}, NB = 10^{18}, \frac{\mu A}{\mu B} = \frac{1}{3}$$

$$\sigma = n q \mu \text{ (n concentration)}$$

$$\frac{\sigma A}{\sigma B} = \left(\frac{\mu A}{\mu B} \right) = \frac{1}{3} \quad (3)$$

$$\frac{\sigma A}{\sigma B} = \frac{1}{3}$$

45. (B)

$$C = \frac{\epsilon_0 \epsilon_r}{t} = \frac{11.7 \times 8.85 \times 10^{-12}}{10 \times 10^{-6}}$$

$$C = 10.35 \mu F$$

46. (C) It is high pass,


$$f = \frac{1}{2\pi RC}; R = 1k, C = 1\mu F$$

$$\omega = \frac{1}{1K \times 1\mu F} = 1000 \text{ rad/sec}$$

47. ()


48. (A)

49. (D) Equivalent circuit of BJT is

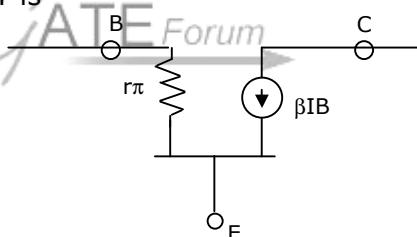

Differential mode gain (A_d):

Small signal model for difference mode

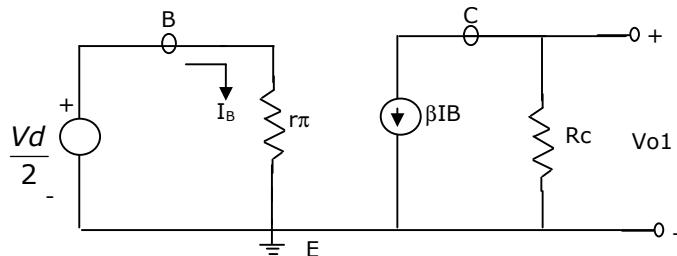

$$A_d = \frac{V_{o1}}{V_d} = \frac{-\beta R_c}{2r_\pi} = -\frac{g_m R_c}{2}$$

$$A_d = \left(\frac{-g_m R_c}{2} \right)$$


Common mode gain (A_c):

$$AC =$$

$$\frac{V_{01}}{V_C} = \frac{-\beta R_C}{2(HB)R_E + r_\pi}$$

$$A_c = \frac{-R_C}{2R_E}$$

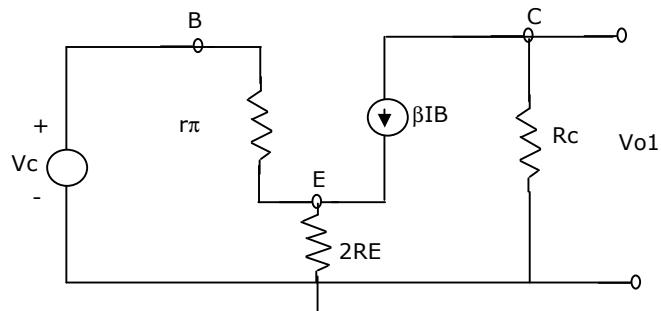for $\beta \gg 1$ $r_\pi \ll 2R_E$
decrease A_c with $R_E \uparrow$



$$CMRR = \frac{Ad}{Ac}$$

$$CMRR = gmRE$$

50. (C) $V_{Ds} = 5 - 1 = 4V$ $V_{t=1}$


$$V_{Gs} = 3 - 1 = 2$$

$$V_{Gs} - V_t = 2 - 1 = 1$$

$$V_{Ds} >, V_{Gs} - \text{if}$$

$$4 >, 1$$

so device in saturation.

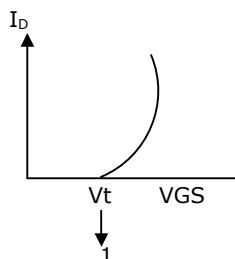

51. (B)

$$\beta = 50, \alpha = \frac{50}{51} = 0.98039$$

$$V_{BE} = 0.7V$$


$$20V(430K)I_B + 0.7 + I_E(1k)$$

$$20 = (430K)I_B + 0.7 + (51I_B)1k$$

$$I_B = 40\mu A$$

$$I_C = \beta I_B = 2000 \mu A$$
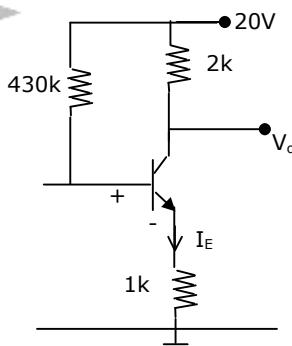
$$V_o = 20 - 2k \times 2000 \mu A = 16V$$



52. (A) For the zener diode to be operated in the breakdown region, the maximum load current is

$$i_{L(\max)} = \frac{V_s(\min) - V_{ZD}}{R_s} - I_2 k$$

$$= \frac{20 - 5.8}{1k} - \left(\frac{1}{2}\right)mA$$

$$i_{L(\max)} = 13.7mA$$

53. (C) V_o is at logic 0. So transistor is in saturation.

$$V_{BE} = 0.75 V$$

$$\therefore I_R = \frac{0.75}{1k} = 0.75mA$$

$$I_R = 0.75mA$$

54. (A)

$$\begin{aligned}
 f &= A'BC + ABC' \\
 &= B[A'C + AC'] = B[(A+C)(A'+C')] \\
 f &= B[A+C][A'+C']
 \end{aligned}$$

55. (C)

$$\begin{aligned}
 I_{DS}(T_1) &= I_{DS}(T_2) \\
 \frac{1}{2}K_1(VGs_1 - V_t)^2 &= \frac{1}{2}K_2(VGs_2 - V_t)^2 \\
 36(5 - V_o - 1)^2 &= 9(V_o - 1)^2 \\
 6(4 - V_o) &= 3(V_o - 1) \Rightarrow 2(4 - V_o) = V_o - 1 \\
 8 + 1 &= 3V_o = 9 \\
 V_o &= 3
 \end{aligned}$$

56. (C)

JK	Q_{n+1}
00	Q(n)
01	0
10	1
11	[Q(n)] ¹

If J = 1,

$$\begin{aligned}
 Q(n+1) &= 1 \text{ (or)} [Q(n)]^1 \\
 &= 1 \text{ (or)} (0)^1
 \end{aligned}$$

Q(n+1) = 1 [given Q(n) = 0]

57. (A) T Flip-flop will toggle if T = 1

$$Q_0 1 \rightarrow 0$$

$$Q_1 1 \rightarrow 0$$

$$Q_2 0 \rightarrow 1$$

Answer is 100

58. (D) Address range of chip 1 ε¹ chip 2 →

A0 - A7	A9A8A7 - A0
∞ - FF	00FF - 00
	01FF - 00
	10FF - 00
	11FF - 00

A8 A9 → selecting chip #1

[Address range is 100 - 1FF]

A8 A9 → selecting chip #2

[200 - 2FF]

Address range is 100 - 2FF

Since A10 – A15 are not used, the address range can be 100 – 2FF (or) 500 – 6FF (or) 900 – AFF,

Answer is (D).

For the address space F800 – F9FF chip #1 ϵ^1 chip #2 are not selected.

59. (A)

$$\begin{aligned} x(t - to) &\leftrightarrow e^{-j\omega to} \times (\omega) \\ Y(\omega) &= 0.5e^{-j\omega(td-T)} \times (\omega) + e^{-j\omega td} \times (\omega) + 0.5e^{-j\omega c(td+T)} \\ &= e^{-j\omega td} \times (\omega) [1 + 0.5(2 \cos(\omega T))] \\ \frac{Y(\omega)}{X(\omega)} &= e^{-j\omega td} [1 + \cos \omega T] = H(\omega) \end{aligned}$$

60. (C)

61. (B) $y(n) = Ax(n - no)$

$$\begin{aligned} Y(e^{j\omega}) &= Ae^{-j\omega no} \times (e^{j\omega}) \\ H(e^{j\omega}) &= \frac{Y(e^{j\omega})}{X(e^{j\omega})} = Ae^{-j\omega no} = |H(e^{j\omega})| e^{j\arg(H(e^{j\omega}))} \\ |H(e^{j\omega})| &= -\omega no \\ |H(e^{j\omega})| &= -\omega_o no + 2\pi k \end{aligned}$$

General solution; k is a arbitrary integer

62. (B) Inverse Fourier transform of

$$\begin{aligned} x(ab + b) &\square \quad \frac{1}{a} e^{-j2\pi\left(\frac{b}{a}\right)t} x\left(\frac{t}{a}\right) \\ a = 3, b = 2 &\square \quad \frac{1}{3} x\left(\frac{t}{3}\right) e^{-j\frac{4\pi t}{3}} \end{aligned}$$

63. (B) The closed loop system is stable for


$$8K < 1 \rightarrow K < \frac{1}{8}$$

$$0.2K < 1 \rightarrow K < 5$$

$$2K > 1 \rightarrow K > \frac{1}{2}$$


$$K < \frac{1}{8} \text{ or } \frac{1}{2} < K < 5$$

64. (C)

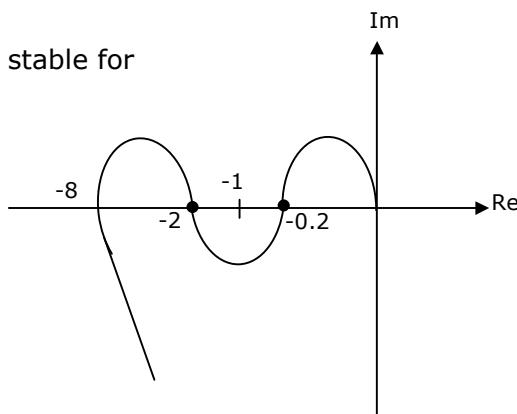


65. (A) $V_{out} = \pm 10V$; as $V_{supply} = \pm 10V$


When $V_o = 10V$

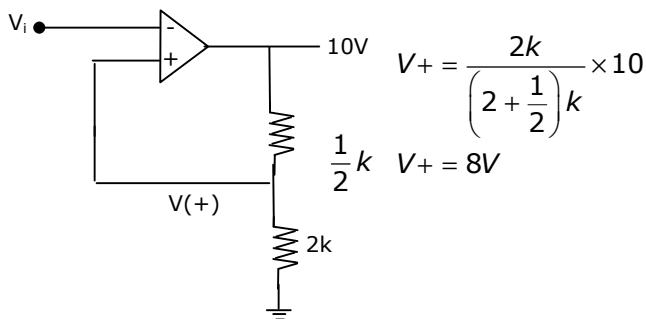

When $V_o = -10V$

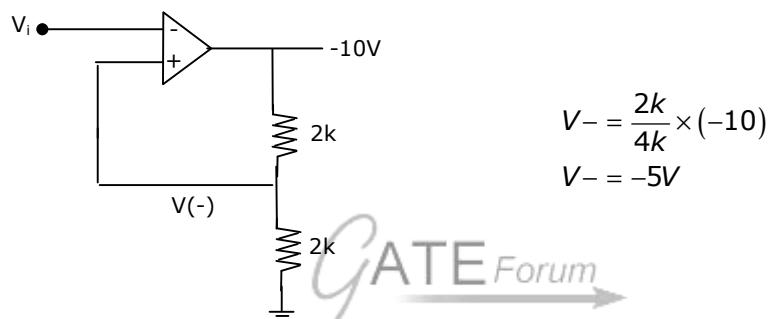

Hysteresis loop is

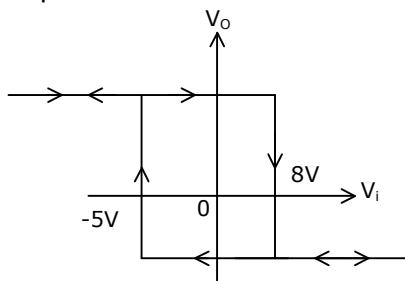

66. (A)

67. (A)

68. (C) The Rough sketch of the root locus is a circle.

$$\frac{d}{ds}[G(s)H(s)] = 0;$$

The breakaway point is

$$\frac{-s(s+3)-(1-s)(2s+3)}{s(s+3)} = 0 \Rightarrow s = 3 \text{ or } -1$$

Answer is C

69. (C)

70. (C) FM equation is

$$A \cos [\omega ct + \beta \sin \omega mt]$$

$$\beta = \frac{\Delta f}{f_m} = \frac{90}{5} = 18 = A \cos[\omega_c t + 18 \sin \omega_m t]$$

$$y(t) = x^2(t) = A^2 \cos^2 [\omega_c t + 18 \sin \omega_m t]$$

$$= A^2 \left[\frac{1}{2} + \frac{1}{2} \cos(2\omega_c t + 36 \sin \omega_m t) \right]$$


$$= \frac{A^2}{2} + \frac{A^2}{2} \cos(2\omega_c t + 36 \sin \omega_m t)$$

$$\beta = 36 = \frac{\Delta f}{f_m} \Rightarrow \Delta f = 36 \times 5 = 180$$

By carsons rule bandwidth = $2(\Delta f + f_m) = 2(180+5)$

$B\omega = 370$

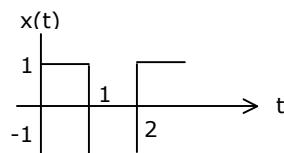71. (C) $x(t) = \mu(t) - 2\mu(t-1) + \mu(t-2)$ for $x(t)$




The impulse of a matched filter is delayed version of the input.

Now delay not given, so assumed to be zero.


$\therefore y(t) = x(t) * x(t)$ [$n(t) = x(t)$] where * represents convolution.

$$y(t) = r(t) - 4r(t-1) + 6r(t-2) - 4r(t-3) + r(t-4)$$

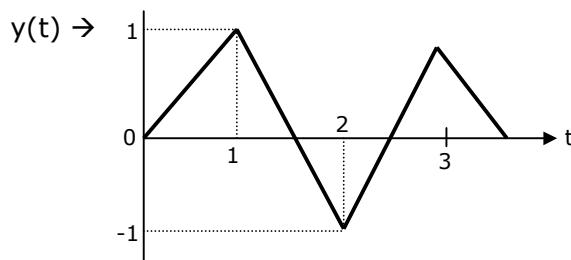Here $\mu(t) * \mu(t) = r(t)$ Ramp function.



72. (A)

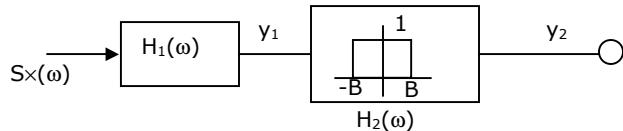

PSD of input $S \times (\omega) = N_o$ W/H2. $H_1(\omega) = 2e^{-j\omega t d}$

$$S y_1(\omega) |H_1(\omega)|^2 S \times (\omega) = 4N_o \text{ W/Hz}$$

$$S y_2(\omega) |H_2(\omega)|^2 S y_1(\omega) = 4N_o \text{ W/Hz}, -B \leq \omega \leq B$$

$$\text{Noise power} = \int_{-B}^B S y_2(\omega) d\omega = 2 \times 4N_o B = 8N_o B$$

73. ()

74. (C) From plot, $P(V) = \frac{k}{4}V$,

$$\int_0^4 P(V) dV = 1, \int_0^4 \frac{K}{4} V dV = 1 \Rightarrow K = \frac{1}{2}$$

$$\text{mean square value of } V = \int_0^4 VP(V) dV = \int_0^4 V \cdot \frac{K}{4} V dV$$

mean square value = 8.

75. (D)

76. (D)


$$Z_0 = \sqrt{Z_o c^2 S_c}$$

$$Z_{Sc} = \frac{Z_o^2}{Z_{oc}} = \frac{50^2}{100 + j150} = 7.69 - j11.54$$

$$Z_{Sc} = 7.69 - j11.54$$

77. (B)

78. () The equivalent circuit of JFET is

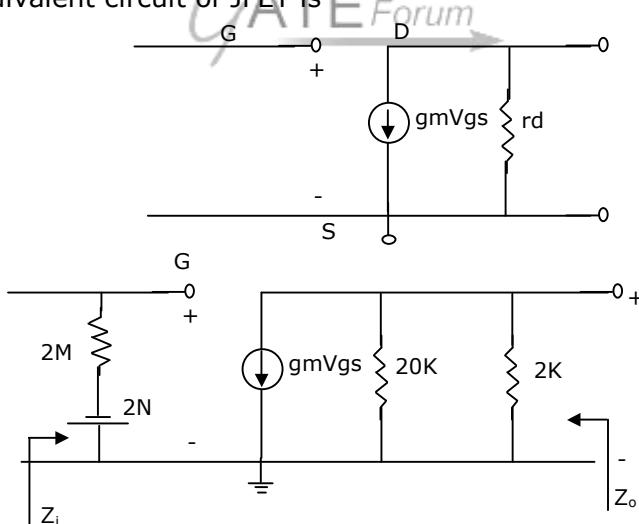

$$Z_i = 2M; Z_{out} = 20k \parallel 8k = \left(\frac{20}{11}\right)k\Omega$$

79. (A) $I_D = I_{DSS} \left(1 - \frac{VG_s}{V_p}\right)^2 = 10 \left(1 - \frac{2}{8}\right)^2 = 5.625$

$$I_D = 5.625 \text{ mA}$$

$$V_{DS} = 20 - 2k \times 5.625 = 8.75 \text{ V}$$

$$V_{DS} = 8.75 \text{ V}$$

80. (B)

$$gm = \frac{-2I_{DSS}}{V_P} \left[1 - \frac{VGs}{V_p} \right] = \frac{-2 \times 10mA}{-8} \left[1 - \frac{-2}{-8} \right]$$

$$gm = 1.875 \text{ msiemens}$$

$$\frac{V_0}{Vgs} = V_{gain} = -\left[\frac{20}{11} \right] KAgm = -3.41$$

$$AV = -3.41$$

81. (A) (C)

(B) (C)

82. (A) () Gain crossover frequency

gain of

$$\frac{3e^{-2s}}{s(s+2)} = \left| \frac{3e^{-2s}}{s(s+2)} \right| = 1$$

$$e^{-2s} = \cos(2\omega) - j \sin 2\omega; |e^{-2s}| = 1$$

$$\left| \frac{3}{j\omega(2+j\omega)} \right| = 1; \left| \frac{3}{-\omega^2 + j2\omega} \right| = 1$$

$$\omega = 1.26$$

phase crossover frequency

$$\text{phase angle} = -90 - \tan^{-1}\left(\frac{\omega}{2}\right) - 2\omega\left(\frac{180}{\pi}\right)$$

$$\text{phase} = -180 \Rightarrow -90 - \tan^{-1}\left(\frac{\omega}{2}\right) - 2\omega\left(\frac{180}{\pi}\right) = -180$$

$$\omega = 0.632$$

(B) ()

Gain margin

$$a = \text{Gain} = \left| \frac{3e^{-2s}}{s(s+2)} \right|_{\omega=0.632} = 2.2631$$

$$GM = 20\log\left(\frac{1}{a}\right) = -7.094dB$$

$$\text{Phase margin} = 180 + [-90 - \tan^{-1}\left(\frac{\omega}{2}\right) - 2\omega\left(\frac{180}{\pi}\right)]$$

$$\omega = 1.26$$

$$\text{Phase margin} = -86.59^\circ$$

83. (A) (B) Area of region 1 = Area of region 2 = Area of region 3

$$2a \times \frac{1}{4} = 2 \times \frac{1}{8} + \frac{(1-a)}{4} \Rightarrow a = \frac{2}{3}$$

(B) () Quantization noise power between $-a$ to $+a$ = $\int_{-\frac{2}{3}}^{\frac{2}{3}} x^2 p(x) dx$

$$= \int_{-\frac{2}{3}}^{\frac{2}{3}} \frac{x^2}{4} dx = \frac{x^3}{12} \Big|_{-\frac{2}{3}}^{\frac{2}{3}}$$

$$\text{Quantization noise power} = \frac{4}{81}$$

84. (A) (B)

$$V_{\max} = 4V$$

$$V_{\min} = 1V \quad V_{\max} = |V_i| + |V_r| [V_i = V_{\text{incident}}, V_r = V_{\text{reflected}}]$$

$$V_{\min} = |V_i| - |V_r|$$

$$V_i = 2.5, V_r = 1.5$$

$$K = \frac{V_r}{V_i} = \frac{1.5}{2.5} = 0.6$$

$$K = \frac{Z_R - 20}{Z_R + 20} = \frac{3}{5} = \frac{Z_R - 50}{Z_R + 50} \Rightarrow Z_R = 200\Omega$$

(B) (C) $K = 0.6 \rightarrow K = \frac{|V_r|}{|V_i|} = 0.6 (+ve)$

85. (A) (A) $y(2) = x(0) = 2$

$$y(4) = x(1) = 1$$

Answer is (A)

(B) (C) $y(2n) \left\{ \frac{1}{2}, 1, 2, 1, \frac{1}{2}, \dots \right\}$

Fourier transform of $y(n)$ is $\sum_{n=-\infty}^{\infty} y(n) e^{-j\omega n}$

$$y(2n) \square \frac{1}{2} e^{j\omega} + 1 + 2e^{-j\omega} + e^{j2\omega} + \frac{1}{2} e^{-j3\omega}$$

$$y(2n) \square e^{j\omega} [\cos 2\omega + 2 \cos \omega + 2]$$