

**MADE EASY**

India's Best Institute for IES, GATE &amp; PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Lucknow | Pune | Bhubaneswar | Kolkata | Patna

Web: [www.madeeasy.in](http://www.madeeasy.in) | E-mail: [info@madeeasy.in](mailto:info@madeeasy.in) | Ph: 011-45124612**ELECTRICAL ENGINEERING****Analog Electronics****Duration : 1:00 hr.****Maximum Marks : 50**


Read the following instructions carefully

1. This question paper contains **30** objective questions. **Q.1-10** carry one mark each and **Q.11-30** carry two marks each.
2. Answer all the questions.
3. Questions must be answered on Objective Response Sheet (**ORS**) by darkening the appropriate bubble (marked **A, B, C, D**) using HB pencil against the question number. Each question has only one correct answer. In case you wish to change an answer, erase the old answer completely using a good soft eraser.
4. There will be **NEGATIVE** marking. For each wrong answer **1/3rd** of the full marks of the question will be deducted. More than one answer marked against a question will be deemed as an incorrect response and will be negatively marked.
5. Write your name & Roll No. at the specified locations on the right half of the **ORS**.
6. No charts or tables will be provided in the examination hall.
7. Choose the **Closest** numerical answer among the choices given.
8. If a candidate gives more than one answer, it will be treated as a **wrong answer** even if one of the given answers happens to be correct and there will be same penalty as above to that questions.
9. If a question is left blank, i.e., no answer is given by the candidate, there will be **no penalty** for that question.

**DO NOT OPEN THIS TEST BOOKLET UNTIL YOU ARE ASKED TO DO SO**

## Q. No. 1 to Q. No. 10 carry 1 mark each

 Q.1 Consider the feedback amplifier shown in the figure below:



Then the amplifier is a

- (a) Voltage amplifier
- (b) Current Amplifier
- (c) Transresistance Amplifier
- (d) Transconductance Amplifier

Q.2 In a centre tap full-wave rectifier, 100 V is the peak voltage between the centre tap and one end of the secondary. What is the maximum voltage across the reverse biased diode?

- (a) 200 V
- (b) 141 V
- (c) 100 V
- (d) 86 V


Q.3 An op-amp with an open loop gain of 1000 V/V is used in the inverting configuration. If in this application, the output voltage ranges from +10 V to -10 V, then the maximum voltage by which the virtual ground node departs from its ideal value is equal to

- (a) +10 V from ideal voltage of  $V_0$
- (b) +10 mV from ideal voltage of  $V_0$
- (c) +10 V from ideal voltage of zero
- (d) +10 mV from ideal voltage of zero

Q.4 A BJT can act as a switch, when it changes from

- (a) cut-off to active region
- (b) active to saturation region
- (c) forward active mode to reverse active mode
- (d) saturation to cut-off region

 
Q.5 Consider the circuit shown in the figure below:



If the value of voltage on the secondary side of transformer is  $V_m(t) = V_m \sin(\omega t)$ , then the value of  $V_0$  is equal to

- (a)  $0.5V_m$
- (b)  $2V_m$
- (c)  $V_m$
- (d)  $-V_m$

 
Q.6 Consider the circuit shown in the figure below




If the cut-in voltage of the diode  $D_1$  is equal to 0.7 V, then the value of current flowing through the diode is

- (a) 0
- (b) 1 mA
- (c) 2 mA
- (d) 3 mA

 
Q.7 Consider a  $p-n-p$  common emitter amplifier shown in the figure below:



 
The transfer characteristic of the circuit can be approximately represented as





 

 Q.8 In the figure shown below, the voltage  $V_0$  is



- (a)  $|V_m \sin(\omega t)|$  (b)  $-2 V_m$   
(c)  $-|V_m \sin(\omega t)|$  (d)  $2 V_m$

Q.9 Which of the following statements is not correct?


- (a) MOSFETs have lower power dissipation than BJTs.  
(b) MOSFETs requires lower area for the process of fabrication than BJTs.  
(c) MOSFETs are less noise than BJTs.  
(d) MOSFETs can drive a larger current than BJTs due to presence of majority carriers only.

Q.10 A diode whose internal resistance is  $40 \Omega$ , is used to supply power to a  $1 \text{ k}\Omega$  load from a  $110 \text{ V}$  (RMS) source supply. Then the dc load current will be

- (a)  $149.58 \text{ mA}$  (b)  $47.61 \text{ mA}$   
(c)  $42 \text{ mA}$  (d)  $18.26 \text{ mA}$

Q. No. 11 to Q. No. 30 carry 2 marks each

 
Q.11 Consider the circuit shown in the figure below:



If the diodes  $D_1$  and  $D_2$  are ideal, then the value of  $V_0$  and  $I_0$  are respectively

- (a)  $1 \text{ V}$  and  $0.1 \text{ mA}$  (b)  $4 \text{ V}$  and  $0.1 \text{ mA}$   
(c)  $1 \text{ V}$  and  $0.4 \text{ mA}$  (d)  $4 \text{ V}$  and  $0.4 \text{ mA}$

 Q.12 Consider the circuit shown in the figure below:



The op-amp is having an open loop finite gain  $A_0$ . Rest of the parameters of op-amp is ideal. Then value of pole for the above circuit is located at

- (a)  $\frac{-A_0}{(RC+1)}$  (b)  $-A_0 RC$   
(c)  $\frac{A_0}{RC}$  (d)  $\frac{-(A_0+1)}{RC}$


Q.13 A negative feedback amplifier with open-

loop gain  $\frac{A_0}{1+j\frac{\omega}{\omega_0}}$  is connected with a

negative feedback circuit with  $A_0 > 0$  and feedback factor  $\beta (> 0)$ . The 3 dB cut-off frequency at which the gain of the resultant feedback circuit reduces by a factor of 0.707 is

- (a)  $\omega_0 A_0 \beta$  (b)  $\omega_0 (1 + A_0 \beta)$   
(c)  $\omega_0 / (1 + A_0 \beta)$  (d)  $\omega_0 (1 - A_0 \beta)$

 
- Q.14 Consider the circuit shown in the figure below:



A diode  $D_1$  is connected in parallel with a diode  $D_2$  with reverse saturation current equal to  $10^{-12}$  A and  $10^{-10}$  A respectively. The diodes are connected across a voltage source ( $V_s$ ) in series with a resistance of 1 kΩ. Then the value of voltage ' $V_s$ ' is approximately equal to

- (Assuming  $\eta = 1$  and  $V_{Th} = 26$  mV)  
 (a) 5.241 V (b) 2.004 V  
 (c) 2.436 V (d) 4.444 V


- Q.15 In the figure shown below,

 

The  $V_{out}$  of the circuit is \_\_\_\_\_. (Assume the cut in voltage of the diode  $V_Y = 0.7$  V)


- (a) 8.4 V (b) 6.2 V  
 (c) 9.2 V (d) 0 V

 - Q.16 For the operational amplifier circuit shown, the output saturation voltage are  $\pm 15$  V. The upper and lower threshold voltages for the circuit are respectively,




- (a) +5 V and -5 V (b) +7 V and -3 V  
 (c) +3 V and -7 V (d) +3 V and -3 V

 - Q.17 In the following circuit, if the op-amp is ideal, then the minimum required value of the ratio  $R_2/R_1$  to produce sustained oscillations will be



- (a) 1 (b) 2  
 (c) 3 (d) 4

- Q.18 Consider the BJT shown below:

 


Which of the following relation is correct?

- (a)  $I_C + I_E + \beta I_B = 0$   
 (b)  $I_C = \beta I_B + \frac{1}{1 + \beta} I_{CO}$   
 (c)  $I_C = \beta I_B + \frac{1}{1 - \alpha} I_{CO}$   
 (d)  $I_C = \alpha I_B + (1 + \beta) I_{CO}$

- Q.19 A Bipolar junction transistor has  $\alpha = 0.98$ , base current  $I_B = 25$   $\mu$ A and  $I_{CBO} = 200$  nA. The emitter current is

- (a) 1.05 mA (b) 1.235 mA  
 (c) 1.33 mA (d) 1.26 mA

 
- Q.20 Consider the circuit shown in the figure below:



The diode ' $D$ ' can be modeled as a battery of voltage  $V_Y$  in series with a resistor ' $r_f$ ' when biased in forward direction. If the value of resistance  $R = 1$  kΩ, then the value of resistance  $r_f$  is equal to


- (a) 0.923  $\Omega$  (b) 7.133  $\Omega$   
 (c) 83.33  $\Omega$  (d) 101.33  $\Omega$

 **Q.21** In the diode circuit shown below, the value of voltage  $V_A$  is (Assume  $V_Y = 0.7$  V for each diode)




- (a) 2 V (b) 0 V  
(c) 1.75 V (d) -2.15 V

 **Q.22** The 6 V zener diode shown below has zero zener resistance and a knee current of 5 mA. The minimum value of  $R$ , so that the voltage across it does not fall below 6 V is




- (a) 1.2 kΩ (b) 50 Ω  
(c) 80 Ω (d) 0 Ω

 **Q.23** In the circuit shown below, transistor M1 is in saturation and has transconductance  $g_m = 0.01$  S. Ignoring internal parasitic capacitances and assuming the channel length modulation  $\lambda$  to be zero, then the small signal input pole frequency (in kHz) is



- (a) 57.87 kHz (b) 75.78 kHz  
(c) 87.57 kHz (d) None

 
**Q.24** Assuming that the op-amp in the circuit shown is ideal,



The output voltage  $V_O$  is

- (a)  $\frac{5}{2}V_1 - 3V_2$  (b)  $2V_1 - \frac{5}{2}V_2$   
(c)  $\frac{-3}{2}V_1 + \frac{7}{2}V_2$  (d)  $-3V_1 + \frac{11}{2}V_2$

 
**Q.25** Consider the circuit shown in the figure. Assume base-to-emitter voltage  $V_{BE} = 0.8$  V and common-base current gain ( $\alpha$ ) of the transistor is unity.



The value of the collector-to-emitter voltage  $V_{CE}$

- (a) 3 V (b) 4 V  
(c) 5 V (d) 6 V

 
**Q.26** In the circuit shown below, the condition to be satisfied such that the silicon transistor will never enter into saturation is (Assume  $V_{BE} = 0.7$  V,  $V_{CE(sat)} = 0$  V)



- (a)  $R_B < 232.5$  kΩ (b)  $R_B > 232.5$  kΩ  
(c)  $R_B < 116.25$  kΩ (d)  $R_B > 116.25$  kΩ



 
Q.27 Consider a differential amplifier as shown below,



Where the first set of signals is  $V_1 = 50 \mu\text{V}$ ,  $V_2 = -50 \mu\text{V}$  and the second set of signals is  $V_1 = 1050 \mu\text{V}$ ,  $V_2 = 950 \mu\text{V}$ . If the common mode rejection ratio is 100, then the percentage difference in output voltage obtained for the two sets of input signals is

- (a) 10%                      (b) 15%  
(c) 20%                      (d) 25%

 Q.28 The op-amp shown in the figure is ideal,  $R_1 = 20 \text{ k}\Omega$ ,  $R_2 = 40 \text{ k}\Omega$  and  $C = 10 \mu\text{F}$ :




If  $V_{in}(t) = 2e^{-2t} u(t) \text{ V}$  and  $V_c(0) = 0$ , then  $V_o(t)$  is

- (a)  $10 e^{-2t} u(t) + 10 e^{-2.5t} u(t)$   
(b)  $-20 e^{-2.5t} u(t) + 20 e^{-2t} u(t)$   
(c)  $-10 e^{-2t} u(t) - 10 e^{-2.5t} u(t)$   
(d)  $20 e^{-2.5t} u(t) - 20 e^{-2t} u(t)$

Q.29 For a practical integrator, the component values are  $R_1 = 120 \text{ k}\Omega$ ,  $R_F = 1.2 \text{ M}\Omega$  and the capacitor  $C_F = 10 \text{ nF}$ . The dc gain of the integrator is

- (a) 10 dB                      (b) 20 dB  
(c) 30 dB                      (d) 40 dB

 Q.30 In the circuit below, a filter capacitor  $C$  is used to smooth out the pulses from the full wave rectifier.



The value of capacitor  $C$  to maintain the peak to peak ripple voltage as 1% of maximum value of input voltage ( $V_{\text{max}}$ ) is

- (a)  $10 \mu\text{F}$                       (b)  $50 \mu\text{F}$   
(c)  $75 \mu\text{F}$                       (d)  $100 \mu\text{F}$

■■■■