


ELECTRICAL ENGINEERING

Power Electronics


Multiple Select Questions : Workbook Sheet



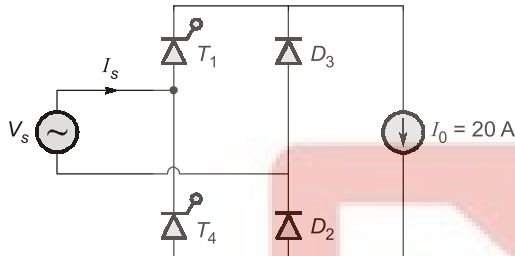- Q.1** Consider the bridge rectifier shown below. If RMS value of source current is 10 A, then which of the following is/are correct?



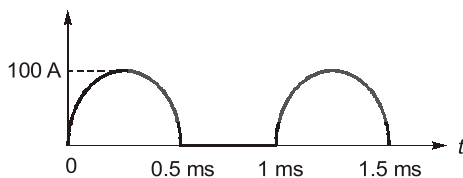- (a) Firing angle for the thyristors is $\frac{3\pi}{4}$.
- (b) RMS value of thyristor current is 7.07 A.
- (c) Average current of each diode is 10 A.
- (d) RMS value of each diode is 10 A.
- Q.2** A thyristor is used in an application carrying half sinusoidal current of period of 1 msec and a peak of 100 A as shown in figure. The thyristor may modeled during conduction to have a constant voltage drop of 1.1 V and a dynamic resistance of 8 m Ω . Then which of the following is/are correct?




- (a) Average current through thyristor is $\frac{100}{\pi}$ A.
- (b) rms current through thyristor is $\frac{100}{\sqrt{2}}$ A.
- (c) Conduction losses are 55 W.
- (d) rms current through thyristor is 50 A.

- Q.3** A single phase asymmetrical semiconverter feeds an RL load with $R = 10 \Omega$ and large L so that load current is ripple free. The source voltage to the bridge is 200 V, 50 Hz. For a firing angle of 30° , which of the following is/are correct?
- (a) Average output voltage is 168 V.
- (b) Average output current is 1.68 A.
- (c) rms current through diode is 12.83 A.
- (d) Average current through diode is 8.4 A.

- Q.4** An ideal chopper operating at a frequency of 500 Hz, supplies a load having resistance of 3 Ω and inductance of 9 mH from a 60 V battery. The switch on/off ratio is 4/1, then which of the following is/are correct?
- (a) Duty ratio of chopper is 0.8
- (b) Duty ratio of chopper is 0.6
- (c) Average output voltage is 36 V
- (d) Average output voltage is 48 V


- Q.5** A 1- ϕ diode rectifier is feeding a capacitor load. The supply is 230 V, 50 Hz and capacitor is 1 μ F. Then which of the following is/are correct?
- (a) The conduction time of diode is 90° .
- (b) The conduction time of diode is 180° .
- (c) The final voltage across capacitor is 230 V.
- (d) The final voltage across capacitor is $230\sqrt{2}$.

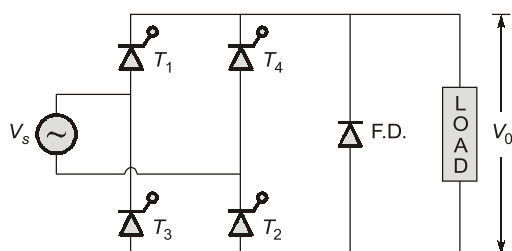- Q.6** A single phase full bridge converter with a freewheeling diode feeds an inductive load. The load resistance is 15.53 Ω and it has a large inductance providing constant and ripple free d.c. current. Input to converter is from an ideal 230 V, 50 Hz. Single phase source, for a firing delay angle of 60° .



- (a) average output current is 10 A
- (b) average current through free wheeling diode is 3.33 A
- (c) average output current is 20 A
- (d) average current through free wheeling diode is 5 A.

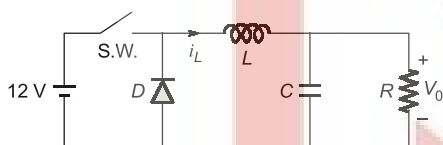
Q.7 A buck converter is shown in the figure. The switch is operating at 25 kHz.



For an average output voltage of 5 V, which of the following is/are correct?

- (a) For $\Delta V_0 = 20$ mV and $\Delta i_L = 0.8$ A, the value of capacitance is 200 μ F
- (b) For $\Delta V_0 = 10$ mV and $\Delta i_L = 0.8$ A, the value of capacitance is 400 μ F
- (c) For $\Delta V_0 = 20$ mV and $\Delta i_L = 0.8$ A, the value of capacitance is 100 μ F
- (d) For $\Delta V_0 = 10$ mV and $\Delta i_L = 0.8$ A, the value of capacitance is 200 μ F

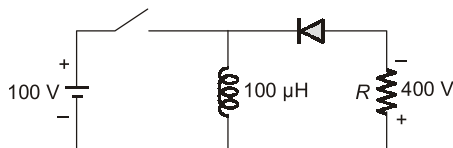Q.8 In the following circuit the ideal switch S is operated at 10 kHz then the circuit is operated in steady state at the boundary of the continuous and discontinuous then which of the following is/are correct?



- (a) The duty ratio of the converter is 0.8
- (b) The duty ratio of the converter is 0.6
- (c) Critical resistance of the converter is 40 Ω
- (d) Critical resistance of the converter is 25 Ω

Q.9 A thyristor string is formed by series and parallel connection of thyristors. The voltage and current ratings of the string are 11 kV, 4 kA respectively. The thyristor to be employed has voltage and current ratings of 1.7 kV, 1 kA. The string efficiency is 90 for both series and parallel combination. If the maximum blocking current is 15 mA and maximum charge storage ΔQ_{\max} is 24 μ C. Then which one of the following is/are correct?

- (a) Number of thyristors in series must be 7.
- (b) Number of thyristors in series must be 8.
- (c) The capacitance of equalizer circuit is 64.6 μ F
- (d) The capacitance of equalizer circuit is 46.6 μ F

Q.10 A single SCR is inserted in between voltage source $200 \sin 314 t$ and a resistive load of 10 Ω . If the gate trigger voltage lags the A.C. supply voltage by 120° , then which of the following is/are correct?

- (a) The average load current is $\frac{15}{\pi}$ A
- (b) The average load voltage is $\frac{150}{\pi}$ V
- (c) The average load current is $\frac{5}{\pi}$ A
- (d) The average load voltage is $\frac{50}{\pi}$ V


Q.11 In a dc - dc step down converter, if D , f , V_s , L and R are duty ratio, switching frequency, source average voltage, inductance and load resistance respectively, then

- (a) The average output voltage is $D \cdot V_s$
- (b) Critical inductance is $\frac{(1-D)R}{2f}$.
- (c) Peak to peak ripple current of inductor is $\frac{V_s(1-D)D}{fL}$
- (d) Average source current is $\frac{D^2 V_s}{R}$

Q.12 A 3- ϕ , thyristor controlled rectifier is feeding a purely resistive load on the DC side. AC side is connected to a balanced 3- ϕ supply. Then which of the following is/are correct?

- (a) The maximum firing angle for 12-pulse converter is 105° .
- (b) The maximum firing angle for 6-pulse converter is 120° .
- (c) The maximum firing angle for 3-pulse converter is 150° .
- (d) The maximum firing angle for 2-pulse converter is 150° .

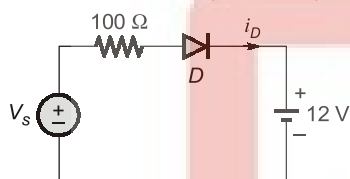Q.13 For the diode circuit shown in figure below if V_s is a sinusoid with 24 V peak amplitude, then



- (a) The maximum reverse bias voltage that appears across the diode is 36 V.
- (b) The fraction of period during which the diode conduction each cycle is $\frac{T}{4}$.
- (c) The maximum reverse bias voltage that appears across the diode is 24 V.
- (d) The fraction of period during which the diode conducts in each cycle is $\frac{T}{3}$.

Q.14 A single phase auto sequential commutated CSI is fed from 220 V dc source. The load is $R = 12 \Omega$ from a 240 V dc source. If the inverter output frequency is 60 Hz, thyristor turnoff time 15 μ s and factor of safety 2, then (neglect all losses and assume a maximum current change of 0.4 in one cycle). Which of the following is/are correct?


- (a) The source inductance is 5 H.
- (b) The commutating capacitor is 2 μ F.
- (c) The source inductance is 10 H.
- (d) The commutating capacitance is 3.6 μ F.

Q.15 A 3- ϕ , three pulse converter fed from 3-phase, 400 V, 50 Hz supply has a load $R = 2 \Omega$ per phase, $E = 230$ V and large inductance so that

load current is 25 A level. If source has an inductance value of 2 mH. Then which of the following is/are correct?

- (a) firing angle = 129.7°
- (b) overlap angle = 4.27°
- (c) firing angle = 133.4°
- (d) overlap angle = 6.52°

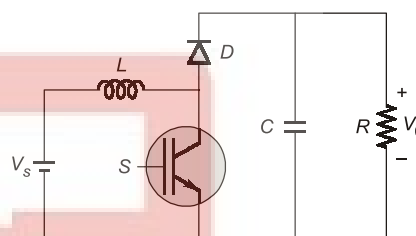Q.16 A converter shown in the figure below is operating with $V_{in} = 5$ V, $V_0 = 12$ V and $P_0 = 11$ W. It is operating in dc steady state with $f_s = 200$ kHz and $\Delta I_L = 2$ A, then which of the following is/are correct?



- (a) Duty ratio = 0.5333
- (b) Inductance, $L = 7.29 \mu$ H
- (c) Inductance, $L = 7.72 \mu$ H
- (d) Duty ratio = 0.5833

Q.17 Which of the following is/are correct about Buck boost converter?

- (a) at duty ratio 60%, the converter acts as buck converter.
- (b) at duty ratio 40%, the converter acts as boost converter.
- (c) at duty ratio 60%, the converter acts as boost converter.
- (d) at duty ratio 40%, the converter acts as buck converter.

Q.18 Which of the following is/are correct about buck converter?

- (a) when the switch is on, the inductor absorbs energy.
- (b) when the switch is off, the inductor delivers energy.
- (c) when the switch is on, the inductor delivers energy.
- (d) when the switch is off, the inductor absorbs energy.

■■■■