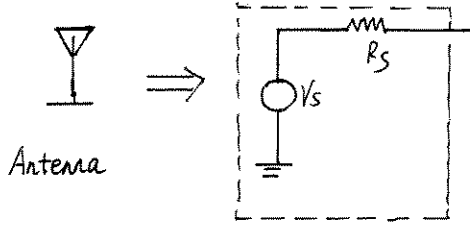



1)



Thevenin Equivalent:

$$V_s = V_0 \cos \omega t$$

$$R_s = R_{out}$$

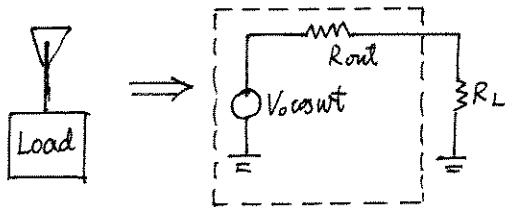

Average power delivered to load = $(I_{RMS})^2 R_L$,

$$I_{RMS} = \frac{V_{RMS}}{R_{out} + R_L}, \quad V_{RMS} = \frac{V_0}{\sqrt{2}} \Rightarrow I_{RMS} = \frac{V_0}{\sqrt{2}(R_{out} + R_L)}$$

$$\text{Average power} = (I_{RMS})^2 R_L = \frac{V_0^2 R_L}{2(R_{out} + R_L)^2} \quad (\text{Eq. 1})$$

Plot of Average Power

When R_L is small, Eq. 1 is small.

When R_L is large, Eq. 1 is also small.


So for some R_L between zero and infinity, the average power will reach its peak. Let's take the derivative of Eq. 1 with respect to R_L to find the optimum R_L .

$$\frac{\partial}{\partial R_L} \left[\frac{V_0^2 R_L}{2(R_{out} + R_L)^2} \right] = \frac{V_0^2}{2(R_{out} + R_L)^2} - \frac{V_0^2 R_L}{(R_{out} + R_L)^3}$$


Setting it to zero and solve for R_L

$$\frac{V_0^2}{2(R_{out} + R_L)^2} = \frac{V_0^2 R_L}{(R_{out} + R_L)^3} \Rightarrow \frac{(R_{out} + R_L)}{2} = R_L$$

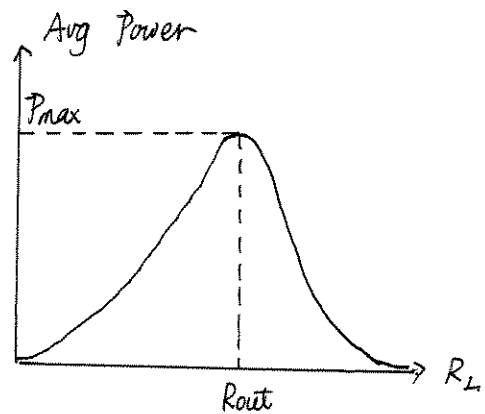
$$\Rightarrow R_{out} + R_L = 2R_L \Rightarrow R_L = R_{out}$$



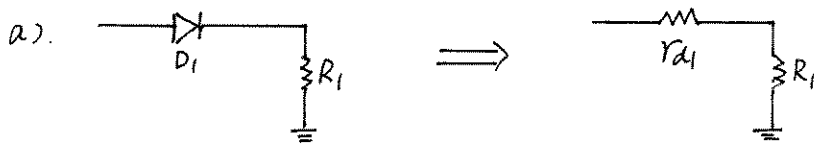
2) In small signal operation, a diode can be replaced by a linear resistor if charges are small.



$$R_{in} = r_{d1} + R_1$$

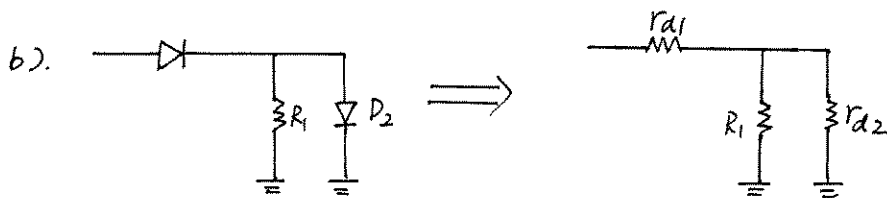

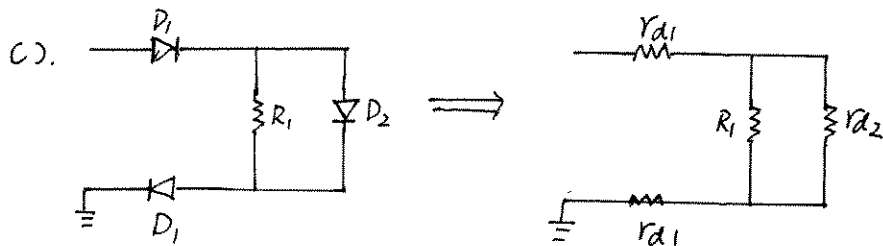
$$R_{in} = r_{d1} + R_1 // r_{d2} \quad (// \text{ means in parallel })$$




$$R_{in} = 2r_{d1} + R_1 // r_{d2}$$

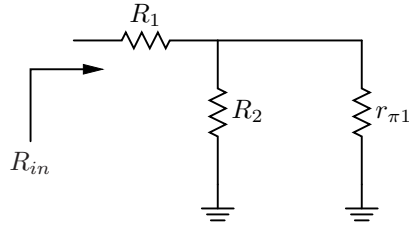- 5.3 (a) Looking into the base of Q_1 we see an equivalent resistance of $r_{\pi 1}$, so we can draw the following equivalent circuit for finding R_{in} :




$$R_{in} = R_1 + R_2 \parallel r_{\pi 1}$$

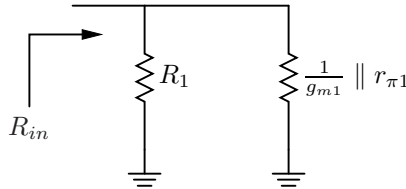- (b) Looking into the emitter of Q_1 we see an equivalent resistance of $\frac{1}{g_{m1}} \parallel r_{\pi 1}$, so we can draw the following equivalent circuit for finding R_{in} :




$$R_{in} = R_1 \parallel \left(\frac{1}{g_{m1}} \parallel r_{\pi 1} \right)$$

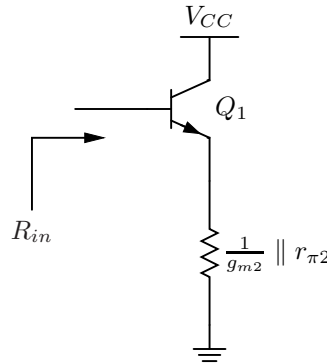- (c) Looking down from the emitter of Q_1 we see an equivalent resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2}$, so we can draw the following equivalent circuit for finding R_{in} :




$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

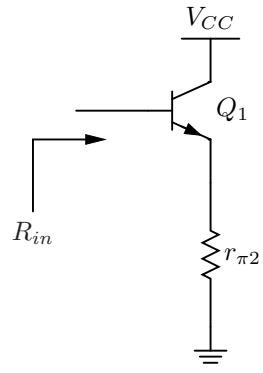- (d) Looking into the base of Q_2 we see an equivalent resistance of $r_{\pi 2}$, so we can draw the following equivalent circuit for finding R_{in} :




$$R_{in} = r_{\pi 1} + (1 + \beta_1)r_{\pi 2}$$

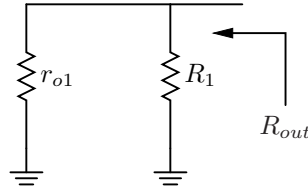- 5.4 (a) Looking into the collector of Q_1 we see an equivalent resistance of r_{o1} , so we can draw the following equivalent circuit for finding R_{out} :



$$R_{out} = r_{o1} \parallel R_1$$

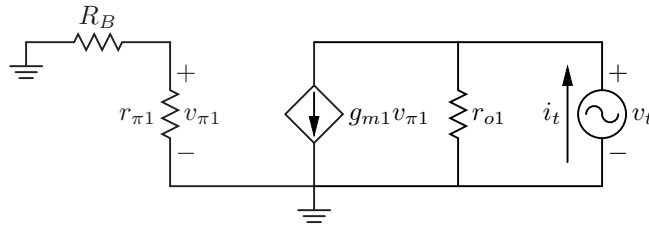- (b) Let's draw the small-signal model and apply a test source at the output.




$$i_t = g_{m1}v_{\pi 1} + \frac{v_t}{r_{o1}}$$

$$v_{\pi 1} = 0$$

$$i_t = \frac{v_t}{r_{o1}}$$


$$R_{out} = \frac{v_t}{i_t} = r_{o1}$$

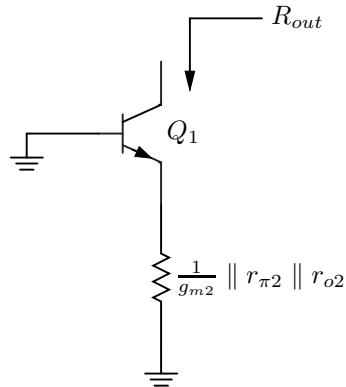- (c) Looking down from the emitter of Q_1 we see an equivalent resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}$, so we can draw the following equivalent circuit for finding R_{out} :




$$R_{out} = r_{o1} + (1 + g_{m1}r_{o1}) \left(r_{\pi 1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

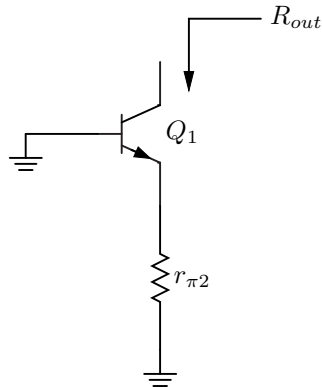- (d) Looking into the base of Q_2 we see an equivalent resistance of $r_{\pi 2}$, so we can draw the following equivalent circuit for finding R_{out} :




$$R_{out} = \boxed{r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi 1} \parallel r_{\pi 2})}$$

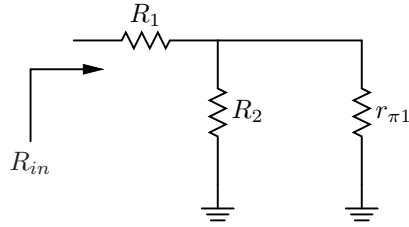- 5.5 (a) Looking into the base of Q_1 we see an equivalent resistance of $r_{\pi 1}$, so we can draw the following equivalent circuit for finding R_{in} :



$$R_{in} = R_1 + R_2 \parallel r_{\pi 1}$$

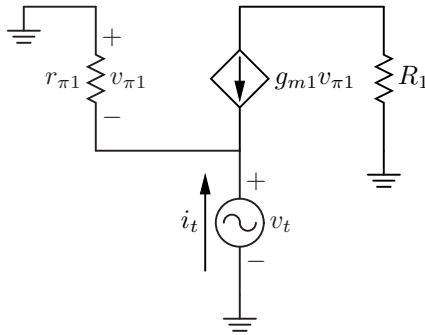- (b) Let's draw the small-signal model and apply a test source at the input.



$$i_t = -\frac{v_{\pi 1}}{r_{\pi 1}} - g_{m1}v_{\pi 1}$$


$$v_{\pi 1} = -v_t$$

$$i_t = \frac{v_t}{r_{\pi 1}} + g_{m1}v_t$$

$$i_t = v_t \left(g_{m1} + \frac{1}{r_{\pi 1}} \right)$$


$$R_{in} = \frac{v_t}{i_t} = \frac{1}{g_{m1}} \parallel r_{\pi 1}$$

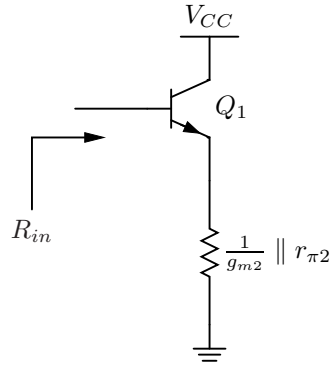- (c) From our analysis in part (b), we know that looking into the emitter we see a resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2}$. Thus, we can draw the following equivalent circuit for finding R_{in} :



$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

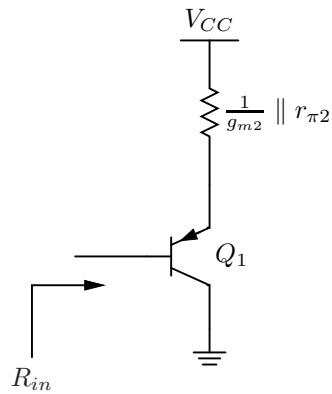
- (d) Looking up from the emitter of Q_1 we see an equivalent resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2}$, so we can draw the following equivalent circuit for finding R_{in} :



$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$


- (e) We know that looking into the base of Q_2 we see $R_{in} = r_{\pi 2}$ if the emitter is grounded. Thus, transistor Q_1 does not affect the input impedance of this circuit.

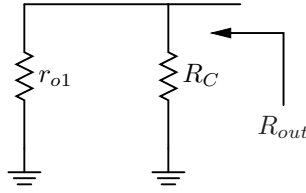- 5.6 (a) Looking into the collector of Q_1 we see an equivalent resistance of r_{o1} , so we can draw the following equivalent circuit for finding R_{out} :



$$R_{out} = R_C \parallel r_{o1}$$

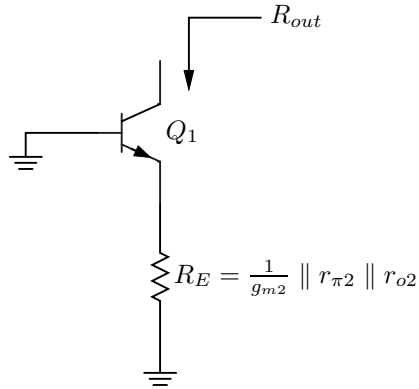- (b) Looking into the emitter of Q_2 we see an equivalent resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}$, so we can draw the following equivalent circuit for finding R_{out} :



$$R_{out} = r_{o1} + (1 + g_{m1}r_{o1}) \left(r_{\pi 1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

5.7 (a)

$$\begin{aligned}V_{CC} - I_B(100 \text{ k}\Omega) &= V_{BE} = V_T \ln(I_C/I_S) \\V_{CC} - \frac{1}{\beta}I_C(100 \text{ k}\Omega) &= V_T \ln(I_C/I_S) \\I_C &= \boxed{1.754 \text{ mA}} \\V_{BE} &= V_T \ln(I_C/I_S) = \boxed{746 \text{ mV}} \\V_{CE} &= V_{CC} - I_C(500 \text{ }\Omega) = \boxed{1.62 \text{ V}}\end{aligned}$$

Q_1 is operating in forward active.

(b)

$$\begin{aligned}I_{E1} = I_{E2} &\Rightarrow V_{BE1} = V_{BE2} \\V_{CC} - I_{B1}(100 \text{ k}\Omega) &= 2V_{BE1} \\V_{CC} - \frac{1}{\beta}I_{C1}(100 \text{ k}\Omega) &= 2V_T \ln(I_{C1}/I_S) \\I_{C1} = I_{C2} &= \boxed{1.035 \text{ mA}} \\V_{BE1} = V_{BE2} &= \boxed{733 \text{ mV}} \\V_{CE2} = V_{BE2} &= \boxed{733 \text{ mV}} \\V_{CE1} &= V_{CC} - I_C(1 \text{ k}\Omega) - V_{CE2} \\&= \boxed{733 \text{ mV}}\end{aligned}$$

Both Q_1 and Q_2 are at the edge of saturation.

(c)

$$\begin{aligned}V_{CC} - I_B(100 \text{ k}\Omega) &= V_{BE} + 0.5 \text{ V} \\V_{CC} - \frac{1}{\beta}I_C(100 \text{ k}\Omega) &= V_T \ln(I_C/I_S) + 0.5 \text{ V} \\I_C &= \boxed{1.262 \text{ mA}} \\V_{BE} &= \boxed{738 \text{ mV}} \\V_{CE} &= V_{CC} - I_C(1 \text{ k}\Omega) - 0.5 \text{ V} \\&= \boxed{738 \text{ mV}}\end{aligned}$$

Q_1 is operating at the edge of saturation.


5.8 See Problem 7 for the derivation of I_C for each part of this problem.

(a)

$$I_{C1} = 1.754 \text{ mA}$$

$$g_{m1} = I_{C1}/V_T = \boxed{67.5 \text{ mS}}$$
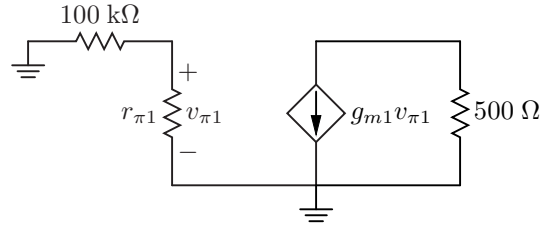
$$r_{\pi1} = \beta/g_{m1} = \boxed{1.482 \text{ k}\Omega}$$




(b)

$$I_{C1} = I_{C2} = 1.034 \text{ mA}$$

$$g_{m1} = g_{m2} = I_{C1}/V_T = \boxed{39.8 \text{ mS}}$$
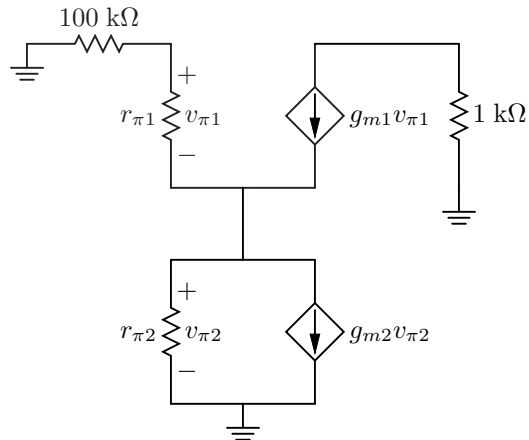
$$r_{\pi1} = r_{\pi2} = \beta/g_{m1} = \boxed{2.515 \text{ k}\Omega}$$




(c)

$$I_{C1} = 1.26 \text{ mA}$$

$$g_{m1} = I_{C1}/V_T = \boxed{48.5 \text{ mS}}$$
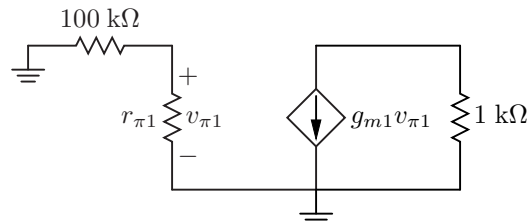
$$r_{\pi1} = \beta/g_{m1} = \boxed{2.063 \text{ k}\Omega}$$



5.9 (a)

$$\begin{aligned} \frac{V_{CC} - V_{BE}}{34 \text{ k}\Omega} - \frac{V_{BE}}{16 \text{ k}\Omega} &= I_B = \frac{I_C}{\beta} \\ I_C &= \beta \frac{V_{CC} - V_T \ln(I_C/I_S)}{34 \text{ k}\Omega} - \beta \frac{V_T \ln(I_C/I_S)}{16 \text{ k}\Omega} \\ I_C &= \boxed{677 \text{ }\mu\text{A}} \\ V_{BE} &= \boxed{726 \text{ mV}} \\ V_{CE} &= V_{CC} - I_C(3 \text{ k}\Omega) = \boxed{468 \text{ mV}} \end{aligned}$$

Q_1 is in soft saturation.

(b)

$$\begin{aligned} I_{E1} &= I_{E2} \\ \Rightarrow I_{C1} &= I_{C2} \\ \Rightarrow V_{BE1} &= V_{BE2} = V_{BE} \\ \frac{V_{CC} - 2V_{BE}}{9 \text{ k}\Omega} - \frac{2V_{BE}}{16 \text{ k}\Omega} &= I_{B1} = \frac{I_{C1}}{\beta} \\ I_{C1} &= \beta \frac{V_{CC} - 2V_T \ln(I_{C1}/I_S)}{9 \text{ k}\Omega} - \beta \frac{2V_T \ln(I_{C1}/I_S)}{16 \text{ k}\Omega} \\ I_{C1} = I_{C2} &= \boxed{1.72 \text{ mA}} \\ V_{BE1} = V_{BE2} = V_{CE2} &= \boxed{751 \text{ mV}} \\ V_{CE1} = V_{CC} - I_{C1}(500 \text{ }\Omega) - V_{CE2} &= \boxed{890 \text{ mV}} \end{aligned}$$

Q_1 is in forward active and Q_2 is on the edge of saturation.

(c)

$$\begin{aligned} \frac{V_{CC} - V_{BE} - 0.5 \text{ V}}{12 \text{ k}\Omega} - \frac{V_{BE} + 0.5 \text{ V}}{13 \text{ k}\Omega} &= I_B = \frac{I_C}{\beta} \\ I_C &= \beta \frac{V_{CC} - V_T \ln(I_C/I_S) - 0.5 \text{ V}}{12 \text{ k}\Omega} - \beta \frac{V_T \ln(I_C/I_S) + 0.5 \text{ V}}{13 \text{ k}\Omega} \\ I_C &= \boxed{1.01 \text{ mA}} \\ V_{BE} &= \boxed{737 \text{ mV}} \\ V_{CE} &= V_{CC} - I_C(1 \text{ k}\Omega) - 0.5 \text{ V} = \boxed{987 \text{ mV}} \end{aligned}$$

Q_1 is in forward active.


5.10 See Problem 9 for the derivation of I_C for each part of this problem.

(a)

$$I_C = 677 \mu\text{A}$$

$$g_m = I_C/V_T = \boxed{26.0 \text{ mS}}$$
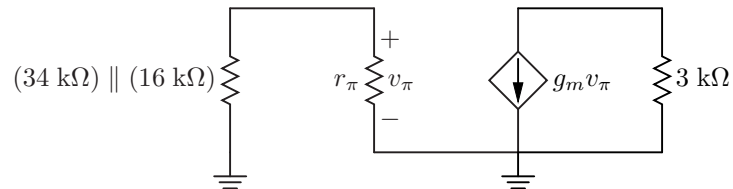
$$r_\pi = \beta/g_m = \boxed{3.84 \text{ k}\Omega}$$




(b)

$$I_{C1} = I_{C2} = 1.72 \text{ mA}$$

$$g_{m1} = g_{m2} = I_{C1}/V_T = \boxed{66.2 \text{ mS}}$$
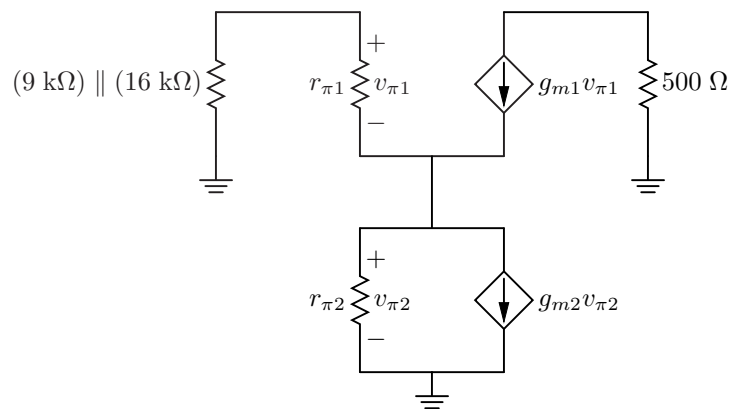
$$r_{\pi1} = r_{\pi2} = \beta/g_{m1} = \boxed{1.51 \text{ k}\Omega}$$




(c)

$$I_C = 1.01 \text{ mA}$$

$$g_m = I_C/V_T = \boxed{38.8 \text{ mS}}$$
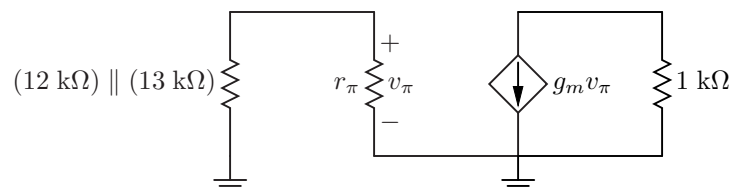
$$r_\pi = \beta/g_m = \boxed{2.57 \text{ k}\Omega}$$



5.11 (a)

$$V_{CE} \geq V_{BE} \text{ (in order to guarantee operation in the active mode)}$$

$$V_{CC} - I_C(2 \text{ k}\Omega) \geq V_{BE}$$

$$V_{CC} - I_C(2 \text{ k}\Omega) \geq V_T \ln(I_C/I_S)$$

$$I_C \leq 886 \text{ }\mu\text{A}$$

$$\frac{V_{CC} - V_{BE}}{R_B} - \frac{V_{BE}}{3 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$\frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} - \frac{V_T \ln(I_C/I_S)}{3 \text{ k}\Omega} = \frac{I_C}{\beta}$$

$$R_B \left(\frac{I_C}{\beta} + \frac{V_T \ln(I_C/I_S)}{3 \text{ k}\Omega} \right) = V_{CC} - V_T \ln(I_C/I_S)$$

$$R_B = \frac{V_{CC} - V_T \ln(I_C/I_S)}{\frac{I_C}{\beta} + \frac{V_T \ln(I_C/I_S)}{3 \text{ k}\Omega}}$$

$$R_B \geq \boxed{7.04 \text{ k}\Omega}$$

(b)

$$\frac{V_{CC} - V_{BE}}{R_B} - \frac{V_{BE}}{3 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$



$$I_C = \beta \frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} - \beta \frac{V_T \ln(I_C/I_S)}{3 \text{ k}\Omega}$$

$$I_C = 1.14 \text{ mA}$$

$$V_{BE} = 735 \text{ mV}$$

$$V_{CE} = V_{CC} - I_C(2 \text{ k}\Omega) = 215 \text{ mV}$$
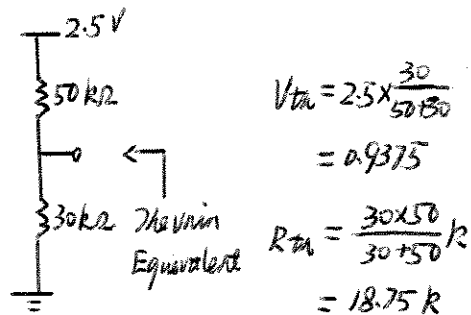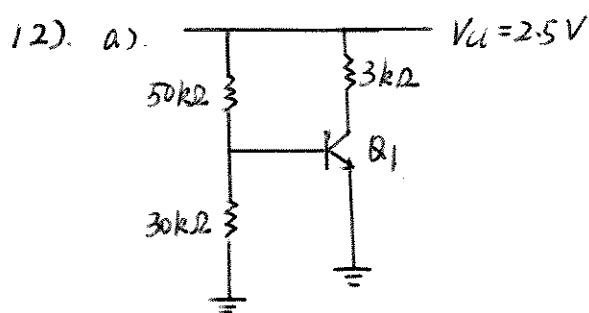
$$V_{BC} = V_{BE} - V_{CE} = \boxed{520 \text{ mV}}$$



Since $I_C = 0.5 \text{ mA}$, $I_B = \frac{I_C}{\beta} = 0.005 \text{ mA}$.

$$I_B = \frac{V_{th} - V_{BE}}{R_{th}} \Rightarrow V_{BE} = V_{th} - I_B \cdot R_{th} = 0.84375$$

$$I_C = I_S e^{\left(\frac{V_{BE}}{V_T}\right)} \Rightarrow I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = 4.03 \times 10^{-15} \text{ (mA)}$$

b). At the edge of saturation means $V_{BE} - V_{CE} = 0$.

(soft saturation not allowed)

$$V_{CE} = 2.5 - I_C \cdot (3k), \text{ in which } I_C = \beta I_B = \beta \left(\frac{V_{th} - V_{BE}}{R_{th}} \right)$$

$$\text{SO } V_{BE} = 2.5 - \beta \left(\frac{V_{th} - V_{BE}}{R_{th}} \right) \cdot (3k)$$

Solve this equation:

$$V_{BE} = 0.83.$$

$$I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = \frac{\beta \left(\frac{V_{th} - V_{BE}}{R_{th}} \right)}{e^{\left(\frac{V_{BE}}{V_T}\right)}} = 7.84 \times 10^{-15} \text{ (mA)}$$

5.13 We know the input resistance is $R_{in} = R_1 \parallel R_2 \parallel r_\pi$. Since we want the minimum values of R_1 and R_2 such that $R_{in} > 10 \text{ k}\Omega$, we should pick the maximum value allowable for r_π , which means picking the minimum value allowable for g_m (since $r_\pi \propto 1/g_m$), which is $g_m = 1/260 \text{ S}$.

$$g_m = \frac{1}{260} \text{ S}$$

$$I_C = g_m V_T = 100 \text{ }\mu\text{A}$$

$$V_{BE} = V_T \ln(I_C/I_S) = 760 \text{ mV}$$

$$I_B = \frac{I_C}{\beta} = 1 \text{ }\mu\text{A}$$

$$\frac{V_{CC} - V_{BE}}{R_1} - \frac{V_{BE}}{R_2} = I_B$$

$$R_1 = \frac{V_{CC} - V_{BE}}{I_B + \frac{V_{BE}}{R_2}}$$

$$r_\pi = \frac{\beta}{g_m} = 26 \text{ k}\Omega$$

$$R_{in} = R_1 \parallel R_2 \parallel r_\pi$$

$$= \left(\frac{V_{CC} - V_{BE}}{I_B + \frac{V_{BE}}{R_2}} \right) \parallel R_2 \parallel r_\pi$$

$$> 10 \text{ k}\Omega$$

$$R_2 > \boxed{23.57 \text{ k}\Omega}$$

$$R_1 > \boxed{52.32 \text{ k}\Omega}$$

5.14

$$\begin{aligned}g_m &= \frac{I_C}{V_T} \geq \frac{1}{26} \text{ S} \\r_\pi &= \frac{\beta}{g_m} = 2.6 \text{ k}\Omega \\R_{in} &= R_1 \parallel R_2 \parallel r_\pi \\&\leq r_\pi\end{aligned}$$

According to the above analysis, R_{in} cannot be greater than 2.6 k Ω . This means that the requirement that $R_{in} \geq 10 \text{ k}\Omega$ cannot be met. Qualitatively, the requirement for g_m to be large forces r_π to be small, and since R_{in} is bounded by r_π , it puts an upper bound on R_{in} that, in this case, is below the required 10 k Ω .

$$\begin{aligned}
R_{out} &= R_C = R_0 \\
A_v &= -g_m R_C = -g_m R_0 = -\frac{I_C}{V_T} R_0 = -A_0 \\
I_C &= \frac{A_0}{R_0} V_T \\
r_\pi &= \beta \frac{V_T}{I_C} = \beta \frac{R_0}{A_0} \\
V_{BE} &= V_T \ln(I_C/I_S) = V_T \ln\left(\frac{A_0 V_T}{R_0 I_S}\right) \\
\frac{V_{CC} - V_{BE}}{R_1} - \frac{V_{BE}}{R_2} &= I_B = \frac{I_C}{\beta} \\
R_1 &= \frac{V_{CC} - V_{BE}}{\frac{I_C}{\beta} + \frac{V_{BE}}{R_2}} \\
R_{in} &= R_1 \parallel R_2 \parallel r_\pi \\
&= \left(\frac{V_{CC} - V_T \ln\left(\frac{A_0 V_T}{R_0 I_S}\right)}{\frac{I_C}{\beta} + \frac{V_T}{R_2} \ln\left(\frac{A_0 V_T}{R_0 I_S}\right)} \right) \parallel R_2 \parallel \beta \frac{R_0}{A_0}
\end{aligned}$$

In order to maximize R_{in} , we can let $R_2 \rightarrow \infty$. This gives us

$$R_{in,max} = \boxed{\left(\frac{V_{CC} - V_T \ln\left(\frac{A_0 V_T}{R_0 I_S}\right)}{\beta \frac{I_C}{\beta}} \right) \parallel \beta \frac{R_0}{A_0}}$$

5.16 (a)

$$\begin{aligned}
 I_C &= 0.25 \text{ mA} \\
 V_{BE} &= 696 \text{ mV} \\
 \frac{V_{CC} - V_{BE} - I_E R_E}{R_1} - \frac{V_{BE} + I_E R_E}{R_2} &= I_B = \frac{I_C}{\beta} \\
 R_1 &= \frac{V_{CC} - V_{BE} - \frac{1+\beta}{\beta} I_C R_E}{\frac{I_C}{\beta} + \frac{V_{BE} + \frac{1+\beta}{\beta} I_C R_E}{R_2}} \\
 &= \boxed{22.74 \text{ k}\Omega}
 \end{aligned}$$

(b) First, consider a 5 % increase in R_E .

$$\begin{aligned}
 R_E &= 210 \Omega \\
 \frac{V_{CC} - V_{BE} - I_E R_E}{R_1} - \frac{V_{BE} + I_E R_E}{R_2} &= I_B = \frac{I_C}{\beta} \\
 \frac{V_{CC} - V_T \ln(I_C/I_S) - \frac{1+\beta}{\beta} I_C R_E}{R_1} - \frac{V_T \ln(I_C/I_S) + \frac{1+\beta}{\beta} I_C R_E}{R_2} &= I_B = \frac{I_C}{\beta} \\
 I_C &= 243 \mu\text{A} \\
 \frac{I_C - I_{C,nom}}{I_{C,nom}} \times 100 &= \boxed{-2.6 \%}
 \end{aligned}$$

Now, consider a 5 % decrease in R_E .

$$\begin{aligned}
 R_E &= 190 \Omega \\
 I_C &= 257 \mu\text{A} \\
 \frac{I_C - I_{C,nom}}{I_{C,nom}} \times 100 &= \boxed{+2.8 \%}
 \end{aligned}$$

5.17

$$V_{CE} \geq V_{BE} \text{ (in order to guarantee operation in the active mode)}$$

$$V_{CC} - I_C R_C \geq V_T \ln(I_C/I_S)$$

$$I_C \leq 833 \mu\text{A}$$

$$\frac{V_{CC} - V_{BE} - I_E R_E}{30 \text{ k}\Omega} - \frac{V_{BE} + I_E R_E}{R_2} = I_B = \frac{I_C}{\beta}$$

$$R_2 = \frac{V_{BE} + I_E R_E}{\frac{V_{CC} - V_{BE} - I_E R_E}{30 \text{ k}\Omega} - \frac{I_C}{\beta}}$$

$$= \frac{V_T \ln(I_C/I_S) + \frac{1+\beta}{\beta} I_C R_E}{\frac{V_{CC} - V_T \ln(I_C/I_S) - \frac{1+\beta}{\beta} I_C R_E}{30 \text{ k}\Omega} - \frac{I_C}{\beta}}$$

$$R_2 \leq \boxed{20.66 \text{ k}\Omega}$$

5.18 (a) First, note that $V_{BE1} = V_{BE2} = V_{BE}$, but since $I_{S1} = 2I_{S2}$, $I_{C1} = 2I_{C2}$. Also note that $\beta_1 = \beta_2 = \beta = 100$.


$$I_{B1} = \frac{I_{C1}}{\beta} = \frac{V_{CC} - V_{BE} - (I_{E1} + I_{E2})R_E}{R_1} - \frac{V_{BE} + (I_{E1} + I_{E2})R_E}{R_2}$$

$$I_{C1} = \beta \frac{V_{CC} - V_T \ln(I_{C1}/I_{S1}) - \frac{3}{2} \frac{1+\beta}{\beta} I_{C1} R_E}{R_1} - \frac{V_T \ln(I_{C1}/I_{S1}) + \frac{3}{2} \frac{1+\beta}{\beta} I_{C1} R_E}{R_2}$$


$$I_{C1} = \boxed{707 \mu\text{A}}$$

$$I_{C2} = \frac{I_{C1}}{2} = \boxed{354 \mu\text{A}}$$

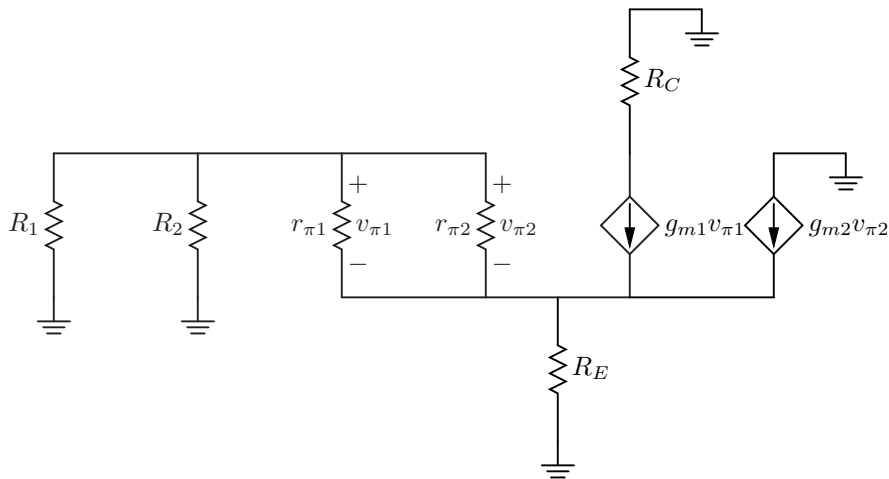(b) The small-signal model is shown below.



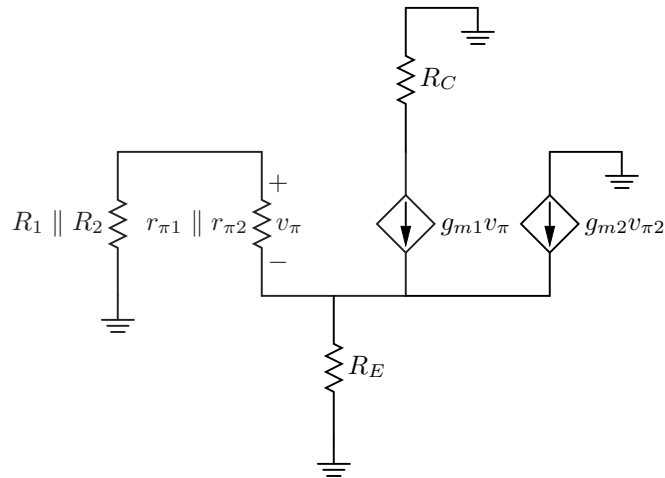We can simplify the small-signal model as follows:



$$g_{m1} = I_{C1}/V_T = \boxed{27.2 \text{ mS}}$$

$$r_{\pi1} = \beta_1/g_{m1} = \boxed{3.677 \text{ k}\Omega}$$

$$g_{m2} = I_{C2}/V_T = \boxed{13.6 \text{ mS}}$$

$$r_{\pi2} = \beta_2/g_{m2} = \boxed{7.355 \text{ k}\Omega}$$

5.19 (a)

$$I_{E1} = I_{E2} \Rightarrow V_{BE1} = V_{BE2}$$

$$\frac{V_{CC} - 2V_{BE1}}{9 \text{ k}\Omega} - \frac{2V_{BE1}}{16 \text{ k}\Omega} = I_{B1} = \frac{I_{C1}}{\beta_1}$$

$$I_{C1} = \beta_1 \frac{V_{CC} - 2V_T \ln(I_{C1}/I_{S1})}{9 \text{ k}\Omega} - \beta_1 \frac{2V_T \ln(I_{C1}/I_{S1})}{16 \text{ k}\Omega}$$


$$I_{C1} = I_{C2} = \boxed{1.588 \text{ mA}}$$

$$V_{BE1} = V_{BE2} = V_T \ln(I_{C1}/I_{S1}) = \boxed{754 \text{ mV}}$$

$$V_{CE2} = V_{BE2} = \boxed{754 \text{ mV}}$$

$$V_{CE1} = V_{CC} - I_{C1}(100 \Omega) - V_{CE2} = \boxed{1.587 \text{ V}}$$

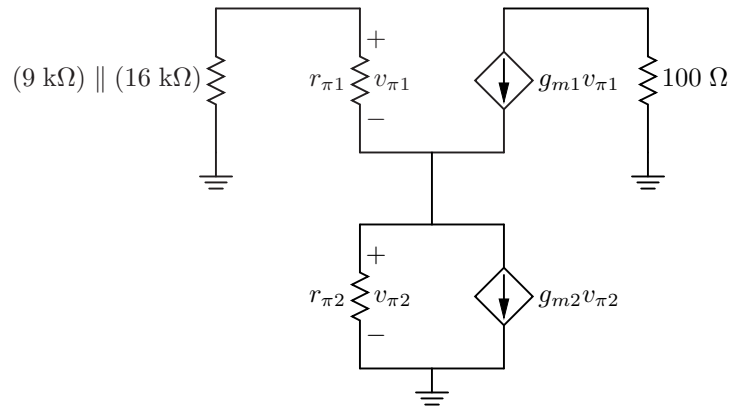
(b) The small-signal model is shown below.



$$g_{m1} = g_{m2} = \frac{I_{C1}}{V_T} = \boxed{61.1 \text{ mS}}$$

$$r_{\pi 1} = r_{\pi 2} = \frac{\beta_1}{g_{m1}} = \boxed{1.637 \text{ k}\Omega}$$

20)

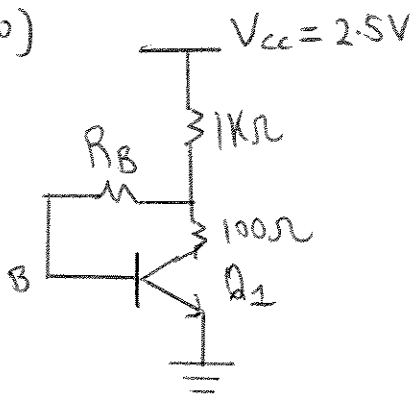

$$I_c = 1 \text{ mA}$$

$$V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.750 \text{ V}$$

$$V_B = 2.5 - (I_E (1 \text{ k}\Omega) + I_B R_B) = 0.750 \text{ V}$$

$$I_E = 1.01 \text{ mA}$$


$$I_B = 0.01 \text{ mA}$$

$$V_B = 2.5 - 1.01 - 0.01 R_B = 0.750$$

$$0.74 = 0.01 R_B$$

$$R_B = 74 \text{ k}\Omega$$

21)

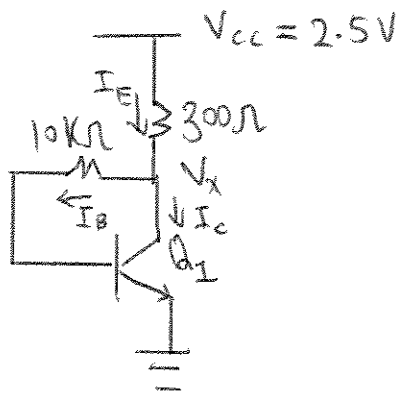

$$V_X = 1.1V$$

$$\beta = 100$$

$$I_S = ?$$

$$I_E = I_B + I_C$$

$$I_E = \frac{2.5 - 1.1}{300\Omega} = 4.67 \text{ mA}$$

$$I_B = \frac{I_C}{\beta}$$

$$I_E = \frac{I_C}{\beta} + I_C = 4.67 \text{ mA}$$

$$I_C = 4.624 \text{ mA}$$

$$I_S = \frac{I_C}{e^{\left(\frac{V_{BE}}{V_T}\right)}}, \quad V_{BE} = 1.1 - \frac{4.624(10K)}{100} = 0.6376V$$

$$I_S = 1.035 \times 10^{-10} \text{ mA}$$

$$I_S = 1.035 \times 10^{-13} \text{ A}$$

5.22

$$\begin{aligned}V_{CC} - I_E(500 \Omega) - I_B(20 \text{ k}\Omega) - I_E(400 \Omega) &= V_{BE} \\V_{CC} - \frac{1+\beta}{\beta}I_C(500 \Omega + 400 \Omega) - \frac{1}{\beta}I_C(20 \text{ k}\Omega) &= V_T \ln(I_C/I_S) \\I_C &= \boxed{1.584 \text{ mA}} \\V_{BE} = V_T \ln(I_C/I_S) &= \boxed{754 \text{ mV}} \\V_{CE} = V_{CC} - I_E(500 \Omega) - I_E(400 \Omega) \\&= V_{CC} - \frac{1+\beta}{\beta}I_C(500 \Omega + 400 \Omega) = \boxed{1.060 \text{ V}}\end{aligned}$$

Q_1 is operating in forward active.

$$V_{BC} \leq 200 \text{ mV}$$

$$V_{CC} - I_E(1 \text{ k}\Omega) - I_B R_B - (V_{CC} - I_E(1 \text{ k}\Omega) - I_C(500 \text{ }\Omega)) \leq 200 \text{ mV}$$

$$I_C(500 \text{ }\Omega) - I_B R_B \leq 200 \text{ mV}$$

$$I_B R_B \geq I_C(500 \text{ }\Omega) - 200 \text{ mV}$$

$$V_{CC} - I_E(1 \text{ k}\Omega) - I_B R_B = V_{BE} = V_T \ln(I_C/I_S)$$


$$V_{CC} - \frac{1+\beta}{\beta} I_C(1 \text{ k}\Omega) - I_C(500 \text{ }\Omega) + 200 \text{ mV} \leq V_T \ln(I_C/I_S)$$

$$I_C \geq 1.29 \text{ mA}$$

$$R_B \geq \frac{I_C(500 \text{ }\Omega) - 200 \text{ mV}}{\frac{I_C}{\beta}}$$

$$\geq \boxed{34.46 \text{ k}\Omega}$$

24). a).

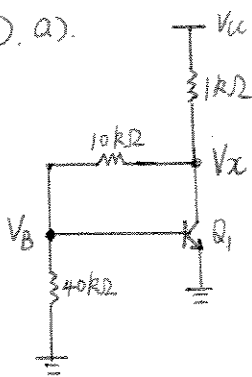

$$I_S = 8 \times 10^{-16} \text{ A}$$

$$\beta = 100$$

$$V_A = \infty$$

$$V_C = 2.5 - \left(\frac{I_C}{\alpha} + \frac{V_B}{40k} \right) \cdot 1k$$

$$V_C = \left(\frac{V_B}{40k} + 2I_B \right) 10k + V_B = \left(\frac{V_B}{40k} + \frac{I_C}{\beta} \right) 10k + V_B$$

$$\text{Equating } V_C \Rightarrow 2.5 - \left(V_B + \frac{V_B \cdot 1k}{40k} + \frac{V_B \cdot 10k}{40k} \right) = \frac{I_C}{\alpha} \cdot 1k + \frac{I_C}{\beta} \cdot 10k.$$

$$\Rightarrow I_C = \frac{2.5 - 1.275V_B}{\frac{1k}{\alpha} + \frac{10k}{\beta}}$$

Guess $V_B = 0.8$

$$I_C = \frac{1.48}{\frac{1k}{0.99} + \frac{10k}{100}} = 1.33 \text{ mA}$$

Then

$$V_B = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.732, \text{ not } 0.8.$$

Reiterate

$$I_C = \frac{1.5667}{1.11} = 1.4113 \text{ mA}$$

$$V_B = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.733$$

So V_B converges to 0.73V


$$I_C = 1.41 \text{ mA}$$

$$I_B = 14.1 \text{ } \mu\text{A}$$

$$V_{CE} = 2.5 \text{ V} - \left(\frac{1.41}{0.99} + \frac{0.73}{40} \right) \times 1 \text{ V} = 1.06 \text{ V}.$$

$$V_{BE} = 0.73 \text{ V}$$

24 b) Small Signal

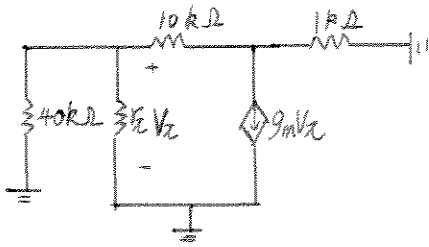


$$g_m = \frac{I_C}{V_T} = 0.054 \text{ S}$$

$$r_z = \frac{\beta}{g_m} = 1844 \Omega$$

5.25 (a)

$$\begin{aligned}
 I_{C1} &= 1 \text{ mA} \\
 V_{CC} - (I_{E1} + I_{E2})(500 \Omega) &= V_T \ln(I_{C2}/I_{S2}) \\
 V_{CC} - \left(\frac{1+\beta}{\beta} I_{C1} + \frac{1+\beta}{\beta} I_{C2} \right) (500 \Omega) &= V_T \ln(I_{C2}/I_{S2}) \\
 I_{C2} &= 2.42 \text{ mA} \\
 V_B - (I_{E1} + I_{E2})(500 \Omega) &= V_T \ln(I_{C1}/I_{S1}) \\
 V_B - \left(\frac{1+\beta}{\beta} I_{C1} + \frac{1+\beta}{\beta} I_{C2} \right) (500 \Omega) &= V_T \ln(I_{C1}/I_{S1}) \\
 V_B &= \boxed{2.68 \text{ V}}
 \end{aligned}$$

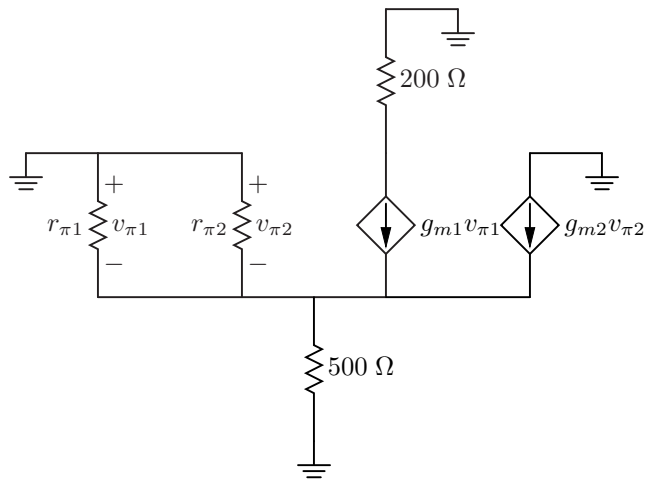(b) The small-signal model is shown below.



$$\begin{aligned}
 g_{m1} &= I_{C1}/V_T = \boxed{38.5 \text{ mS}} \\
 r_{\pi1} &= \beta_1/g_{m1} = \boxed{2.6 \text{ k}\Omega} \\
 g_{m2} &= I_{C2}/V_T = \boxed{93.1 \text{ mS}} \\
 r_{\pi2} &= \beta_2/g_{m2} = \boxed{1.074 \text{ k}\Omega}
 \end{aligned}$$

5.26 (a)

$$\begin{aligned}
 V_{CC} - I_B(60 \text{ k}\Omega) &= V_{EB} \\
 V_{CC} - \frac{1}{\beta_{pnp}} I_C(60 \text{ k}\Omega) &= V_T \ln(I_C/I_S) \\
 I_C &= \boxed{1.474 \text{ mA}} \\
 V_{EB} &= V_T \ln(I_C/I_S) = \boxed{731 \text{ mV}} \\
 V_{EC} &= V_{CC} - I_C(200 \Omega) = \boxed{2.205 \text{ V}}
 \end{aligned}$$

Q_1 is operating in forward active.


(b)

$$\begin{aligned}
 V_{CC} - V_{BE1} - I_{B2}(80 \text{ k}\Omega) &= V_{EB2} \\
 V_{CC} - V_T \ln(I_{C1}/I_S) - I_{B2}(80 \text{ k}\Omega) &= V_T \ln(I_{C2}/I_S) \\
 I_{C1} &= \frac{\beta_{npn}}{1 + \beta_{npn}} I_{E1} \\
 &= \frac{\beta_{npn}}{1 + \beta_{npn}} I_{E2} \\
 &= \frac{\beta_{npn}}{1 + \beta_{npn}} \cdot \frac{1 + \beta_{pnp}}{\beta_{pnp}} I_{C2} \\
 V_{CC} - V_T \ln\left(\frac{\beta_{npn}}{1 + \beta_{npn}} \cdot \frac{1 + \beta_{pnp}}{\beta_{pnp}} \cdot \frac{I_{C2}}{I_S}\right) - \frac{1}{\beta_{pnp}} I_{C2}(80 \text{ k}\Omega) &= V_T \ln(I_{C2}/I_S) \\
 I_{C2} &= \boxed{674 \text{ }\mu\text{A}} \\
 V_{BE2} &= V_T \ln(I_{C2}/I_S) = \boxed{711 \text{ mV}} \\
 I_{C1} &= \boxed{680 \text{ }\mu\text{A}} \\
 V_{BE1} &= V_T \ln(I_{C1}/I_S) = \boxed{711 \text{ mV}} \\
 V_{CE1} &= V_{BE1} = \boxed{711 \text{ mV}} \\
 V_{CE2} &= V_{CC} - V_{CE1} - I_{C2}(300 \Omega) \\
 &= \boxed{1.585 \text{ V}}
 \end{aligned}$$

Q_1 is operating on the edge of saturation. Q_2 is operating in forward active.

5.27 See Problem 26 for the derivation of I_C for each part of this problem.

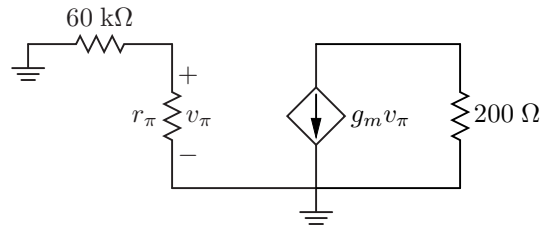(a) The small-signal model is shown below.




$$I_C = 1.474 \text{ mA}$$

$$g_m = \frac{I_C}{V_T} = \boxed{56.7 \text{ mS}}$$

$$r_\pi = \frac{\beta}{g_m} = \boxed{1.764 \text{ k}\Omega}$$

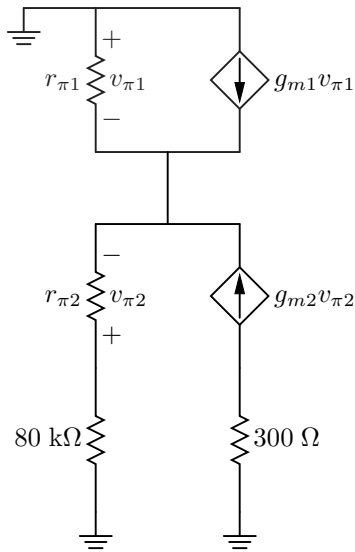(b) The small-signal model is shown below.



$$I_{C1} = 680 \text{ }\mu\text{A}$$

$$g_{m1} = \frac{I_{C1}}{V_T} = \boxed{26.2 \text{ mS}}$$


$$r_{\pi 1} = \frac{\beta_{npn}}{g_{m1}} = \boxed{3.824 \text{ k}\Omega}$$

$$I_{C2} = 674 \text{ }\mu\text{A}$$

$$g_{m2} = \frac{I_{C2}}{V_T} = \boxed{25.9 \text{ mS}}$$

$$r_{\pi 2} = \frac{\beta_{pnp}}{g_{m2}} = \boxed{1.929 \text{ k}\Omega}$$

28)

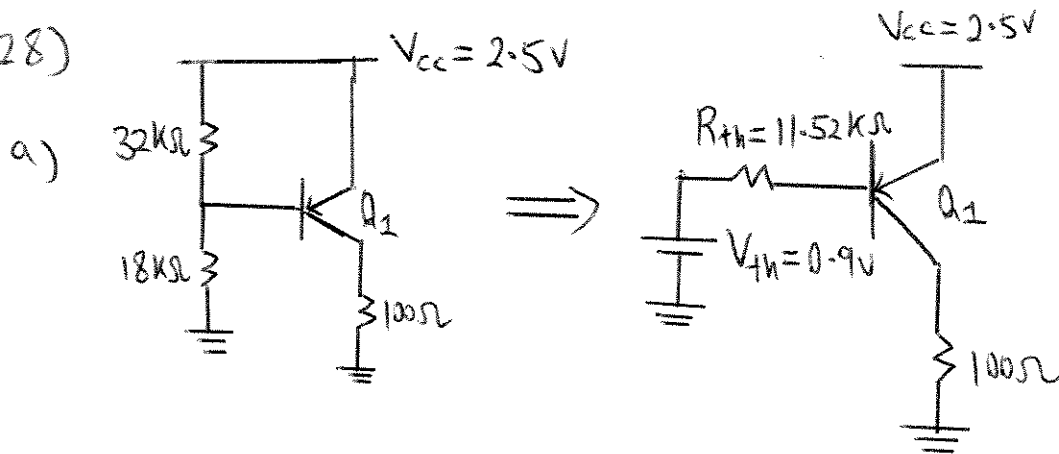

$$I_c = \beta_{npn} \left(\frac{2.5 - |V_{BE}| - V_{th}}{R_{th}} \right)$$

Guess $|V_{BE}| = 0.7 \text{ V}$, $I_c = 3.91 \text{ mA}$

$$|V_{BE}| = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.757 \text{ V}$$

Reiterate, $|V_{BE}| = 0.757 \text{ V}$, $I_c = 3.66 \text{ mA}$

$$|V_{BE}| = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.755 \text{ V}$$

Reiterate, $|V_{BE}| = 0.755 \text{ V}$, $I_c = 3.67 \text{ mA}$

$$|V_{BE}| = V_T \ln \left(\frac{I_c}{I_s} \right) = 0.755 \text{ V, Converged!!}$$

$$V_c = (3.67 \text{ mA})(0.1 \text{ k}\Omega) = 0.367 \text{ V}, \quad V_B = 2.5 - 0.755 = 1.745 \text{ V}$$


Q_1 in forward active.

Bias point:

$$I_c = 3.67 \text{ mA} \quad |V_{BE}| = 0.755$$

$$I_B = 73.4 \text{ }\mu\text{A} \quad |V_{CE}| = 2.5 - 0.367 = 2.133 \text{ V}$$

28)
b)

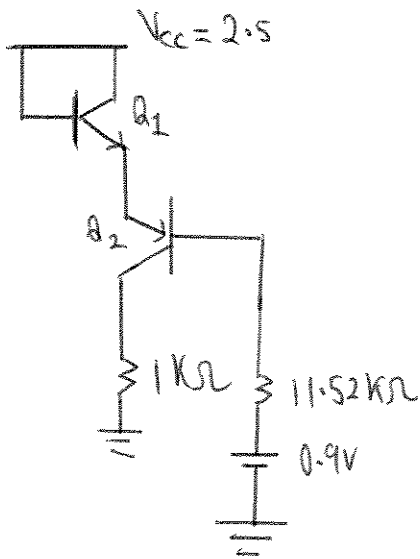

$$I_{c2} = \frac{(2.5 - (V_{BE1} + V_{BE2}) - 0.9)}{11.52 \text{ k}} \cdot 50$$

$$I_{c1} = I_{c2} (1.00997)$$

(From β relation)

$$V_{BE1} = V_T \ln\left(\frac{I_{c1}}{I_S}\right)$$

$$|V_{BE2}| = V_T \ln\left(\frac{I_{c2}}{I_S}\right)$$

Guess, $V_{BE1} = V_{BE2} = 0.7 \text{ V}$

$$I_{c2} = 0.868 \text{ mA}, \quad I_{c1} = 0.877 \text{ mA}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{c1}}{I_S}\right) = 0.718 \text{ V}, \quad |V_{BE2}| = V_T \ln\left(\frac{I_{c2}}{I_S}\right) = 0.717 \text{ V}$$

Reiterate, $V_{BE1} = 0.718 \text{ V}, \quad |V_{BE2}| = 0.717 \text{ V}$

$$I_{c2} = 0.716 \text{ mA}, \quad I_{c1} = 0.723 \text{ mA}$$

$$V_{BE1} = V_T \ln\left(\frac{I_{c1}}{I_S}\right) = 0.713 \text{ V}, \quad |V_{BE2}| = V_T \ln\left(\frac{I_{c2}}{I_S}\right) = 0.712 \text{ V}$$

Reiterate, $V_{BE1} = 0.713 \text{ V}, \quad |V_{BE2}| = 0.712 \text{ V}$

$$I_{c2} = 0.760 \text{ mA}, \quad I_{c1} = 0.767 \text{ mA}$$

$$V_{BE1} = 0.714 \text{ V}, \quad |V_{BE2}| = 0.714 \text{ V}$$

28)

b)

$$\text{Reiterate, } V_{BE_1} = 0.714 \text{ V, } |V_{BE_2}| = 0.714 \text{ V}$$

$$I_{C_2} = 0.747 \text{ mA, } I_{C_1} = 0.754 \text{ mA}$$

$$V_{BE_1} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.714 \text{ V,}$$

$$|V_{BE_2}| = 0.714 \text{ V}$$

$$V_{B_2} = \frac{(0.747 \text{ mA})(11.52 \text{ k}\Omega) + 0.9}{50} = 1.07 \text{ V}$$

$$V_{C_2} = (0.747 \text{ mA})(1 \text{ k}\Omega) = 0.747 \text{ V}$$

Q_2 is in forward-active region. Q_1 is always in forward-active region.

Bias point:

$$V_{BE_1} = 0.714 \text{ V}$$

$$I_{C_1} = 0.754 \text{ mA}$$

$$I_{B_1} = 7.54 \mu\text{A}$$

$$V_{CE_1} = 0.714 \text{ V}$$

$$|V_{BE_2}| = 0.714 \text{ V}$$


$$I_{C_2} = 0.747 \text{ mA}$$

$$I_{B_2} = 14.94 \mu\text{A}$$


$$|V_{CE_2}| = 2.5 - 0.714 - 0.747 = 1.039 \text{ V}$$

29)

a)

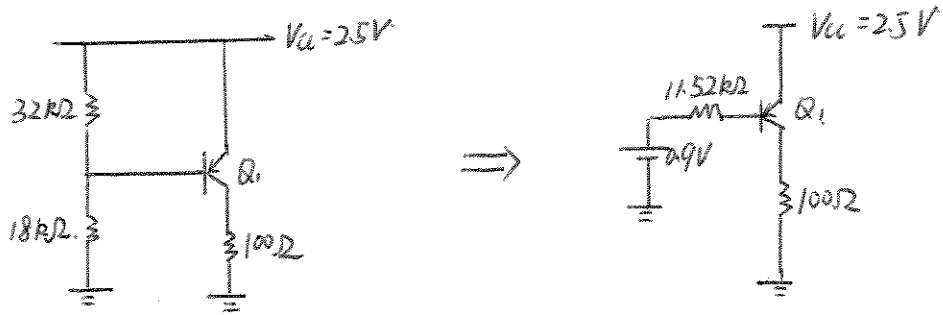


Small Signal:

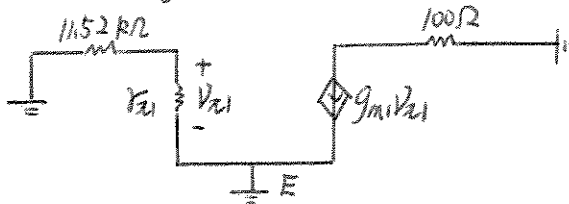

$$g_{m1} = \frac{3.67 \text{ mA}}{26 \text{ mV}} = 0.141 \text{ S}$$

$$r_{e1} = \frac{50}{0.141} \Omega = 354.2 \Omega$$

b)

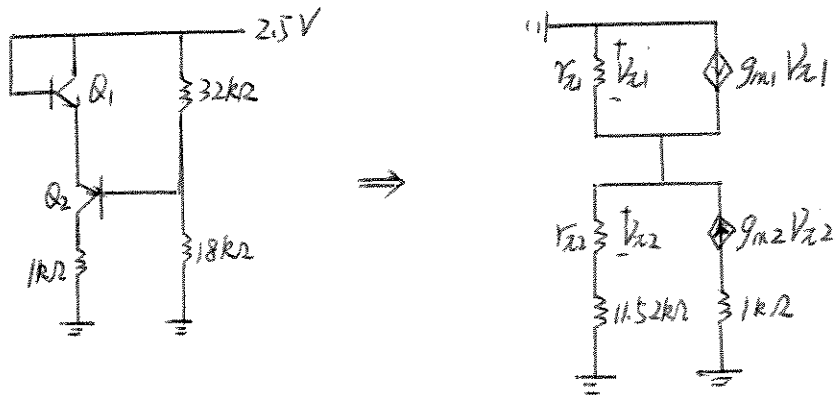

$$g_{m1} = 0.029 \text{ S}$$

$$r_{e1} = 3448.3 \Omega$$

$$g_{m2} = 0.0287 \text{ S}$$

$$r_{e2} = 17403 \Omega$$

$$V_{CC} - I_C(1 \text{ k}\Omega) = V_{EC} = V_{EB} \text{ (in order for } Q_1 \text{ to operate at the edge of saturation)}$$

$$= V_T \ln(I_C/I_S)$$

$$I_C = 1.761 \text{ mA}$$

$$V_{EB} = 739 \text{ mV}$$

$$\frac{V_{CC} - V_{EB}}{R_B} - \frac{V_{EB}}{5 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$R_B = 9.623 \text{ k}\Omega$$

First, let's consider when R_B is 5 % larger than its nominal value.

$$R_B = 10.104 \text{ k}\Omega$$

$$\frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} - \frac{V_T \ln(I_C/I_S)}{5 \text{ k}\Omega} = \frac{I_C}{\beta}$$

$$I_C = 1.411 \text{ mA}$$

$$V_{EB} = 733 \text{ mV}$$

$$V_{EC} = V_{CC} - I_C(1 \text{ k}\Omega) = 1.089 \text{ V}$$

$$V_{CB} = \boxed{-355 \text{ mV}} \text{ (the collector-base junction is reverse biased)}$$

Now, let's consider when R_B is 5 % smaller than its nominal value.

$$R_B = 9.142 \text{ k}\Omega$$

$$\frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} - \frac{V_T \ln(I_C/I_S)}{5 \text{ k}\Omega} = \frac{I_C}{\beta}$$

$$I_C = 2.160 \text{ mA}$$

$$V_{EB} = 744 \text{ mV}$$

$$V_{EC} = V_{CC} - I_C(1 \text{ k}\Omega) = 340 \text{ mV}$$

$$V_{CB} = \boxed{405 \text{ mV}} \text{ (the collector-base junction is forward biased)}$$

5.31

$$\frac{V_{BC} + I_C(5 \text{ k}\Omega)}{10 \text{ k}\Omega} - \frac{V_{CC} - V_{BC} - I_C(5 \text{ k}\Omega)}{10 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$V_{BC} = 300 \text{ mV}$$

$$I_C = 194 \text{ }\mu\text{A}$$

$$V_{EB} = V_T \ln(I_C/I_S) = 682 \text{ mV}$$

$$V_{CC} - I_E R_E - I_C(5 \text{ k}\Omega) = V_{EC} = V_{EB} + 300 \text{ mV}$$

$$V_{CC} - \frac{1+\beta}{\beta} I_C R_E - I_C(5 \text{ k}\Omega) = V_{EB} + 300 \text{ mV}$$

$$R_E = \boxed{2.776 \text{ k}\Omega}$$

Let's look at what happens when R_E is halved.

$$R_E = 1.388 \text{ k}\Omega$$

$$\frac{V_{CC} - I_E R_E - V_{EB}}{10 \text{ k}\Omega} - \frac{V_{CC} - (V_{CC} - I_E R_E - V_{EB})}{10 \text{ k}\Omega} = I_B = \frac{I_C}{\beta}$$

$$\beta \frac{V_{CC} - \frac{1+\beta}{\beta} I_C R_E - V_T \ln(I_C/I_S)}{10 \text{ k}\Omega} - \beta \frac{V_{CC} - \left(V_{CC} - \frac{1+\beta}{\beta} I_C R_E - V_T \ln(I_C/I_S) \right)}{10 \text{ k}\Omega} = I_C$$

$$I_C = 364 \text{ }\mu\text{A}$$

$$V_{EB} = 698 \text{ }\mu\text{V}$$

$$V_{EC} = 164 \text{ }\mu\text{V}$$

Thus, when R_E is halved, Q_1 operates in deep saturation.

5.32

$$V_{CC} - I_B(20 \text{ k}\Omega) - I_E(1.6 \text{ k}\Omega) = V_{BE} = V_T \ln(I_C/I_S)$$


$$V_{CC} - \frac{I_C}{\beta}(20 \text{ k}\Omega) - \frac{1+\beta}{\beta}I_C(1.6 \text{ k}\Omega) = V_{BE} = V_T \ln(I_C/I_S)$$

$$I_S = \frac{I_C}{e^{[V_{CC} - \frac{I_C}{\beta}(20 \text{ k}\Omega) - \frac{1+\beta}{\beta}I_C(1.6 \text{ k}\Omega)]/V_T}}$$

$$I_C = 1 \text{ mA}$$

$$I_S = \boxed{3 \times 10^{-14} \text{ A}}$$

33)

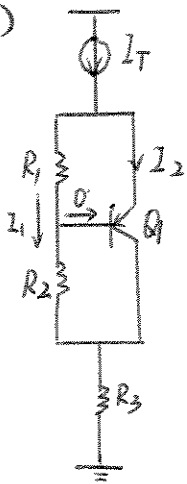

If Base current is neglected, $I_C = I_E$


$$I_1 = \frac{V_E - V_C}{R_1 + R_2}$$

$$|V_{BE}| = I_1 R_1 = \frac{V_E - V_C}{R_1 + R_2} R_1 = \frac{|V_{CE}|}{R_1 + R_2} R_1$$

$$\text{So } \frac{|V_{CE}|}{|V_{BE}|} = \frac{R_1 + R_2}{R_1}$$

Let $A = \frac{R_1 + R_2}{R_1}$, $|V_{CE}| = A |V_{BE}|$, thus $|V_{BE}|$ is multiplied.

34)

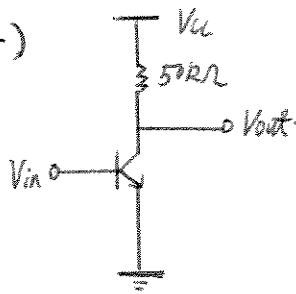

$$A_V = g_m R_C = 20$$


$$\frac{I_C R_C}{V_T} = 20 \Rightarrow I_C = \frac{20 V_T}{R_C}$$

$$I_C = 0.0104 \text{ mA}$$

$$V_{CC} - (50 \text{ k}\Omega) (0.0104 \text{ mA}) = V_{BE}$$

$$\Rightarrow V_{CC} - 50 \times 0.0104 \text{ V} = 0.8 \text{ V}$$

$$\Rightarrow V_{CC} = 1.32 \text{ V}$$

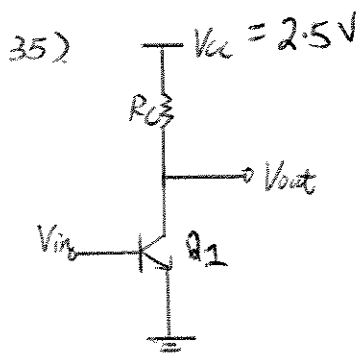

$$V_A = 10V, r_o = \frac{V_A}{I_C}, g_m = \frac{I_C}{V_T}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = g_m (R_C // r_o) = g_m \left(\frac{R_C r_o}{R_C + r_o} \right) = \frac{R_C V_A}{V_T \left(R_C + \frac{V_A}{I_C} \right)}$$

As the equation above shows, a large gain means a large I_C . However, a large I_C will drive Q_1 into saturation. So a tradeoff must be made. The maximum limit for I_C is when it drives Q_1 into the edge of saturation, namely, $V_{BE} = V_{CE}$.


$$V_{CE} = V_{CC} - I_C (1K)$$

$$V_{BE} = 0.8V, V_{CC} = 2.5V$$

$$0.8 = 2.5 - I_C 1K$$

$$I_C = 1.7mA$$

36)

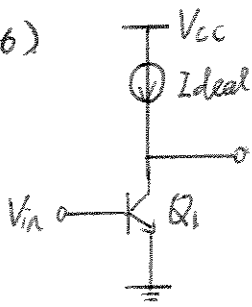


$$A_v = 50$$

$$R_{out} = R_o = 10k\Omega$$

$$A_v = g_m R_{out} = \frac{I_c}{V_T} R_{out} = 50$$

$$I_c = 50 \left(\frac{V_T}{R_{out}} \right) = 0.13mA$$

37).

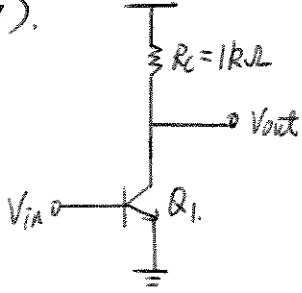

$$I_c = I_s \exp\left(\frac{V_{BE}}{2V_T}\right)$$

$$g_m = \frac{\partial I_c}{\partial V_{BE}} = \frac{I_c}{2V_T}$$

$$R_{out} = R_c$$

$$\left|\frac{V_{out}}{V_{in}}\right| = g_m R_{out} = \frac{I_c R_c}{2V_T} = \frac{(1mA)(1k\Omega)}{(2)(0.026V)} = 19.23$$

5.38 (a)

$$A_v = -g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

(b)

$$A_v = -g_{m1} \left(R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$


(c)

$$A_v = -g_{m1} \left(R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

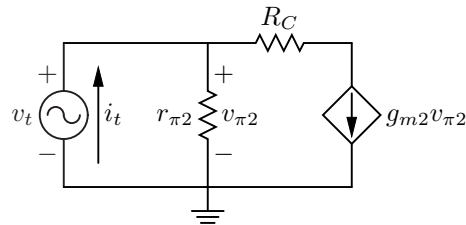(d) Let's determine the equivalent resistance seen looking up from the output by drawing a small-signal model and applying a test source.



$$i_t = \frac{v_{\pi 2}}{r_{\pi 2}} + g_{m2}v_{\pi 2}$$

$$v_{\pi 2} = v_t$$

$$i_t = v_t \left(\frac{1}{r_{\pi 2}} + g_{m2} \right)$$


$$\frac{v_t}{i_t} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

$$A_v = -g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

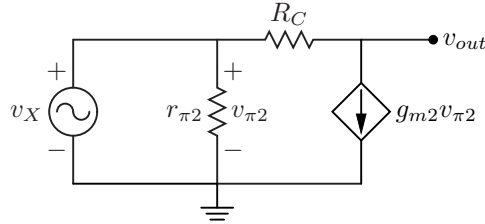- (e) From (d), we know the gain from the input to the collector of Q_1 is $-g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$. If we find the gain from the collector of Q_1 to v_{out} , we can multiply these expressions to find the overall gain. Let's draw the small-signal model to find the gain from the collector of Q_1 to v_{out} . I'll refer to the collector of Q_1 as node X in the following derivation.




$$\begin{aligned} \frac{v_X - v_{out}}{R_C} &= g_{m2}v_{\pi 2} \\ v_{\pi 2} &= v_X \\ \frac{v_X - v_{out}}{R_C} &= g_{m2}v_X \\ v_X \left(\frac{1}{R_C} - g_{m2} \right) &= \frac{v_{out}}{R_C} \\ \frac{v_{out}}{v_X} &= 1 - g_{m2}R_C \end{aligned}$$

Thus, we have

$$A_v = \boxed{-g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right) (1 - g_{m2}R_C)}$$

$$R_{in} = \boxed{r_{\pi 1}}$$

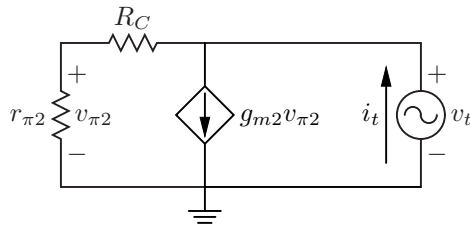To find the output resistance, let's draw the small-signal model and apply a test source at the output. Note that looking into the collector of Q_1 we see infinite resistance, so we can exclude it from the small-signal model.



$$\begin{aligned}
i_t &= g_{m2}v_{\pi2} + \frac{v_{\pi2}}{r_{\pi2}} \\
v_{\pi2} &= \frac{r_{\pi2}}{r_{\pi2} + R_C}v_t \\
i_t &= \left(g_{m2} + \frac{1}{r_{\pi2}}\right) \frac{r_{\pi2}}{r_{\pi2} + R_C}v_t \\
R_{out} &= \frac{v_t}{i_t} \\
&= \boxed{\left(\frac{1}{g_{m2}} \parallel r_{\pi2}\right) \frac{r_{\pi2} + R_C}{r_{\pi2}}}
\end{aligned}$$

5.39 (a)

$$A_v = -g_{m1} \left(r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}$$

(b)

$$A_v = -g_{m1} \left[r_{o1} \parallel \left(R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right) \right]$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = r_{o1} \parallel \left(R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$


(c)

$$A_v = -g_{m1} \left[r_{o1} \parallel \left(R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right) \right]$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = r_{o1} \parallel \left(R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

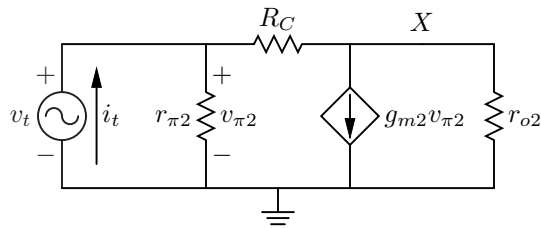(d) Let's determine the equivalent resistance seen looking up from the output by drawing a small-signal model and applying a test source.



$$\begin{aligned}
i_t &= \frac{v_{\pi 2}}{r_{\pi 2}} + \frac{v_t - v_X}{R_C} \\
\frac{v_X - v_t}{R_C} + g_{m2}v_{\pi 2} + \frac{v_X}{r_{o2}} &= 0 \\
v_{\pi 2} &= v_t \\
v_X \left(\frac{1}{R_C} + \frac{1}{r_{o2}} \right) &= v_t \left(\frac{1}{R_C} - g_{m2} \right) \\
v_X &= v_t \left(\frac{1}{R_C} - g_{m2} \right) (r_{o2} \parallel R_C) \\
i_t &= \frac{v_t}{r_{\pi 2}} + \frac{v_t}{R_C} - \frac{1}{R_C} v_t \left(\frac{1}{R_C} - g_{m2} \right) (r_{o2} \parallel R_C) \\
&= v_t \left[\frac{1}{r_{\pi 2}} + \frac{1}{R_C} - \frac{1}{R_C} \left(\frac{1}{R_C} - g_{m2} \right) (r_{o2} \parallel R_C) \right] \\
&= v_t \left[\frac{1}{r_{\pi 2}} + \frac{1}{R_C} + \left(g_{m2} - \frac{1}{R_C} \right) \frac{r_{o2}}{r_{o2} + R_C} \right] \\
\frac{v_t}{i_t} &= r_{\pi 2} \parallel R_C \parallel \left[\frac{r_{o2} + R_C}{r_{o2}} \frac{1}{g_{m2} - \frac{1}{R_C}} \right]
\end{aligned}$$


$$A_v = -g_{m1} \left(r_{o1} \parallel r_{\pi 2} \parallel R_C \parallel \left[\frac{r_{o2} + R_C}{r_{o2}} \frac{1}{g_{m2} - \frac{1}{R_C}} \right] \right)$$

$$R_{in} = r_{\pi 1}$$

$$R_{out} = r_{o1} \parallel r_{\pi 2} \parallel R_C \parallel \left[\frac{r_{o2} + R_C}{r_{o2}} \frac{1}{g_{m2} - \frac{1}{R_C}} \right]$$

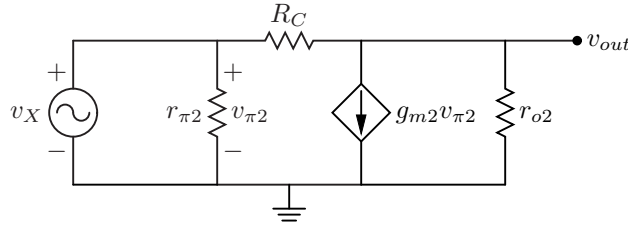(e) From (d), we know the gain from the input to the collector of Q_1 is $-g_{m1} \left(r_{o1} \parallel r_{\pi 2} \parallel R_C \parallel \left[\frac{r_{o2} + R_C}{r_{o2}} \frac{1}{g_{m2} - \frac{1}{R_C}} \right] \right)$.

If we find the gain from the collector of Q_1 to v_{out} , we can multiply these expressions to find the overall gain. Let's draw the small-signal model to find the gain from the collector of Q_1 to v_{out} . I'll refer to the collector of Q_1 as node X in the following derivation.




$$\begin{aligned} \frac{v_{out} - v_X}{R_C} + g_{m2}v_{\pi 2} + \frac{v_{out}}{r_{o2}} &= 0 \\ v_{\pi 2} &= v_X \\ \frac{v_{out} - v_X}{R_C} + g_{m2}v_X + \frac{v_{out}}{r_{o2}} &= 0 \\ v_{out} \left(\frac{1}{R_C} + \frac{1}{r_{o2}} \right) &= v_X \left(\frac{1}{R_C} - g_{m2} \right) \\ \frac{v_{out}}{v_X} &= \left(\frac{1}{R_C} - g_{m2} \right) (R_C \parallel r_{o2}) \end{aligned}$$

Thus, we have

$$A_v = \boxed{-g_{m1} \left(r_{o1} \parallel r_{\pi 2} \parallel R_C \parallel \left[\frac{r_{o2} + R_C}{r_{o2}} \frac{1}{g_{m2} - \frac{1}{R_C}} \right] \right) \left(\frac{1}{R_C} - g_{m2} \right) (R_C \parallel r_{o2})}$$

$$R_{in} = \boxed{r_{\pi 1}}$$

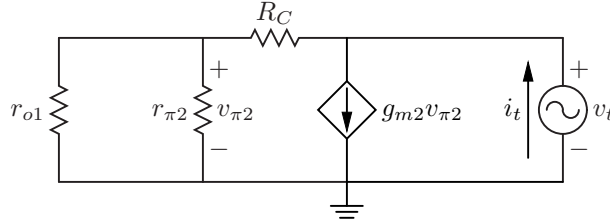To find the output resistance, let's draw the small-signal model and apply a test source at the output. Note that looking into the collector of Q_1 we see r_{o1} , so we replace Q_1 in the small-signal model with this equivalent resistance. Also note that r_{o2} appears from the output to ground, so we can remove it from this analysis and add it in parallel at the end to find R_{out} .



$$\begin{aligned} i_t &= g_{m2}v_{\pi 2} + \frac{v_{\pi 2}}{r_{\pi 2} \parallel r_{o1}} \\ v_{\pi 2} &= \frac{r_{\pi 2} \parallel r_{o1}}{r_{\pi 2} \parallel r_{o1} + R_C} v_t \\ i_t &= \left(g_{m2} + \frac{1}{r_{\pi 2} \parallel r_{o1}} \right) \frac{r_{\pi 2} \parallel r_{o1}}{r_{\pi 2} \parallel r_{o1} + R_C} v_t \\ R_{out} &= r_{o2} \parallel \frac{v_t}{i_t} \\ &= \boxed{r_{o2} \parallel \left[\left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o1} \right) \frac{r_{\pi 2} \parallel r_{o1} + R_C}{r_{\pi 2} \parallel r_{o1}} \right]} \end{aligned}$$

40)

Gain of a degenerated CE stage ($V_A = \infty$)

$$A_v = \frac{-R_c}{\frac{1}{g_m} + R_E} = \frac{-R_c g_m}{1 + R_E g_m}$$

$$\frac{\partial A_v}{\partial I_c} = R_c \left(\frac{g_m R_E}{(1 + R_E g_m)^2} \frac{\partial g_m}{\partial I_c} - \frac{\partial g_m / \partial I_c}{1 + g_m R_E} \right)$$

$$\frac{\partial g_m}{\partial I_c} = \frac{1}{V_T} = \frac{1}{26 \text{ mV}} = 38.46 \left(\frac{1}{\text{V}} \right)$$

a) $g_m R_E = 3$

$$\frac{\partial A_v}{\partial I_c} = R_c (-2.404) \quad , \quad \partial I_c = 0.1 I_c$$

$$\partial A_v = -R_c I_c (0.24)$$

$$\text{Relative change in gain} = \frac{\partial A_v}{A_v} = \frac{-0.24 (R_c I_c)}{\frac{-R_c I_c}{V_T (1 + R_E g_m)}} = 2.5\%$$

40)


$$b) g_m R_E = 7$$

$$\frac{\partial A_v}{\partial I_c} = -R_c \cdot 0.6$$

$$\partial A_v = -R_c I_c (0.06)$$

Relative change in gain
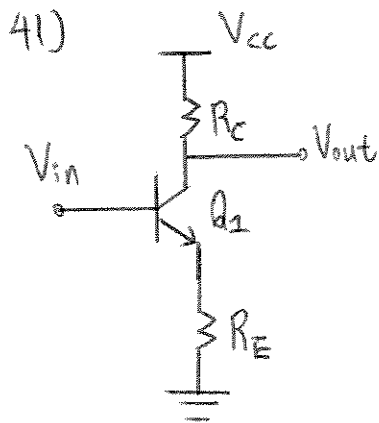
$$\frac{\partial A_v}{A_v} = \frac{-0.06 (R_c I_c)}{\frac{-R_c I_c}{V_T (1 + R_E g_m)}} = 1.25\%$$



$$V_A = \infty$$

$$R_C I_C = 20 V_T$$

$$R_E I_C = 5 V_T$$


$$|A_v| = \frac{R_C}{R_E + \frac{1}{g_m}} = \frac{R_C}{R_E + \frac{V_T}{I_C}} = \frac{R_C I_C}{R_E I_C + V_T}$$

Assume β is large, so $I_C = I_E$.

$$R_C I_C = 20 V_T, \quad R_E I_C = 5 V_T$$

$$|A_v| = \frac{20 V_T}{5 V_T + V_T} = \frac{20 V_T}{6 V_T} = 3.33$$

42)

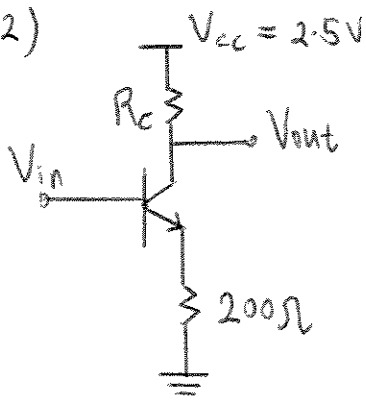

$$|A_v| = \frac{R_c I_c}{R_E I_c + V_T} = 10$$

Edge of Saturation

$$V_{CE} = V_{BE} = 2.5 - I_c (R_c + R_E)$$

$$V_{BE} = 0.8 \text{ V} \Rightarrow I_c R_c = 1.7 - I_c 0.2 \quad (\text{operating point})$$

$$|A_v| = 10 \Rightarrow R_c I_c = 10 (R_E I_c + V_T) \quad (\text{Gain Equation})$$

Equating the two equations above \Rightarrow

$$1.7 - 0.2 I_c = 2 I_c + 0.26 \Rightarrow I_c = 0.655 \text{ mA}$$

Check for $V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_0}\right) = 0.725$, not 0.8, Reiterate

$$I_c R_c = 1.775 - I_c 0.2 \quad (\text{operating point})$$

$$I_c R_c = 2 I_c + 0.26 \quad (\text{Gain equation})$$

Equating the two equations $\Rightarrow I_c = 0.689 \text{ mA}$ Check for $V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_0}\right) = 0.727 \text{ V}$, iterate 1 more time

$$I_c R_c = 1.773 - I_c 0.2 \quad (\text{operating point})$$

$$I_c R_c = 2 I_c + 0.26 \quad (\text{Gain equation})$$

42)

Equating the two equations $\Rightarrow I_c = 0.688 \text{ mA}$

Check for $V_{BE} \Rightarrow V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.727 \text{ V}$, converged

$$I_c = 0.688 \text{ mA}$$

$$R_c = \frac{2I_c + 0.26}{I_c} = \frac{(2 \times 0.688) + 0.26}{0.688}$$

$$R_c = 2.38 \text{ k}\Omega$$

$$R_{in} = r_{\pi} + (1 + \beta) R_E$$

$$R_{in} = \frac{\beta}{g_m} + (101)(0.2) = 24.0 \text{ k}\Omega$$

$$\begin{aligned}
 A_v &= -\frac{R_C}{\frac{1}{g_m} + (200 \Omega)} \\
 &= -\frac{R_C}{\frac{V_T}{I_C} + (200 \Omega)} \\
 &= -100
 \end{aligned}$$



$$R_C = 100 \frac{V_T}{I_C} + 100(200 \Omega)$$

$$I_C R_C - I_E(200 \Omega) = V_{CE} = V_{BE} = V_T \ln(I_C/I_S)$$

$$I_C \left(100 \frac{V_T}{I_C} + 100(200 \Omega) \right) - \frac{1 + \beta}{\beta} I_C(200 \Omega) = V_T \ln(I_C/I_S)$$

We can see that this equation has no solution. For example, if we let $I_C = 0$, we see that according to the left side, we should have $V_{BE} = 2.6$ V, which is clearly an infeasible value. Qualitatively, we know that in order to achieve a large gain, we need a large value for R_C . However, increasing R_C will result in a smaller value of V_{CE} , eventually driving the transistor into saturation. When $A_v = -100$, there is no value of R_C that will provide such a large gain without driving the transistor into saturation.

44) $V_A = \infty$

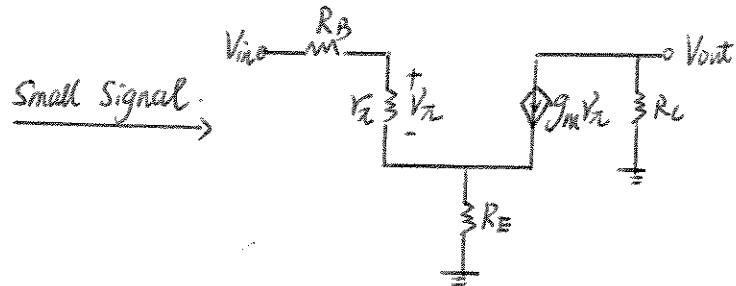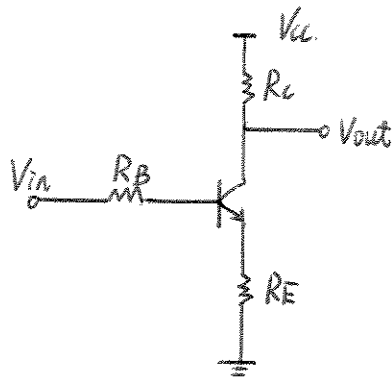


$$V_{out} = -g_m V_{\pi} R_C$$

$$V_{\pi} = \frac{V_{in} r_e}{R_B + r_e + (\beta + 1) R_E}$$


$$V_{out} = \frac{-g_m r_e R_C V_{in}}{R_B + r_e + (\beta + 1) R_E} = \frac{-\beta R_C V_{in}}{R_B + r_e + (\beta + 1) R_E} = \frac{-R_C V_{in}}{\frac{R_B}{\beta} + \frac{1}{g_m} + \frac{\beta + 1}{\beta} R_E}$$

$$\frac{V_{out}}{V_{in}} \approx \frac{-R_C}{\frac{R_B}{\beta + 1} + \frac{1}{g_m} + R_E}$$

45)

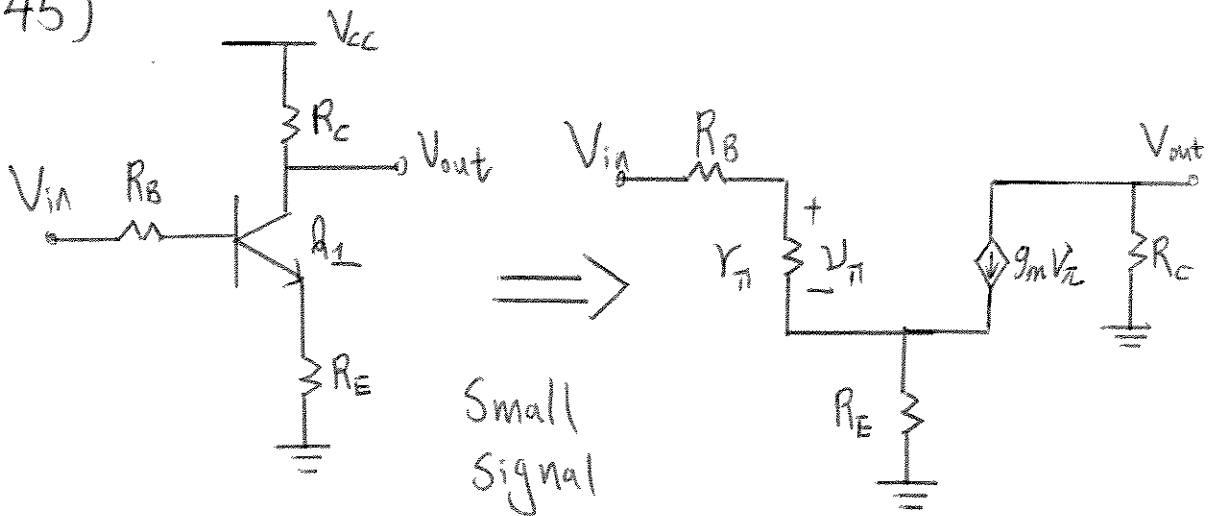

R_{out} Calculation:

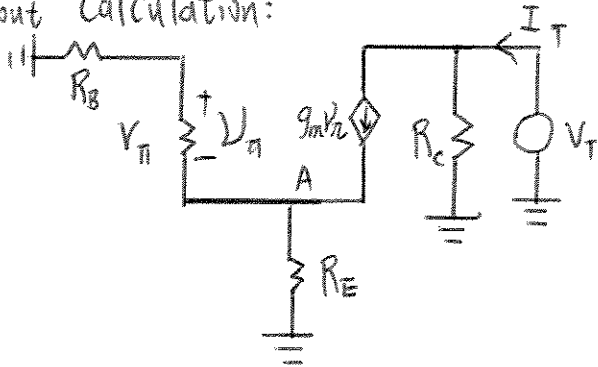

$$V_A = g_m V_{\pi} (R_E \parallel R_B + r_{\pi}) \quad (1)$$

$$V_{\pi} = -\frac{V_A r_{\pi}}{r_{\pi} + R_B} \Rightarrow V_A = -\frac{V_{\pi} (r_{\pi} + R_B)}{r_{\pi}} \quad (2)$$

The only possible solution for 1) and 2) is $V_{\pi} = V_A = 0$,
 since 1) is positive and 2) is negative.

$$V_{\pi} = 0 \Rightarrow g_m V_{\pi} \Rightarrow 0 \Rightarrow \frac{V_i}{I_T} = R_C$$

Therefore, $R_{out} = R_C$

5.46 (a)

$$A_v = -\frac{R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1)R_E$$

$$R_{out} = R_1 + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

(b)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{out} = R_C$$

(c)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{out} = R_C$$

(d)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2} + \frac{R_B}{1 + \beta_1}}$$

$$R_{in} = R_B + r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{out} = R_C$$

(e)

$$A_v = -\frac{R_C}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2} + \frac{R_B}{1 + \beta_1}}$$

$$R_{in} = R_B + r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

$$R_{out} = R_C$$

5.47 (a)

$$A_v = -\frac{R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) R_E$$

$$R_{out} = R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

(b)

$$A_v = -\frac{R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E} \cdot \frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

$$= -\frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) R_E$$

$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2}$$

(c)

$$A_v = -\frac{R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m3}} \parallel r_{\pi 3}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m3}} \parallel r_{\pi 3} \right)$$

$$R_{out} = R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}$$


(d)

$$A_v = -\frac{R_C \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) R_E$$


$$R_{out} = R_C \parallel r_{\pi 2}$$

48).

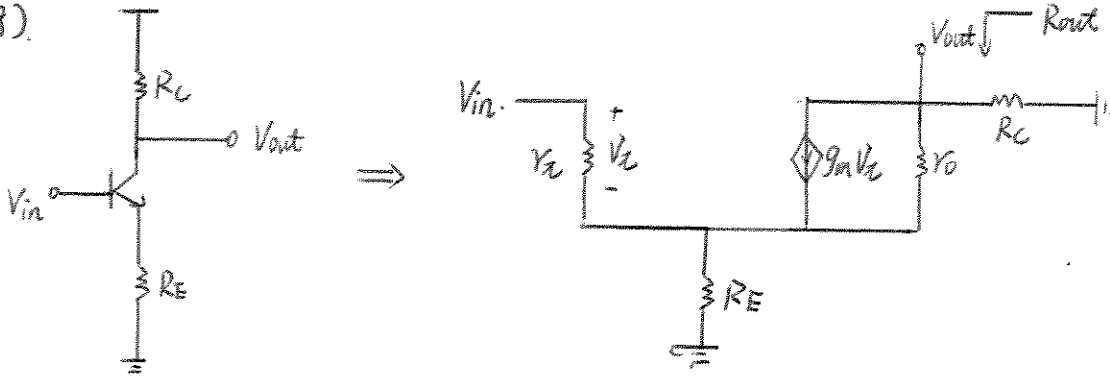

$$R_{out} = R_c \parallel R_{eq}$$

Solve for R_{eq} .

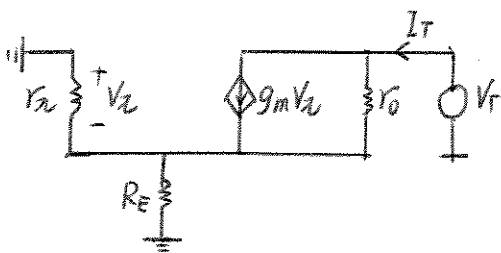

$$I_T = g_m V_{\pi} + \frac{(V_T + V_{\pi})}{r_o}$$

$$V_{\pi} = -I_T (r_{\pi} \parallel R_E)$$

$$I_T = -g_m I_T (r_{\pi} \parallel R_E) + \frac{(V_T - I_T (r_{\pi} \parallel R_E))}{r_o}$$

$$\frac{V_T}{I_T} = r_o \left(1 + \frac{(r_{\pi} \parallel R_E)}{r_o} \right) + g_m (r_{\pi} \parallel R_E)$$


$$\frac{V_T}{I_T} = r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$

$$R_{eq} = r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$

$$R_{out} = R_c \parallel r_o + (1 + g_m r_o) (r_{\pi} \parallel R_E)$$


$$R_{out} \approx R_c \parallel r_o (1 + g_m (r_{\pi} \parallel R_E)) \quad \text{since } g_m r_o \gg 1$$

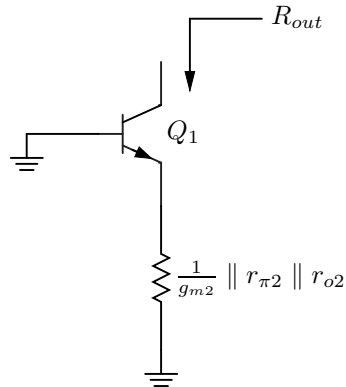- 5.49 (a) Looking into the emitter of Q_2 we see an equivalent resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2}$, so we can draw the following equivalent circuit for finding R_{out} :




$$R_{out} = r_{o1} + (1 + g_{m1}r_{o1}) \left(r_{\pi 1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel r_{o2} \right)$$

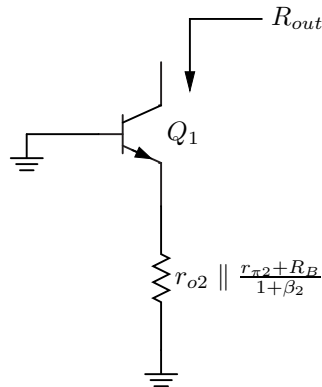- (b) Looking into the emitter of Q_2 we see an equivalent resistance of $r_{o2} \parallel \frac{r_{\pi 2} + R_B}{1 + \beta_2}$ (r_{o2} simply appears in parallel with the resistance seen when $V_A = \infty$), so we can draw the following equivalent circuit for finding R_{out} :




$$R_{out} = r_{o1} + (1 + g_{m1}r_{o1}) \left(r_{\pi 1} \parallel r_{o2} \parallel \frac{r_{\pi 2} + R_B}{1 + \beta_2} \right)$$

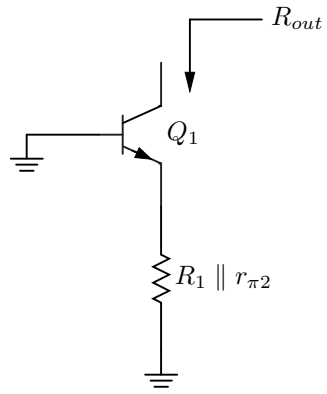- (c) Looking down from the emitter of Q_1 we see an equivalent resistance of $R_1 \parallel r_{\pi 2}$, so we can draw the following equivalent circuit for finding R_{out} :




$$R_{out} = \boxed{r_{o1} + (1 + g_{m1}r_{o1})(r_{\pi 1} \parallel R_1 \parallel r_{\pi 2})}$$

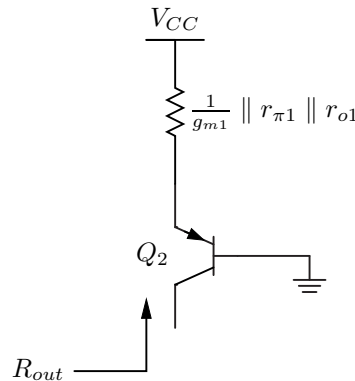- 5.50 (a) Looking into the emitter of Q_1 we see an equivalent resistance of $\frac{1}{g_{m1}} \parallel r_{\pi1} \parallel r_{o1}$, so we can draw the following equivalent circuit for finding R_{out} :



$$R_{out} = \boxed{r_{o2} + (1 + g_{m2}r_{o2}) \left(r_{\pi2} \parallel \frac{1}{g_{m1}} \parallel r_{\pi1} \parallel r_{o1} \right)}$$

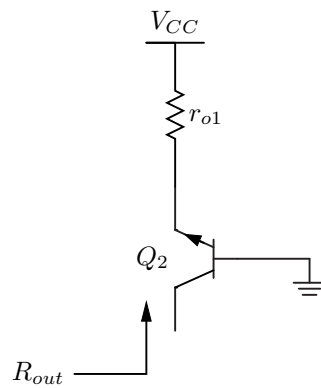- (b) Looking into the emitter of Q_1 we see an equivalent resistance of r_{o1} , so we can draw the following equivalent circuit for finding R_{out} :



$$R_{out} = \boxed{r_{o2} + (1 + g_{m2}r_{o2}) (r_{\pi2} \parallel r_{o1})}$$

Comparing this to the solution to part (a), we can see that the output resistance is larger because instead of a factor of $1/g_{m1}$ dominating the parallel resistors in the expression, $r_{\pi2}$ dominates (assuming $r_{o1} \gg r_{\pi2}$).

$$51). r_2 = \beta V_T / I_C.$$

$$R_{in} = r_2 \parallel R_B = \frac{\frac{\beta V_T}{I_C} R_B}{\frac{\beta V_T}{I_C} + R_B} = \frac{V_T R_B}{V_T + \frac{I_C}{\beta} R_B} = \frac{V_T R_B}{V_T + 2R_B}$$

$$\text{Since } I_B R_B \gg V_T \Rightarrow R_{in} \approx \frac{V_T R_B}{I_B R_B} = \frac{V_T}{I_B} = \frac{V_T}{\frac{I_C}{\beta}} = \frac{\beta V_T}{I_C} \approx r_2$$

$$\text{So } R_{in} = r_2 \parallel R_B \approx r_2.$$

5.52 (a)

$$\begin{aligned}
 V_{CC} - I_B(100 \text{ k}\Omega) - I_E(100 \text{ }\Omega) &= V_{BE} = V_T \ln(I_C/I_S) \\
 V_{CC} - \frac{1}{\beta} I_C(100 \text{ k}\Omega) - \frac{1+\beta}{\beta} I_C(100 \text{ }\Omega) &= V_T \ln(I_C/I_S) \\
 I_C &= 1.6 \text{ mA} \\
 A_v &= -\frac{1 \text{ k}\Omega}{\frac{1}{g_m} + 100 \text{ }\Omega} \\
 g_m &= 61.6 \text{ mS} \\
 A_v &= \boxed{-8.60}
 \end{aligned}$$

(b)

$$\begin{aligned}
 V_{CC} - I_B(50 \text{ k}\Omega) - I_E(2 \text{ k}\Omega) &= V_T \ln(I_C/I_S) \\
 I_C &= 708 \text{ }\mu\text{A} \\
 A_v &= -\frac{1 \text{ k}\Omega}{\frac{1}{g_m} + \frac{(1 \text{ k}\Omega) \parallel (50 \text{ k}\Omega)}{1+\beta}} \\
 g_m &= 27.2 \text{ mS} \\
 A_v &= \boxed{-21.54}
 \end{aligned}$$

(c)

$$\begin{aligned}
 I_B &= \frac{I_C}{\beta} = \frac{V_{CC} - V_{BE} - I_E(2.5 \text{ k}\Omega)}{14 \text{ k}\Omega} - \frac{V_{BE} + I_E(2.5 \text{ k}\Omega)}{11 \text{ k}\Omega} \\
 I_C &= \beta \frac{V_{CC} - V_T \ln(I_C/I_S) - \frac{1+\beta}{\beta} I_C(2.5 \text{ k}\Omega)}{14 \text{ k}\Omega} - \beta \frac{V_T \ln(I_C/I_S) + \frac{1+\beta}{\beta} I_C(2.5 \text{ k}\Omega)}{11 \text{ k}\Omega} \\
 I_C &= 163 \text{ }\mu\text{A} \\
 A_v &= -\frac{10 \text{ k}\Omega}{\frac{1}{g_m} + 500 \text{ }\Omega + \frac{(1 \text{ k}\Omega) \parallel (14 \text{ k}\Omega) \parallel (11 \text{ k}\Omega)}{1+\beta}} \\
 g_m &= 6.29 \text{ mS} \\
 A_v &= \boxed{-14.98}
 \end{aligned}$$

5.53 (a)

$$I_C = \frac{V_{CC} - 1.5 \text{ V}}{R_C}$$

$$= 4 \text{ mA}$$

$$V_{BE} = V_T \ln(I_C/I_S) = 832 \text{ mV}$$

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = 66.7 \text{ } \mu\text{A}$$

$$\beta = \frac{I_C}{I_B} = \boxed{60}$$

(b) Assuming the speaker has an impedance of $8 \text{ } \Omega$, the gain of the amplifier is

$$A_v = -g_m (R_C \parallel 8 \text{ } \Omega)$$

$$= -\frac{I_C}{V_T} (R_C \parallel 8 \text{ } \Omega)$$

$$= \boxed{-1.19}$$

Thus, the circuit provides greater than unity gain.

5.54 (a)

$$A_v = g_m R_C$$

$$g_m = \frac{I_C}{V_T} = 76.9 \text{ mS}$$

$$A_v = \boxed{38.46}$$

$$R_{in} = \frac{1}{g_m} \parallel r_\pi$$


$$r_\pi = \frac{\beta}{g_m} = 1.3 \text{ k}\Omega$$

$$R_{in} = \boxed{12.87 \Omega}$$

$$R_{out} = R_C = \boxed{500 \Omega}$$


- (b) Since $A_v = g_m R_C$ and g_m is fixed for a given value of I_C , R_C should be chosen as large as possible to maximize the gain of the amplifier. V_b should be chosen as small as possible to maximize the headroom of the amplifier (since in order for Q_1 to remain in forward active, we require $V_b < V_{CC} - I_C R_C$).

55) $V_A = \infty$

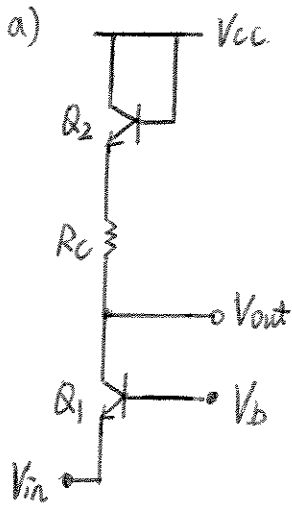


$$|A_v| = \frac{R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}}}$$
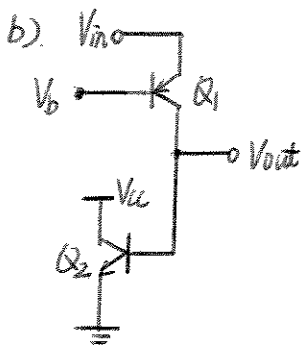
$$= g_{m1} (R_C + \frac{1}{g_{m2}} \parallel r_{\pi 2})$$



$$|A_v| = \frac{r_{\pi 2}}{\frac{1}{g_{m1}}} = g_{m1} r_{\pi 2}$$

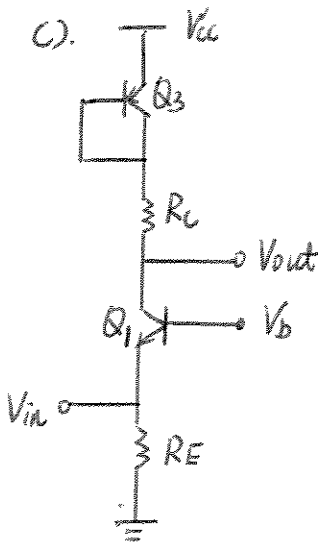


$$|A_v| = \frac{R_C + \frac{1}{g_{m3}} \parallel r_{\pi 3}}{\frac{1}{g_{m1}}}$$

$$= g_{m1} (R_C + \frac{1}{g_{m3}} \parallel r_{\pi 3})$$

55).


d).

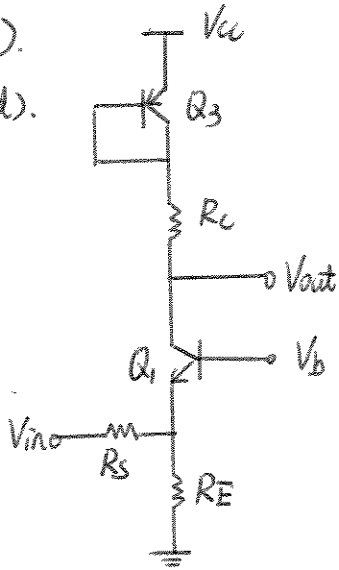

$$|A_v| = \left| \frac{V_{out}}{V_A} \right| \left| \frac{V_A}{V_{in}} \right|$$


$$= \left[g_{m1} (R_C + \frac{1}{g_{m3}} \parallel R_{L3}) \right] \left(\frac{R_E \parallel \frac{1}{g_{m1}}}{R_E \parallel \frac{1}{g_{m1}} + R_S} \right)$$

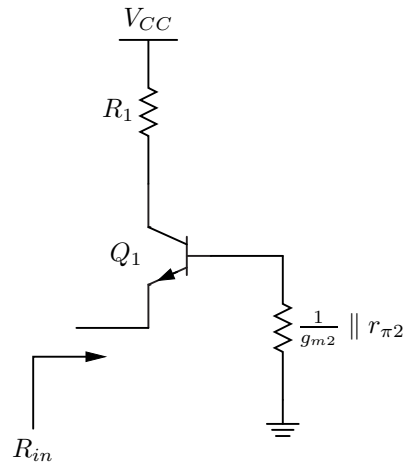- 5.56 (a) Looking into the emitter of Q_2 we see an equivalent resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2}$, so we can draw the following equivalent circuit for finding R_{in} :




$$R_{in} = \frac{r_{\pi 1} + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{1 + \beta_1}$$

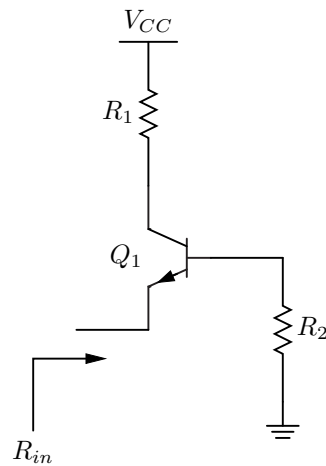- (b) Looking right from the base of Q_1 we see an equivalent resistance of R_2 , so we can draw the following equivalent circuit for finding R_{in} :




$$R_{in} = \frac{r_{\pi 1} + R_2}{1 + \beta_1}$$

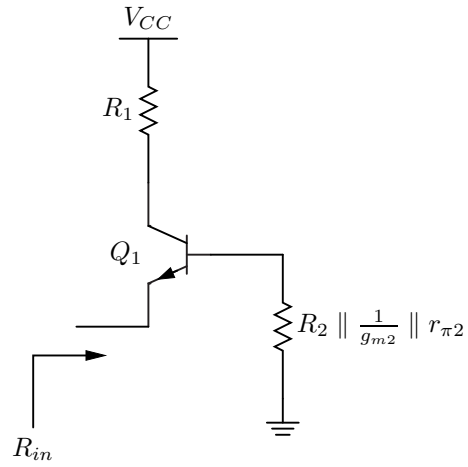- (c) Looking right from the base of Q_1 we see an equivalent resistance of $R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}$, so we can draw the following equivalent circuit for finding R_{in} :




$$R_{in} = \frac{r_{\pi 1} + R_2 \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{1 + \beta_1}$$

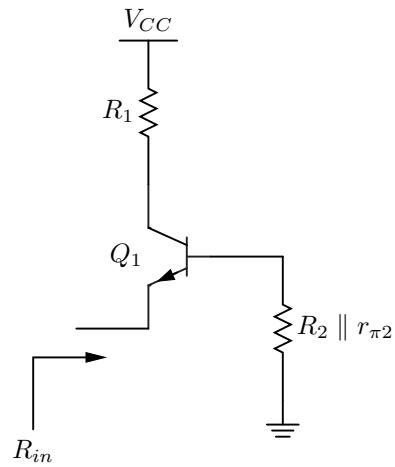- (d) Looking right from the base of Q_1 we see an equivalent resistance of $R_2 \parallel r_{\pi 2}$, so we can draw the following equivalent circuit for finding R_{in} :



$$R_{in} = \frac{r_{\pi 1} + R_2 \parallel r_{\pi 2}}{1 + \beta_1}$$

57)

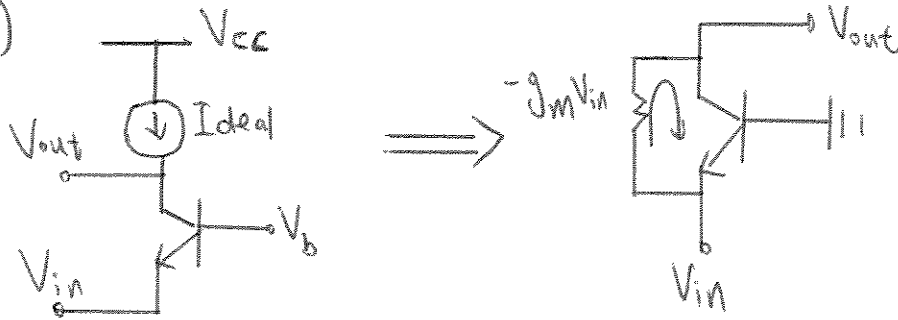

Since an ideal current source is an open circuit, the signal current produced by the transistor has nowhere to go but R_o .

$$\text{So } V_{out} = -(g_m (0 - V_{in})) R_o + V_{in}$$

$$V_{out} = g_m R_o V_{in} + V_{in}$$

$$V_{out} = V_{in} (g_m R_o + 1)$$

$$\frac{V_{out}}{V_{in}} = 1 + g_m R_o$$

5.58 (a)

$$I_B = \frac{I_C}{\beta} = \frac{V_{CC} - V_{BE} - I_E(400 \Omega)}{13 \text{ k}\Omega} - \frac{V_{BE} + I_E(400 \Omega)}{12 \text{ k}\Omega}$$
$$I_C = \beta \frac{V_{CC} - V_T \ln(I_C/I_S) - \frac{1+\beta}{\beta} I_C(400 \Omega)}{13 \text{ k}\Omega} - \beta \frac{V_T \ln(I_C/I_S) + \frac{1+\beta}{\beta} I_C(400 \Omega)}{12 \text{ k}\Omega}$$
$$I_C = \boxed{1.02 \text{ mA}}$$
$$V_{BE} = V_T \ln(I_C/I_S) = \boxed{725 \text{ mV}}$$
$$V_{CE} = V_{CC} - I_C(1 \text{ k}\Omega) - I_E(400 \Omega) = \boxed{1.07 \text{ V}}$$

Q_1 is operating in forward active.


(b)

$$A_v = g_m(1 \text{ k}\Omega)$$

$$g_m = 39.2 \text{ mS}$$

$$A_v = \boxed{39.2}$$

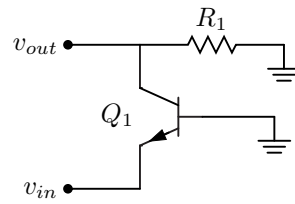5.61 For small-signal analysis, we can draw the following equivalent circuit.



$$A_v = \boxed{g_m R_1}$$
$$R_{in} = \boxed{\frac{1}{g_m} \parallel r_\pi}$$
$$R_{out} = \boxed{R_1}$$

59)

$$C_B = 0$$

a) Since C_B was not considered during DC analysis, it has no effect on operating point analysis. So it is still the same as 58).


$$V_{BE} = 0.725 \text{ V}$$

$$I_C = 1.0163 \text{ mA}$$

$$I_B = 10.163 \mu\text{A}$$

$$V_{CE} = 1.07 \text{ V}$$

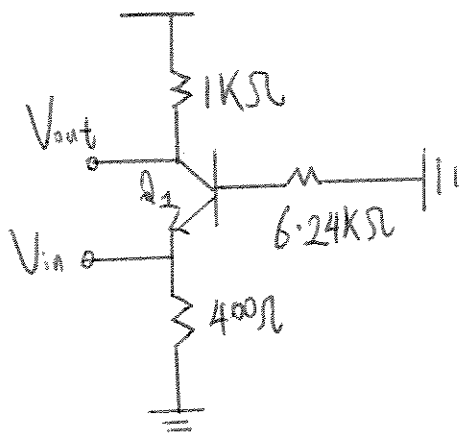b) Since capacitor is frequency dependent, the circuit's AC analysis will be different.




$$|A_v| = \frac{1\text{k}}{\frac{1}{g_m} + \frac{6.24\text{k}\Omega}{\beta + 1}} = 11.4$$

$$R_{in} = 400\Omega \parallel \left(\frac{1}{g_m} + \frac{6.24\text{k}\Omega}{\beta + 1} \right)$$

$$R_{in} = 71.7\Omega$$

$$R_{out} = 1\text{k}\Omega$$

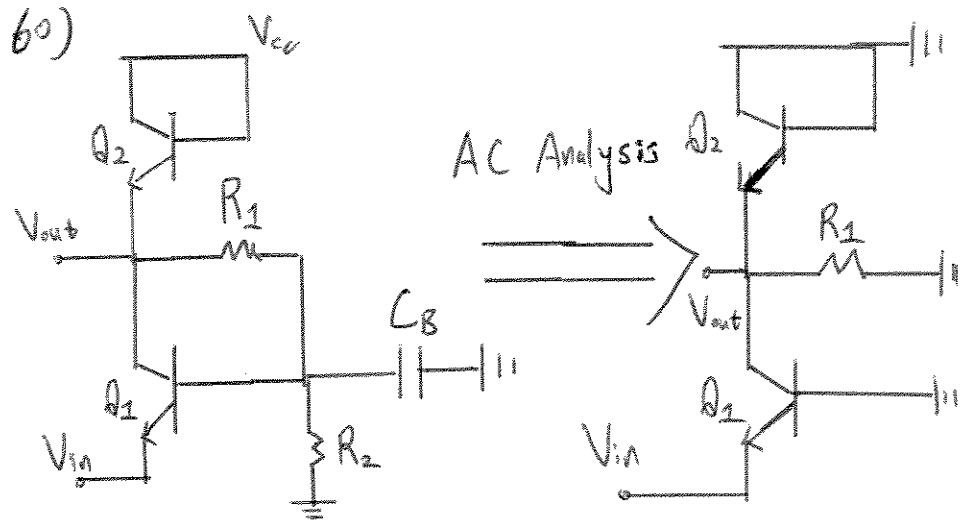Note: $6.24\text{k}\Omega$ is R_{THEV}
of $13\text{k}\Omega$ and $12\text{k}\Omega$
combination.




$$R_{out} = \frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_1 \approx \frac{1}{g_{m2}} \parallel R_1$$

$$A_v = \left| \frac{V_{out}}{V_{in}} \right| = g_{m1} \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \parallel R_1 \right) \approx g_{m1} \left(\frac{1}{g_{m2}} \parallel R_1 \right)$$


$$R_{in} = \frac{1}{g_{m1}} \parallel r_{\pi 1} \approx \frac{1}{g_{m1}}$$

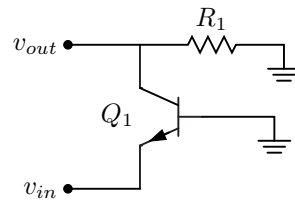5.61 For small-signal analysis, we can draw the following equivalent circuit.



$$A_v = \boxed{g_m R_1}$$
$$R_{in} = \boxed{\frac{1}{g_m} \parallel r_\pi}$$
$$R_{out} = \boxed{R_1}$$

62)

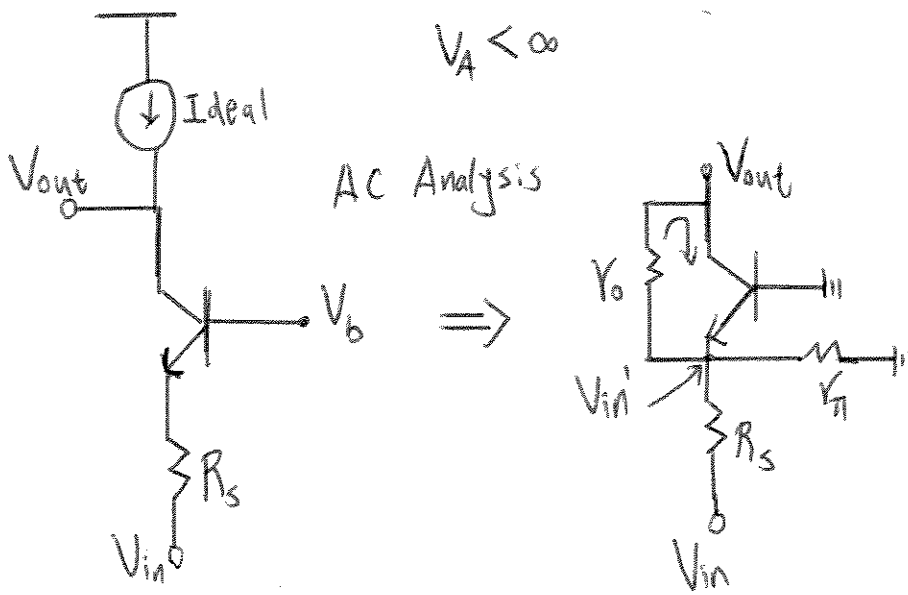

$$A_v = \frac{V_{out}}{V_{in}} = \left(\frac{V_{in}'}{V_{in}} \right) \left(\frac{V_{out}}{V_{in}'} \right), \quad \left(\frac{V_{in}'}{V_{in}} \right) = \frac{r_{\pi}}{r_{\pi} + R_s}$$

Since V_{out} is float, so looking at emitter and r_o , we will see an infinite impedance.

$$\frac{V_{out}}{V_{in}'} \Rightarrow -g_m (-V_{in}') r_o + V_{in}' = V_{out} \Rightarrow \frac{V_{out}}{V_{in}'} = (g_m r_o + 1)$$

$$A_v = (g_m r_o + 1) \left(\frac{r_{\pi}}{r_{\pi} + R_s} \right)$$


5.63 Since $I_{S1} = 2I_{S2}$ and they're biased identically, we know that $I_{C1} = 2I_{C2}$, which means $g_{m1} = 2g_{m2}$.

$$\frac{v_{out1}}{v_{in}} = g_{m1}R_C = 2g_{m2}R_C$$

$$\frac{v_{out2}}{v_{in}} = g_{m2}R_C$$

$$\Rightarrow \boxed{\frac{v_{out1}}{v_{in}} = 2 \frac{v_{out2}}{v_{in}}}$$

64)

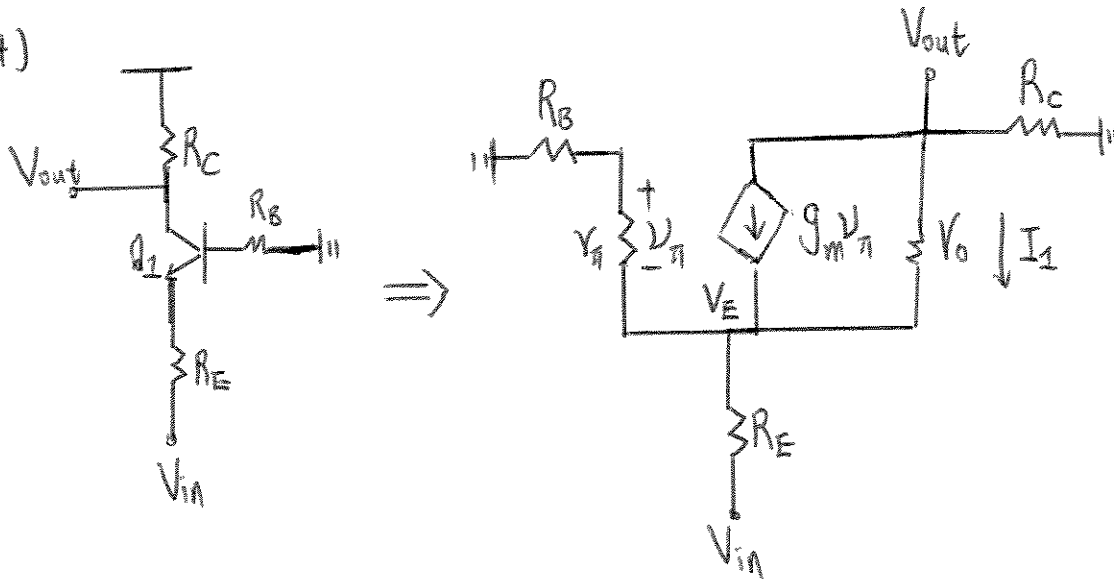

$$V_{out} = -(I_1 + g_m V_{\pi}) R_c, \quad I_1 = \frac{V_{out} - V_E}{r_o}$$

$$V_{out} = -\left(\frac{V_{out} - V_E}{r_o} + g_m V_{\pi}\right) R_c, \quad V_E = -\frac{g_m V_{\pi}}{\beta} (r_{\pi} + R_B)$$

$$V_{out} = -\left(\frac{V_{out} + \frac{g_m V_{\pi}}{\beta} (r_{\pi} + R_B)}{r_o} + g_m V_{\pi}\right) R_c$$

Rearranging

$$V_{\pi} = \frac{-(1 + \frac{R_c}{r_o}) V_{out}}{\frac{g_m (r_{\pi} + R_B) R_c + g_m R_c}{\beta r_o}} = A V_{out}$$

Summing the voltage at node E.

$$V_E - \left(\left(1 + \frac{1}{\beta}\right) g_m V_{\pi} + \frac{(V_{out} - V_E)}{r_o} \right) R_E = V_{in} \quad (1)$$

64) Writing V_E in terms of V_{π} , and V_{π} in terms of V_{out}

1) becomes

$$-\frac{g_m A V_{out}}{\beta} (Y_{\pi} + R_B) \left(1 + \frac{R_E}{Y_0}\right) - \left(1 + \frac{1}{\beta}\right) g_m A V_{out} R_E - \frac{V_{out} R_E}{Y_0} = V_{in}$$


Solving $V_{out} / V_{in} \Rightarrow$

$$\frac{V_{out}}{V_{in}} = \frac{1}{-\frac{g_m A}{\beta} (Y_{\pi} + R_B) \left(1 + \frac{R_E}{Y_0}\right) - \left(1 + \frac{1}{\beta}\right) g_m A R_E - \frac{R_E}{Y_0}}$$

substituting A into equation

$$\frac{V_{out}}{V_{in}} = \frac{g_m (Y_{\pi} + R_B) R_C + g_m R_C}{g_m \left(1 + \frac{R_E}{Y_0}\right) (Y_{\pi} + R_B) \left(1 + \frac{R_E}{Y_0}\right) + \left(1 + \frac{1}{\beta}\right) g_m \left(1 + \frac{R_C}{Y_0}\right) R_E - \frac{R_E}{Y_0} \left(\frac{g_m (Y_{\pi} + R_B) R_C}{\beta Y_0} + g_m R_C\right)}$$

65)

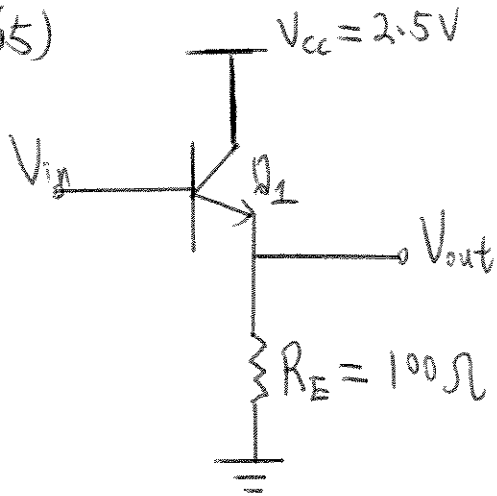

$$R_E = 100\Omega$$

$$V_A = \infty$$

$$|A_v| = 0.8$$


$$|A_v| = \frac{R_E}{R_E + \frac{1}{g_m}} = \frac{R_E I_c}{R_E I_c + V_T} = 0.8$$

$$\Rightarrow R_E I_c = 0.8(R_E I_c + V_T), \quad R_E = 100\Omega$$

$$\Rightarrow 0.1 I_c = 0.08 I_c + 0.0208 \Rightarrow 0.02 I_c = 0.0208$$

$$\Rightarrow I_c = 1.04 \text{ mA}$$

6b)

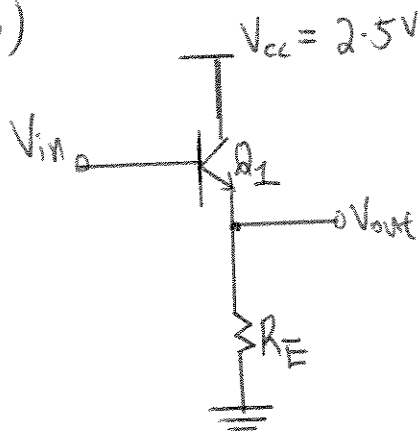

$$|A_v| > 0.9$$

$$R_{in} > 10\text{K}\Omega$$

$$|A_v| = \frac{R_E I_C}{R_E I_C + V_T} > 0.9 \Rightarrow R_E I_C > 0.9 [R_E I_C + V_T]$$

$$\Rightarrow R_E I_C > 9V_T = 234\text{mV}, \text{ Let } R_E I_C = 240\text{mV}$$

$$R_{in} = r_{\pi} + (1 + \beta) R_E > 10\text{K} \Rightarrow 100V_T + (101)R_E I_C > 10\text{K}\Omega I_C$$

substituting $R_E I_C = 240\text{mV} \Rightarrow I_C < 2.684\text{mA}$

$$\text{Choose } I_C \text{ to be } 2.5\text{mA} \Rightarrow R_E = 96\Omega$$

To Verify:


$$R_{in} = \frac{100(0.026)}{2.5} + (101)0.096 = 10.74\text{K}\Omega$$

$$|A_v| = \frac{(0.096)(2.5)}{(0.096)(2.5) + 0.026} = 0.902$$

5.67

$$\begin{aligned}R_{out} &= \frac{r_{\pi} + R_S}{1 + \beta} \\&= \frac{\beta V_T / I_C + R_S}{1 + \beta} \\&\leq 5 \Omega \\I_C &= \frac{\beta}{1 + \beta} I_E = \frac{\beta}{1 + \beta} I_1 \\ \frac{\frac{\beta(1+\beta)V_T}{\beta I_1} + R_S}{1 + \beta} &= \frac{\frac{(1+\beta)V_T}{I_1} + R_S}{1 + \beta} \\&\leq 5 \Omega \\I_1 &\geq \boxed{8.61 \text{ mA}}\end{aligned}$$

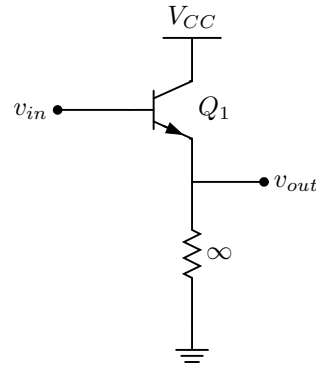- 5.68 (a) Looking into the collector of Q_2 we see an equivalent resistance of $r_{o2} = \infty$, so we can draw the following equivalent circuit:




$$A_v = \boxed{1}$$

$$R_{in} = \boxed{\infty}$$

$$R_{out} = \boxed{\frac{1}{g_{m1}} \parallel r_{\pi 1}}$$

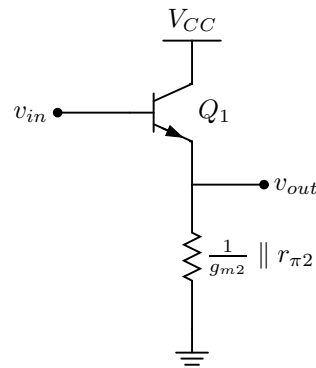- (b) Looking down from the emitter of Q_1 we see an equivalent resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2}$, so we can draw the following equivalent circuit:




$$A_v = \boxed{\frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + \frac{1}{g_{m2}} \parallel r_{\pi 2}}}$$

$$R_{in} = \boxed{r_{\pi 1} + (1 + \beta_1) \left(\frac{1}{g_{m2}} \parallel r_{\pi 2} \right)}$$

$$R_{out} = \boxed{\frac{1}{g_{m1}} \parallel r_{\pi 1} \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

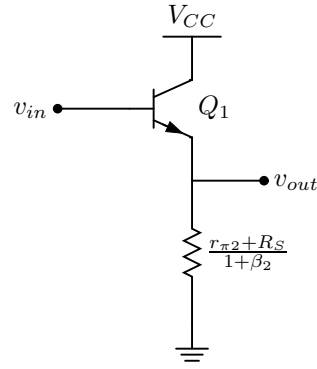- (c) Looking into the emitter of Q_2 we see an equivalent resistance of $\frac{r_{\pi 2} + R_S}{1 + \beta_2}$, so we can draw the following equivalent circuit:




$$A_v = \frac{\frac{r_{\pi 2} + R_S}{1 + \beta_2}}{\frac{1}{g_{m1}} + \frac{r_{\pi 2} + R_S}{1 + \beta_2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(\frac{r_{\pi 2} + R_S}{1 + \beta_2} \right)$$

$$R_{out} = \frac{1}{g_{m1}} \parallel r_{\pi 1} \parallel \left(\frac{r_{\pi 2} + R_S}{1 + \beta_2} \right)$$

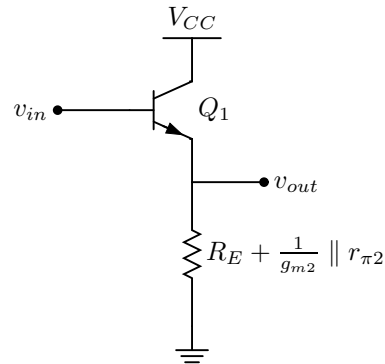- (d) Looking down from the emitter of Q_1 we see an equivalent resistance of $R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}$, so we can draw the following equivalent circuit:




$$A_v = \frac{R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(R_E + \frac{1}{g_{m2}} \right)$$


$$R_{out} = \frac{1}{g_{m1}} \parallel r_{\pi 1} \parallel \left(R_E + \frac{1}{g_{m2}} \right)$$

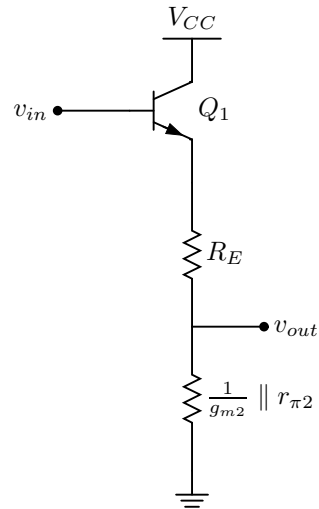- (e) Looking into the emitter of Q_2 we see an equivalent resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2}$, so we can draw the following equivalent circuit:




$$\begin{aligned}
 A_v &= \frac{R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}} \cdot \frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}} \\
 &= \boxed{\frac{\frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + R_E + \frac{1}{g_{m2}} \parallel r_{\pi 2}}} \\
 R_{in} &= \boxed{r_{\pi 1} + (1 + \beta_1) \left(R_E + \frac{1}{g_{m2} \parallel r_{\pi 2}} \right)} \\
 R_{out} &= \boxed{\left(\frac{1}{g_{m1}} \parallel r_{\pi 1} + R_E \right) \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}
 \end{aligned}$$

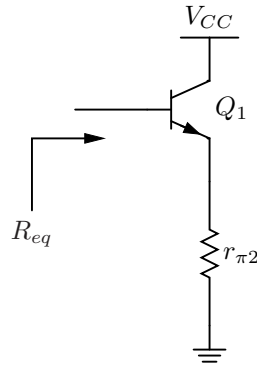- 5.69 (a) Looking into the base of Q_2 we see an equivalent resistance of $r_{\pi 2}$ (assuming the emitter of Q_2 is grounded), so we can draw the following equivalent circuit for finding the impedance at the base of Q_1 :



$$R_{eq} = r_{\pi 1} + (1 + \beta_1)r_{\pi 2}$$

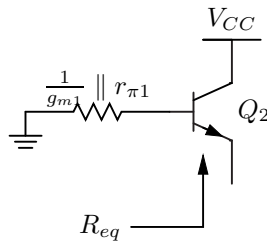- (b) Looking into the emitter of Q_1 we see an equivalent resistance of $\frac{1}{g_{m1}} \parallel r_{\pi 1}$ (assuming the base of Q_1 is grounded), so we can draw the following equivalent circuit for finding the impedance at the emitter of Q_2 :



$$R_{eq} = \frac{r_{\pi 2} + \frac{1}{g_{m1}} \parallel r_{\pi 1}}{1 + \beta_2}$$

- (c)

$$\begin{aligned} \frac{I_{C1} + I_{C2}}{I_{B1}} &= \frac{\beta_1 I_{B1} + \beta_2 (1 + \beta_1) I_{B1}}{I_{B1}} \\ &= \beta_1 + \beta_2 (1 + \beta_1) \end{aligned}$$

If we assume that $\beta_1, \beta_2 \gg 1$, then this simplifies to $\beta_1 \beta_2$, meaning a Darlington pair has a current gain approximately equal to the product of the current gains of the individual transistors.

5.70 (a)


$$R_{CS} = \boxed{r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel R_E)}$$

(b)

$$A_v = \frac{\boxed{r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel R_E)}}{\boxed{\frac{1}{g_{m1}} + r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel R_E)}}$$

$$R_{in} = \boxed{r_{\pi1} + (1 + \beta_1)[r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel R_E)]}$$
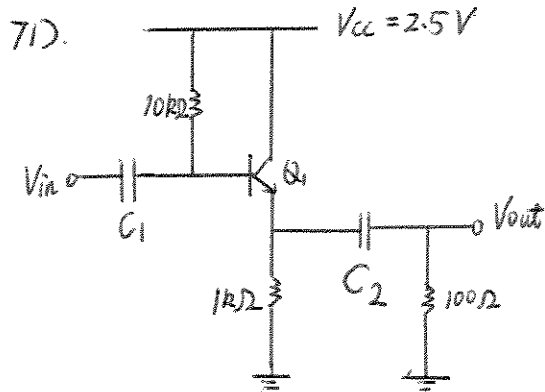
$$R_{out} = \boxed{\frac{1}{g_{m1}} \parallel r_{\pi1} \parallel [r_{o2} + (1 + g_{m2}r_{o2})(r_{\pi2} \parallel R_E)]}$$




$$I_s = 7 \times 10^{-16} \text{ A}$$

$$\beta = 100$$

$$V_A = 5 \text{ V}$$

DC Analysis: (Ignore V_o 's effect).

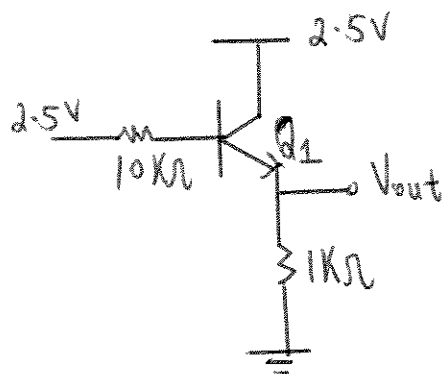

$$I_c = \beta \left(\frac{2.5 - (V_{BE} + \frac{I_c}{\alpha} 1 \text{ k}\Omega)}{10 \text{ k}\Omega} \right)$$

rearrange

$$I_c = \frac{2.5 - V_{BE}}{\frac{10 \text{ k}\Omega}{\beta} + \frac{1 \text{ k}\Omega}{\alpha}}$$

Guess: $V_{BE} = 0.7 \text{ V}$, $I_c = 1.621 \text{ mA}$

check for V_{BE} : $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.740 \text{ V}$, not 0.7, reiterate


$V_{BE} = 0.740 \text{ V}$, $I_c = 1.59 \text{ mA}$

check for V_{BE} : $V_{BE} = V_T \ln\left(\frac{I_c}{I_s}\right) = 0.740 \text{ V}$, converged.

So $I_c = 1.59 \text{ mA}$, $g_m = 0.0612 \left(\frac{1}{\Omega}\right) \text{ S}$, $\frac{1}{g_m} = 16.34 \Omega$,
 $V_o = 3.14 \text{ k}\Omega$


71)

AC Analysis: (Include V_o)

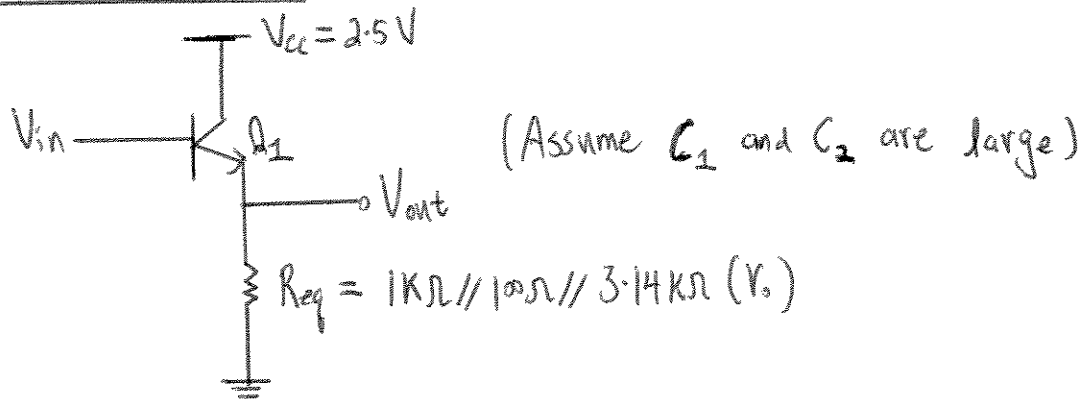

$$A_v = \frac{(1k\Omega // 100\Omega // 3.14k\Omega)}{16.34\Omega + (1k\Omega // 100\Omega // 3.14k\Omega)} = 0.84$$

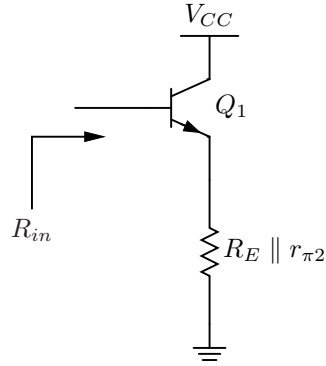- 5.72 (a) Looking into the base of Q_2 we see an equivalent resistance of $r_{\pi 2}$, so we can draw the following equivalent circuit for finding R_{in} :




$$R_{in} = r_{\pi 1} + (1 + \beta_1)(R_E \parallel r_{o1})$$

Looking into the collector of Q_2 we see an equivalent resistance of r_{o2} . Thus,

$$R_{out} = R_C \parallel r_{o2}$$

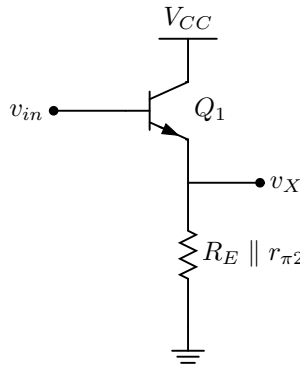- (b) Looking into the base of Q_2 we see an equivalent resistance of $r_{\pi 2}$, so we can draw the following equivalent circuit for finding v_X/v_{in} :



$$\frac{v_X}{v_{in}} = \frac{R_E \parallel r_{\pi 2} \parallel r_{o1}}{\frac{1}{g_{m1}} + R_E \parallel r_{\pi 2} \parallel r_{o1}}$$


We can find v_{out}/v_X by inspection.

$$\frac{v_{out}}{v_X} = -g_{m2}(R_C \parallel r_{o2})$$

$$A_v = \frac{v_X}{v_{in}} \cdot \frac{v_{out}}{v_X}$$

$$= -g_{m2}(R_C \parallel r_{o2}) \frac{R_E \parallel r_{\pi 2} \parallel r_{o1}}{\frac{1}{g_{m1}} + R_E \parallel r_{\pi 2} \parallel r_{o1}}$$

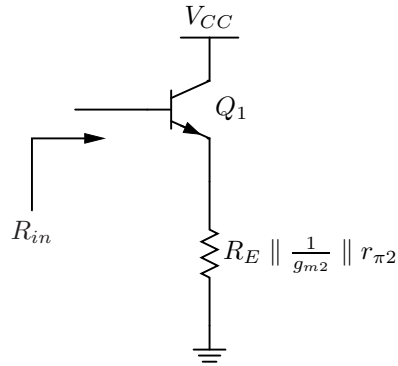- 5.73 (a) Looking into the emitter of Q_2 we see an equivalent resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2}$, so we can draw the following equivalent circuit for finding R_{in} :




$$R_{in} = r_{\pi 1} + (1 + \beta_1) \left(R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2} \right)$$

Looking into the collector of Q_2 , we see an equivalent resistance of ∞ (because $V_A = \infty$), so we have

$$R_{out} = R_C$$

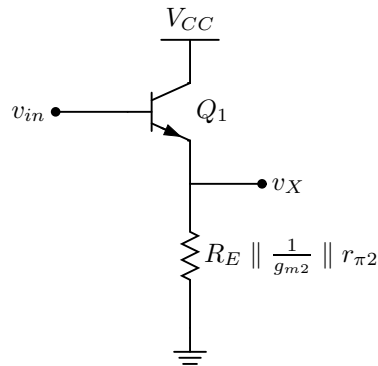- (b) Looking into the emitter of Q_2 we see an equivalent resistance of $\frac{1}{g_{m2}} \parallel r_{\pi 2}$, so we can draw the following equivalent circuit for finding v_X/v_{in} :



$$\frac{v_X}{v_{in}} = \frac{R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}$$

We can find v_{out}/v_X by inspection.

$$\begin{aligned} \frac{v_{out}}{v_X} &= g_{m2} R_C \\ A_v &= \frac{v_X}{v_{in}} \cdot \frac{v_{out}}{v_X} \\ &= g_{m2} R_C \frac{R_E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}}{\frac{1}{g_{m1}} + E \parallel \frac{1}{g_{m2}} \parallel r_{\pi 2}} \end{aligned}$$

$$\begin{aligned}
R_{out} &= R_C = \boxed{1 \text{ k}\Omega} \\
A_v &= -g_m R_C = -10 \\
g_m &= 10 \text{ mS} \\
I_C &= g_m V_T = 260 \text{ }\mu\text{A} \\
\frac{V_{CC} - V_{BE}}{R_B} &= I_B = \frac{I_C}{\beta} \\
R_B &= \beta \frac{V_{CC} - V_T \ln(I_C/I_S)}{I_C} \\
&= \boxed{694 \text{ k}\Omega} \\
R_{in} &= R_B \parallel r_\pi = 9.86 \text{ k}\Omega > 5 \text{ k}\Omega
\end{aligned}$$

In sizing C_B , we must consider the effect a finite impedance in series with the input will have on the circuit parameters. Any series impedance will cause R_{in} to increase and will not impact R_{out} . However, a series impedance can cause gain degradation. Thus, we must ensure that $|Z_B| = \left| \frac{1}{j\omega C_B} \right|$ does not degrade the gain significantly.

If we include $|Z_B|$ in the gain expression, we get:

$$A_v = -\frac{R_C}{\frac{1}{g_m} + \frac{(|Z_B|) \parallel R_B}{1+\beta}}$$

Thus, we want $\frac{1}{1+\beta} |Z_B| \ll \frac{1}{g_m}$ to ensure the gain is not significantly degraded.

$$\begin{aligned}
\frac{1}{1+\beta} \left| \frac{1}{j\omega C_B} \right| &\ll \frac{1}{g_m} \\
\frac{1}{1+\beta} \frac{1}{2\pi f C_B} &= \frac{1}{10} \frac{1}{g_m} \\
C_B &= \boxed{788 \text{ nF}}
\end{aligned}$$

5.75

$$R_{out} = R_C \leq 500 \Omega$$

To maximize gain, we should maximize R_C .

$$\begin{aligned} R_C &= \boxed{500 \Omega} \\ V_{CC} - I_C R_C &\geq V_{BE} - 400 \text{ mV} = V_T \ln(I_C/I_S) - 400 \text{ mV} \\ I_C &\leq 4.261 \text{ mA} \end{aligned}$$

To maximize gain, we should maximize I_C .

$$\begin{aligned} I_C &= \boxed{4.261 \text{ mA}} \\ I_B &= \frac{I_C}{\beta} = \frac{V_{CC} - V_{BE}}{R_B} \\ &= \frac{I_C}{\beta} = \frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} \\ R_B &= \boxed{40.613 \text{ k}\Omega} \end{aligned}$$

5.76

$$\begin{aligned}R_{out} &= R_C = \boxed{1 \text{ k}\Omega} \\|A_v| &= g_m R_C \\&= \frac{I_C R_C}{V_T} \\&\geq 20 \\I_C &\geq 520 \text{ }\mu\text{A}\end{aligned}$$

In order to maximize $R_{in} = R_B \parallel r_\pi$, we need to maximize r_π , meaning we should minimize I_C (since $r_\pi = \frac{\beta V_T}{I_C}$).

$$\begin{aligned}I_C &= 520 \text{ }\mu\text{A} \\I_B &= \frac{I_C}{\beta} = \frac{V_{CC} - V_{BE}}{R_B} \\&= \frac{V_{CC} - V_T \ln(I_C/I_S)}{R_B} \\R_B &= \boxed{343 \text{ k}\Omega}\end{aligned}$$

5.77

$$\begin{aligned}R_{out} &= R_C = \boxed{2 \text{ k}\Omega} \\A_v &= -g_m R_C \\&= -\frac{I_C R_C}{V_T} \\&= -15 \\I_C &= 195 \text{ }\mu\text{A} \\V_{BE} &= V_T \ln(I_C/I_S) = 689.2 \text{ mV} \\V_{CE} &\geq V_{BE} - 400 \text{ mV} = 289.2 \text{ mV}\end{aligned}$$

To minimize the supply voltage, we should minimize V_{CE} .

$$\begin{aligned}V_{CE} &= 289.2 \text{ mV} \\ \frac{V_{CC} - V_{CE}}{R_C} &= I_C \\ V_{CC} &= 679.2 \text{ mV}\end{aligned}$$

Note that this value of V_{CC} is less than the required V_{BE} . This means that the value of V_{CC} is constrained by V_{BE} , not V_{CE} . In theory, we could pick $V_{CC} = V_{BE}$, but in this case, we'd have to set $R_B = 0 \text{ }\Omega$, which would short the input to V_{CC} . Thus, let's pick a reasonable value for R_B , $R_B = \boxed{100 \text{ }\Omega}$.

$$\begin{aligned}\frac{V_{CC} - V_{BE}}{R_B} &= I_B = \frac{I_C}{\beta} \\ V_{CC} &= \boxed{689.4 \text{ mV}}\end{aligned}$$

$$\begin{aligned} |A_v| &= g_m R_C \\ &= \frac{I_C R_C}{V_T} \\ &= A_0 \\ R_{out} &= R_C \\ A_0 &= \frac{I_C R_{out}}{V_T} \\ I_C &= \frac{A_0 V_T}{R_{out}} \\ P &= I_C V_{CC} \\ &= \boxed{\frac{A_0 V_T}{R_{out}} V_{CC}} \end{aligned}$$

Thus, we must trade off a small output resistance with low power consumption (i.e., as we decrease R_{out} , power consumption increases and vice-versa).

5.79

$$P = (I_B + I_C)V_{CC}$$

$$= \frac{1 + \beta}{\beta} I_C V_{CC}$$

$$= 1 \text{ mW}$$

$$I_C = 396 \text{ } \mu\text{A}$$

$$\frac{V_{CC} - V_{BE}}{R_B} = I_B = \frac{I_C}{\beta}$$

$$R_B = \beta \frac{V_{CC} - V_T \ln(I_C/I_S)}{I_C}$$


$$= \boxed{453 \text{ k}\Omega}$$

$$A_v = -g_m R_C$$

$$= -\frac{I_C R_C}{V_T}$$

$$= -20$$

$$R_C = \boxed{1.31 \text{ k}\Omega}$$

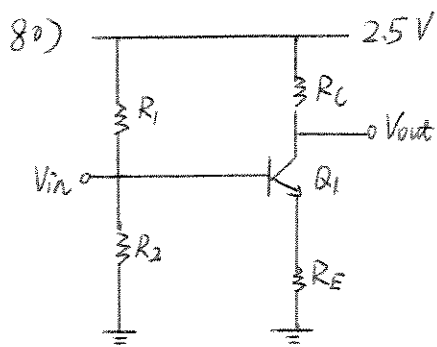

$$A_V = 5$$

$$R_{out} = R_C = 500\Omega$$

$$R_E I_C \approx 300\text{mV}$$

$$A_V = \frac{R_C I_C}{R_E I_C + V_T} = \frac{R_C I_C}{300 + 26} \Rightarrow R_C I_C = 1.63\text{V} \Rightarrow I_C = 3.26\text{mA}$$

$$R_E I_C \approx 300\text{mV} \Rightarrow R_E = 92\Omega$$

$$R_1 = \frac{2.5 - (V_{BE} + 0.3)}{10 I_B}, \quad V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.7624$$

$$10 I_B = 0.326\text{mA}$$

$$R_1 = \frac{2.5 - (0.7624 + 0.3)}{0.326} = 4.41\text{k}\Omega$$

$$R_2 = \frac{(0.7624 + 0.3)}{(9 \times 0.0326)} = 3.62\text{k}\Omega$$

$$V_{CE} = 2.5 - 1.63 - 0.3 = 0.57, \quad V_{BE} = 0.7624.$$

Q_1 is in soft saturation region, so active region characteristics

still apply.

$$R_C = 500\Omega$$

$$R_1 = 4.41\text{k}\Omega$$

$$R_2 = 3.62\text{k}\Omega$$

$$R_E = 92\Omega$$

$$\Rightarrow A_V = 5$$

$$R_{out} = 500\Omega$$

5.81

$$R_{out} = R_C \geq 1 \text{ k}\Omega$$

To maximize gain, we should maximize R_{out} .

$$\begin{aligned} R_C &= \boxed{1 \text{ k}\Omega} \\ V_{CC} - I_C R_C - I_E R_E &= V_{CE} \geq V_{BE} - 400 \text{ mV} \\ V_{CC} - I_C R_C - 200 \text{ mV} &\geq V_T \ln(I_C/I_S) - 400 \text{ mV} \\ I_C &\leq 1.95 \text{ mA} \end{aligned}$$

To maximize gain, we should maximize I_C .

$$\begin{aligned} I_C &= 1.95 \text{ mA} \\ I_E R_E &= \frac{1 + \beta}{\beta} I_C R_E = 200 \text{ mV} \\ R_E &= \boxed{101.5 \Omega} \\ V_{CC} - 10I_B R_1 - I_E R_E &= V_{BE} = V_T \ln(I_C/I_S) \\ R_1 &= \boxed{7.950 \text{ k}\Omega} \\ 9I_B R_2 - I_E R_E &= V_{BE} = V_T \ln(I_C/I_S) \\ R_2 &= \boxed{5.405 \text{ k}\Omega} \end{aligned}$$

$$\begin{aligned}
 P &= (10I_B + I_C)V_{CC} \\
 &= \left(10\frac{I_C}{\beta} + I_C\right)V_{CC} \\
 &= 5 \text{ mW}
 \end{aligned}$$

$$I_C = 1.82 \text{ mA}$$

$$I_E R_E = \frac{1 + \beta}{\beta} I_C R_E = 200 \text{ mV}$$

$$R_E = \boxed{109 \ \Omega}$$

$$\begin{aligned}
 A_v &= -\frac{R_C}{\frac{1}{g_m} + R_E} \\
 &= -\frac{R_C}{\frac{V_T}{I_C} + R_E} \\
 &= -5
 \end{aligned}$$

$$R_C = \boxed{616 \ \Omega}$$

$$V_{CC} - 10I_B R_1 - 200 \text{ mV} = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_1 = \boxed{8.54 \text{ k}\Omega}$$

$$9I_B R_2 - 200 \text{ mV} = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_2 = \boxed{5.79 \text{ k}\Omega}$$

$$R_{in} = \frac{1}{g_m} = 50 \, \Omega \text{ (since } R_E \text{ doesn't affect } R_{in}\text{)}$$

$$g_m = 20 \text{ mS}$$

$$I_C = g_m V_T = 520 \, \mu\text{A}$$

$$I_E R_E = \frac{1 + \beta}{\beta} I_C R_E = 260 \text{ mV}$$

$$R_E = \boxed{495 \, \Omega}$$

$$A_v = g_m R_C = 20$$

$$R_C = \boxed{1 \text{ k}\Omega}$$

$$V_{CC} - 10I_B R_1 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_1 = \boxed{29.33 \text{ k}\Omega}$$

$$9I_B R_2 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_2 = \boxed{20.83 \text{ k}\Omega}$$

To pick C_B , we must consider its effect on A_v . If we assume the capacitor has an impedance Z_B and $|Z_B| \ll R_1, R_2$, then we have:

$$A_v = \frac{R_C}{\frac{1}{g_m} + \frac{|Z_B|}{1+\beta}}$$

Thus, we should choose $\frac{1}{1+\beta} |Z_B| \ll \frac{1}{g_m}$.

$$\frac{1}{1+\beta} |Z_B| = \frac{1}{1+\beta} \frac{1}{2\pi f C_B} = \frac{1}{10} \frac{1}{g_m}$$

$$C_B = \boxed{1.58 \, \mu\text{F}}$$

$$R_{out} = R_C = \boxed{500 \Omega}$$

$$A_v = g_m R_C = 8$$

$$g_m = 16 \text{ mS}$$

$$I_C = g_m V_T = 416 \mu\text{A}$$

$$I_E R_E = \frac{1 + \beta}{\beta} I_C R_E = 260 \text{ mV}$$

$$R_E = \boxed{619 \Omega}$$

$$V_{CC} - 10I_B R_1 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_1 = \boxed{36.806 \text{ k}\Omega}$$

$$9I_B R_2 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_2 = \boxed{25.878 \text{ k}\Omega}$$

To pick C_B , we must consider its effect on A_v . If we assume the capacitor has an impedance Z_B and $|Z_B| \ll R_1, R_2$, then we have:

$$A_v = \frac{R_C}{\frac{1}{g_m} + \frac{|Z_B|}{1+\beta}}$$

Thus, we should choose $\frac{1}{1+\beta} |Z_B| \ll \frac{1}{g_m}$.

$$\frac{1}{1+\beta} |Z_B| = \frac{1}{1+\beta} \frac{1}{2\pi f C_B} = \frac{1}{10} \frac{1}{g_m}$$

$$C_B = \boxed{1.26 \mu\text{F}}$$

5.85

$$R_{out} = R_C = \boxed{200 \Omega}$$

$$A_v = g_m R_C = \frac{I_C R_C}{V_T} = 20$$

$$I_C = 2.6 \text{ mA}$$

$$P = V_{CC} (10I_B + I_C)$$

$$= V_{CC} \left(10 \frac{I_C}{\beta} + I_C \right)$$

$$= \boxed{7.15 \text{ mW}}$$

$$\begin{aligned}
 P &= (I_C + 10I_B) V_{CC} \\
 &= \left(I_C + 10 \frac{I_C}{\beta} \right) V_{CC} \\
 &= 5 \text{ mW}
 \end{aligned}$$

$$I_C = 1.82 \text{ mA}$$

$$A_v = g_m R_C$$

$$= \frac{I_C R_C}{V_T}$$

$$= 10$$

$$R_C = \boxed{143 \Omega}$$

$$I_E R_E = \frac{1 + \beta}{\beta} I_C R_E = 260 \text{ mV}$$

$$R_E = \boxed{141.6 \Omega}$$

$$V_{CC} - 10I_B R_1 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_1 = \boxed{8.210 \text{ k}\Omega}$$

$$9I_B R_2 - I_E R_E = V_{BE} = V_T \ln(I_C/I_S)$$

$$R_2 = \boxed{6.155 \text{ k}\Omega}$$

To pick C_B , we must consider its effect on A_v . If we assume the capacitor has an impedance Z_B and $|Z_B| \ll R_1, R_2$, then we have:

$$A_v = \frac{R_C}{\frac{1}{g_m} + \frac{|Z_B|}{1+\beta}}$$

Thus, we should choose $\frac{1}{1+\beta} |Z_B| \ll \frac{1}{g_m}$.

$$\frac{1}{1+\beta} |Z_B| = \frac{1}{1+\beta} \frac{1}{2\pi f C_B} = \frac{1}{10} \frac{1}{g_m}$$

$$C_B = \boxed{5.52 \mu\text{F}}$$

$$\begin{aligned}
R_{in} &= \frac{1}{g_m} = 50 \, \Omega \text{ (since } R_E \text{ doesn't affect } R_{in}\text{)} \\
g_m &= 20 \text{ mS} \\
I_C &= g_m V_T = 520 \, \mu\text{A} \\
A_v &= g_m R_C = 20 \\
R_C &= \boxed{1 \text{ k}\Omega} \\
I_E R_E &= \frac{1 + \beta}{\beta} I_C R_E = 260 \text{ mV} \\
R_E &= \boxed{495 \, \Omega}
\end{aligned}$$

To minimize the supply voltage, we should allow Q_1 to operate in soft saturation, i.e., $V_{BC} = 400 \text{ mV}$.

$$\begin{aligned}
V_{BE} &= V_T \ln(I_C/I_S) = 715 \text{ mV} \\
V_{CE} &= V_{BE} - 400 \text{ mV} = 315 \text{ mV} \\
V_{CC} - I_C R_C - I_E R_E &= V_{CE} \\
V_{CC} &= \boxed{1.095 \text{ V}} \\
V_{CC} - 10I_B R_1 - I_E R_E &= V_{BE} \\
R_1 &= \boxed{2.308 \text{ k}\Omega} \\
9I_B R_2 - I_E R_E &= V_{BE} \\
R_2 &= \boxed{20.827 \text{ k}\Omega}
\end{aligned}$$


To pick C_B , we must consider its effect on A_v . If we assume the capacitor has an impedance Z_B and $|Z_B| \ll R_1, R_2$, then we have:

$$A_v = \frac{R_C}{\frac{1}{g_m} + \frac{|Z_B|}{1+\beta}}$$

Thus, we should choose $\frac{1}{1+\beta} |Z_B| \ll \frac{1}{g_m}$.

$$\begin{aligned}
\frac{1}{1+\beta} |Z_B| &= \frac{1}{1+\beta} \frac{1}{2\pi f C_B} = \frac{1}{10} \frac{1}{g_m} \\
C_B &= \boxed{1.58 \, \mu\text{F}}
\end{aligned}$$

88)

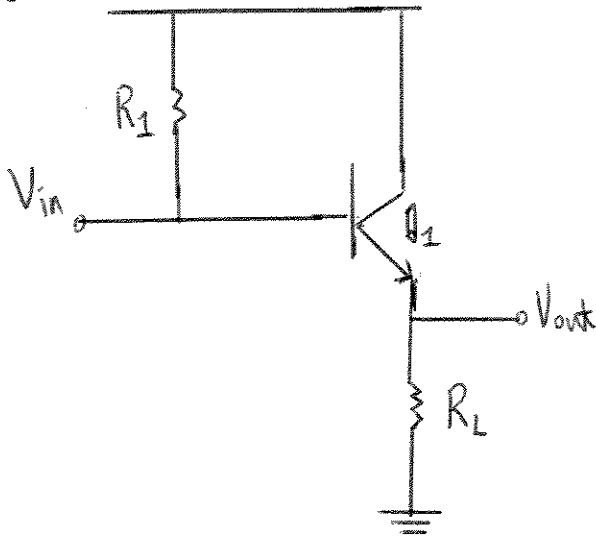

$$A_v = 0.85$$

$$R_{in} > 10\text{K}\Omega$$

$$R_L = 200\Omega$$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}} = 0.85 \Rightarrow \frac{200}{200 + \frac{1}{g_m}} = 0.85$$

$$\Rightarrow 200 = 0.85 \left(200 + \frac{1}{g_m} \right) \Rightarrow \frac{1}{g_m} = 35.294\Omega$$

$$\Rightarrow I_c = \frac{26\text{mV}}{35.294\Omega} = 0.737\text{mA}, \quad V_{BE} = V_T \ln\left(\frac{0.737}{6 \times 10^{-8}}\right) = 0.724\text{V}$$

$$R_{in} = R_1 \parallel (r_{\pi} + (1 + \beta)(200\Omega))$$

$$R_{in} = R_1 \parallel 23.73\text{K}$$

$$R_{in} = \frac{R_1 \cdot 23.73\text{K}}{R_1 + 23.73\text{K}} > 10\text{K} \Rightarrow R_1 > 17.28\text{K} \text{ (Input Impedance Requirement)}$$

To support an I_c of 0.737, R_1 must be determined.

88)


$$R_1 = \frac{2.5 - (0.724 + (0.737)(0.2)/0.99)}{0.737 / 100}$$

$$R_1 = 220.77 \text{ k}\Omega$$

$$R_1 = 220.77 \text{ k}\Omega \Rightarrow R_{in} = 220.77 \text{ k}\Omega // 23.73 \text{ k}\Omega$$
$$R_{in} = 21.43 \text{ k}\Omega > 10 \text{ k}\Omega$$

$$\begin{array}{l} R_1 = 220.77 \text{ k}\Omega \\ R_L = 200 \Omega \end{array} \Rightarrow \begin{array}{l} A_v = 0.85 \\ R_{in} = 21.43 \text{ k}\Omega \end{array}$$

89)

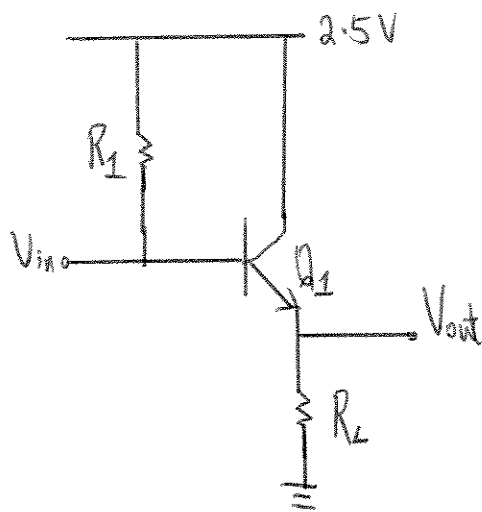

$$\text{Power} = 5 \text{ mW}$$

$$A_v = 0.9$$

$$A_v = \frac{R_L}{R_L + \frac{1}{g_m}} = 0.9 \Rightarrow R_L = 0.9 \left(R_L + \frac{1}{g_m} \right)$$

$$R_L = 9 \frac{1}{g_m}$$

$$\text{Power} = 2.5 \left(I_c + \frac{I_c}{\beta} \right) \Rightarrow I_c = 1.98 \text{ mA}$$

$$\frac{1}{g_m} = \frac{V_T}{I_c} = \frac{26 \text{ mV}}{1.98 \text{ mA}} = 13.13 \Omega$$

$$R_L = (9)(13.13) = 118.17 \Omega.$$

This is the minimum load resistance, since anything lower will lower the voltage gain.

5.90 As stated in the hint, let's assume that $I_E R_E \gg V_T$. Given this assumption, we can assume that R_E does not affect the gain.

$$I_E R_E = 10V_T = 260 \text{ mV}$$

$$A_v = \frac{R_L}{\frac{1}{g_m} + R_L} = 0.8$$

$$g_m = 80 \text{ mS}$$

$$I_C = g_m V_T = 2.08 \text{ mA}$$

$$\frac{1 + \beta}{\beta} I_C R_E = 260 \text{ mV}$$

$$R_E = \boxed{124 \Omega}$$

$$V_{CC} - I_B R_1 - I_E R_E = V_{BE} = V_T \ln(I_C / I_S)$$

$$R_1 = \boxed{71.6 \text{ k}\Omega}$$

To pick C_1 , we must consider its effect on A_v . If we assume the capacitor has an impedance Z_1 and $|Z_1| \ll R_1$, then we have:

$$A_v = \frac{R_E}{\frac{1}{g_m} + R_E + \frac{|Z_1|}{1 + \beta}}$$

Thus, we should choose $\frac{1}{1 + \beta} |Z_1| \ll \frac{1}{g_m}$.

$$\frac{1}{1 + \beta} |Z_1| = \frac{1}{1 + \beta} \frac{1}{2\pi f C_1} = \frac{1}{10} \frac{1}{g_m}$$

$$C_1 = \boxed{12.6 \text{ pF}}$$

To pick C_2 , we must also consider its effect on A_v . Since the capacitor appears in series with R_L , we need to ensure that $|Z_2| \ll R_L$, assuming the capacitor has impedance Z_2 .

$$|Z_2| = \frac{1}{2\pi f C_2} = \frac{1}{10} R_L$$

$$C_2 = \boxed{318 \text{ pF}}$$