

7.1

$$V_{GS} = V_{DD} = 1.8 \text{ V}$$

$V_{DS} > V_{GS} - V_{TH}$ (in order for M_1 to operate in saturation)

$$V_{DS} = V_{DD} - I_D(1 \text{ k}\Omega)$$

$$= V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 \text{ k}\Omega)$$

$$> V_{GS} - V_{TH}$$

$$\frac{W}{L} < \boxed{2.04}$$

② To get $I_{DS} = 1 \text{ mA}$,

$$\frac{1}{2} M C_ox \left(\frac{W}{L}\right) \left(V_{GS} - V_{TH}\right)^2 = 1 \times 10^{-3} \text{ A.}$$

$$\frac{1}{2} (200 \times 10^{-6}) \left(\frac{20}{0.18}\right) \left(V_{GS} - V_{TH}\right)^2 = 10^{-3}$$

$$\left(V_{GS} - V_{TH}\right)^2 = 0.09$$

$$V_{GS} - V_{TH} = 0.3,$$

$$\text{i.e. } V_{GS} = 0.7,$$

Since $V_{GS} = \frac{R_2}{R_1 + R_2} \times 1.8$

$$0.7 = \frac{R_2}{R_1 + R_2} \times 1.8$$

$$0.7 R_1 = R_2,$$

$$\therefore \frac{R_1}{R_2} = \frac{11}{7}. \quad \text{---} \textcircled{1}$$

To get input impedance $\geq 20 \text{ k}\Omega$.

$$R_1 // R_2 \geq 20 \text{ k}\Omega. \quad \text{---} \textcircled{2}$$

By inspection, setting $R_1 = 55 \text{ k}\Omega$ and $R_2 = 35 \text{ k}\Omega$
will satisfy both ① and ②.

7.3

$$\begin{aligned}
 V_{GS} &= V_{DD} - I_D(100 \Omega) \\
 V_{DS} &= V_{DD} - I_D(1 \text{ k}\Omega + 100 \Omega) \\
 &> V_{GS} - V_{TH} \quad (\text{in order for } M_1 \text{ to operate in saturation}) \\
 V_{DD} - I_D(1 \text{ k}\Omega + 100 \Omega) &> V_{DD} - I_D(100 \Omega) - V_{TH} \\
 I_D(1 \text{ k}\Omega + 100 \Omega) &< I_D(100 \Omega) + V_{TH} \\
 I_D(1 \text{ k}\Omega) &< V_{TH} \\
 I_D &< 400 \mu\text{A}
 \end{aligned}$$

Since g_m increases with I_D , we should pick the maximum I_D to determine the maximum transconductance that M_1 can provide.

$$\begin{aligned}
 I_{D,max} &= 400 \mu\text{A} \\
 g_{m,max} &= \frac{2I_{D,max}}{V_{GS} - V_{TH}} \\
 &= \frac{2I_{D,max}}{V_{DD} - I_{D,max}(100 \Omega) - V_{TH}} \\
 &= \boxed{0.588 \text{ mS}}
 \end{aligned}$$

$$\textcircled{4} \quad a) \quad \therefore V_{RS} = 200 \text{ mV}$$

$$\therefore I_{DS} R_S = 200 \text{ mV}$$

$$I_{DS} = \frac{0.2}{100}$$

$$I_{DS} = 2 \text{ mA.}$$

For M, to stay in saturation,

$$V_{DS} \geq V_{GS} - V_{TH}.$$

$$\begin{aligned} \therefore V_{DS} &= V_D - V_S \\ &= [1.8 - (2 \times 10^{-3}) \times 500] - 0.2 \\ &= 0.6, \end{aligned}$$

$$\therefore V_{GS} - V_{TH} \leq 0.6,$$

$$\text{Since } I_{DS} = \frac{1}{2} (M_n C_{ox}) \left(\frac{W}{L}\right) (V_{GS} - V_{TH})^2,$$

$\left(\frac{W}{L}\right)$ is min. when $(V_{GS} - V_{TH})$ is max,

$$\therefore \text{min. } \left(\frac{W}{L}\right), \text{ is when } (V_{GS} - V_{TH}) = 0.6 \text{ V,}$$

$$2 \times 10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{W}{L}\right), (0.6)^2$$

$$\therefore \text{min. } \left(\frac{W}{L}\right), \approx 56$$

b) With $(V_{GS} - V_{TH}) = 0.6$,

$$V_{GS} = 1,$$

$$\therefore V_G = 1 + V_S$$

$$V_G = 1.2V,$$

$$\text{i.e. } 1.8 \times \frac{R_2}{R_1 + R_2} = 1.2V,$$

$$\frac{R_2}{R_1} = 2 \quad \text{--- (1)}$$

$$\text{Input impedance} = R_2 // R_1,$$

$$\text{i.e. } R_2 // R_1 \geq 30k\Omega \quad \text{--- (2)}$$

$$\text{Set } R_1 = 50k\Omega \text{ and } R_2 = 100k\Omega$$

will satisfy both (1) & (2).

7.5

$$I_{D1} = 0.5 \text{ mA}$$

$$V_{GS} = V_{TH} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \frac{W}{L}}}$$

$$= 0.612 \text{ V}$$

$$V_{GS} = \frac{1}{10} I_{D1} R_2$$

$$R_2 = \boxed{12.243 \text{ k}\Omega}$$

$$V_{GS} = V_{DD} - \frac{1}{10} I_{D1} R_1 - \frac{11}{10} I_{D1} R_S$$

$$R_1 = \boxed{21.557 \text{ k}\Omega}$$

7.6

$$I_D = 1 \text{ mA}$$

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}} = \frac{1}{100}$$

$$V_{GS} = 0.6 \text{ V}$$

$$V_{GS} = V_{DD} - I_D R_D$$

$$R_D = \boxed{1.2 \text{ k}\Omega}$$

$$\textcircled{7} \quad I_{DS} = \frac{1}{2} (M_n C_{ox}) \left(\frac{W}{L} \right) (V_{GS} - V_{TN})^2$$

$$0.5 \times 10^{-3} = (100 \times 10^{-6}) \left(\frac{50}{0.18} \right) (V_{GS} - V_{TN})^2$$

$$\therefore V_{GS} = 0.534 V$$

$$\therefore R_2 = \frac{0.534}{0.05 \times 10^{-3}}$$

$$R_2 = \underline{\underline{10.68 k\Omega}}$$

$$\therefore V_{D1} = 1.8 - (1.1 \times I_{DS} \times 2 k\Omega) = 0.1 I_{DS} (R_1 + R_2),$$

$$\therefore 14 k\Omega = R_1 + 10.68 k\Omega.$$

$$\therefore R_1 = \underline{\underline{3320 \Omega}}$$

7.8 First, let's analyze the circuit excluding R_P .

$$V_G = \frac{20 \text{ k}\Omega}{10 \text{ k}\Omega + 20 \text{ k}\Omega} V_{DD} = 1.2 \text{ V}$$


$$V_{GS} = V_G - I_D R_S = V_{DS} = V_{DD} - I_D(1 \text{ k}\Omega + 200 \text{ }\Omega)$$

$$I_D = 600 \text{ }\mu\text{A}$$

$$V_{GS} = 1.08 \text{ V}$$

$$\frac{W}{L} = \frac{2I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^2} = 12.9758 \approx [13]$$

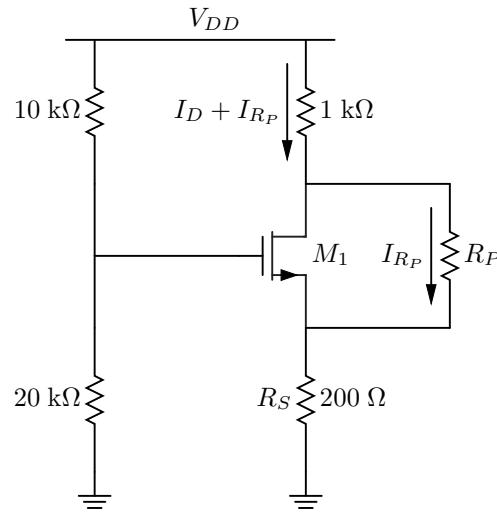Now, let's analyze the circuit with R_P .



$$V_G = 1.2 \text{ V}$$

$$I_D + I_{R_P} = \frac{V_{DD} - V_{DS}}{1 \text{ k}\Omega + 200 \text{ }\Omega}$$

$$V_{GS} = V_G - (I_D + I_{R_P}) R_S = V_{DS} + V_{TH}$$

$$V_G - \frac{V_{DD} - V_{DS}}{1 \text{ k}\Omega + 200 \text{ }\Omega} R_S = V_{DS} + V_{TH}$$

$$V_{DS} = 0.6 \text{ V}$$

$$V_{GS} = 1 \text{ V}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\ = 467 \text{ }\mu\text{A}$$

$$I_D + I_{R_P} = I_D + \frac{V_{DS}}{R_P} = \frac{V_{DD} - V_{DS}}{1 \text{ k}\Omega + 200 \text{ }\Omega}$$

$$R_P = [1.126 \text{ k}\Omega]$$

7.9 First, let's analyze the circuit excluding R_P .


$$V_{GS} = V_{DD} = 1.8 \text{ V}$$

$$V_{DS} = V_{DD} - I_D(2 \text{ k}\Omega) = V_{GS} - 100 \text{ mV}$$

$$V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (2 \text{ k}\Omega) = V_{GS} - 100 \text{ mV}$$

$$\frac{W}{L} = \boxed{0.255}$$

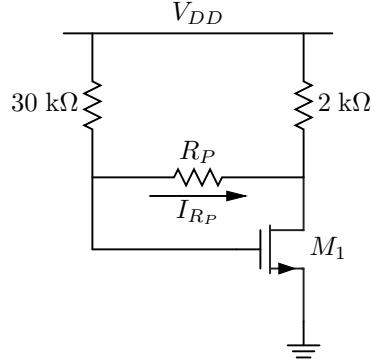Now, let's analyze the circuit with R_P .



$$V_{GS} = V_{DD} - I_{R_P}(30 \text{ k}\Omega)$$

$$I_{R_P} = \frac{V_{GS} - V_{DS}}{R_P} = \frac{50 \text{ mV}}{R_P}$$

$$V_{GS} = V_{DD} - (I_D - I_{R_P})(2 \text{ k}\Omega) + 50 \text{ mV}$$

$$V_{DD} - I_{R_P}(30 \text{ k}\Omega) = V_{DD} - \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 - I_{R_P} \right) (2 \text{ k}\Omega) + 50 \text{ mV}$$

$$V_{DD} - I_{R_P}(30 \text{ k}\Omega) = V_{DD} - \left(\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{DD} - I_{R_P}(30 \text{ k}\Omega) - V_{TH})^2 - I_{R_P} \right) (2 \text{ k}\Omega) + 50 \text{ mV}$$

$$I_{R_P} = 1.380 \mu\text{A}$$

$$R_P = \frac{50 \text{ mV}}{I_{R_P}} = \boxed{36.222 \text{ k}\Omega}$$

(10) For M_1 ,

$$I_x = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{\omega_1}{0.25}\right) (0.8 - 0.4)^2 \times (1 + 0.1(0.8))$$

$$10^{-3} = 0.16 \times 10^{-4} \left(\frac{\omega_1}{0.25}\right) (1.08)$$

$$\therefore \omega_1 \approx 14.5 \text{ rad//}$$

For M_2 ,

$$0.5 \times 10^{-3} = 0.16 \times 10^{-4} \left(\frac{\omega_2}{0.25}\right) (1.08)$$

$$\therefore \omega_2 \approx 7.25 \text{ rad//}$$

$$\begin{aligned} \text{Output resistance} &= r_o \\ &= \frac{1}{\pi} \times \frac{1}{I_d} \end{aligned}$$

$$\begin{aligned} \therefore r_{o1} &= \left(\frac{1}{0.1}\right) \left(\frac{1}{10^{-3}}\right) \\ &= 10 \text{ k}\Omega // \end{aligned}$$

$$\begin{aligned} r_{o2} &= \left(\frac{1}{0.1}\right) \left(\frac{1}{0.5 \times 10^{-3}}\right) \\ &= 20 \text{ k}\Omega // \end{aligned}$$

$$\textcircled{11} \quad R_{out} = \frac{1}{\lambda} \left(\frac{1}{I_p} \right)$$
$$= \frac{1}{0.5 \times 10^{-3} \text{ A}} = 20 \text{ k}\Omega$$

$$\therefore \lambda = 0.1 \text{ V}^{-1}$$

7.12 Since we're not given V_{DS} for the transistors, let's assume $\lambda = 0$ for large-signal calculations. Let's also assume the transistors operate in saturation, since they're being used as current sources.

$$I_X = \frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} (V_{B1} - V_{TH})^2 = 0.5 \text{ mA}$$

$$W_1 = \boxed{3.47 \text{ } \mu\text{m}}$$

$$I_Y = \frac{1}{2} \mu_n C_{ox} \frac{W_2}{L_2} (V_{B2} - V_{TH})^2 = 0.5 \text{ mA}$$

$$W_2 = \boxed{1.95 \text{ } \mu\text{m}}$$

$$R_{out1} = r_{o1} = \frac{1}{\lambda I_X} = 20 \text{ k}\Omega$$

$$R_{out2} = r_{o2} = \frac{1}{\lambda I_Y} = 20 \text{ k}\Omega$$

Since $I_X = I_Y$ and λ is the same for each current source, the output resistances of the current sources are the same.

7.13 Looking into the source of M_1 we see a resistance of $\frac{1}{g_m}$. Including λ in our analysis, we have

$$\begin{aligned}\frac{1}{g_m} &= \frac{1}{\mu_p C_{ox} \frac{W}{L} (V_X - V_{B1} - |V_{TH}|) (1 + \lambda V_X)} \\ &= \boxed{372 \Omega}\end{aligned}$$

(14)

$$I_x = \frac{1}{2} (100 \times 10^{-6}) \left(\frac{2^{\circ}}{0.25} \right) (1 - 1.8 + 0.4)^2$$

$$= 0.64 \text{ mA}$$

$$I_y = \frac{1}{2} (100 \times 10^{-6}) \left(2 \times \frac{2^{\circ}}{0.25} \right) (1 - 1.8 + 0.4)^2$$

$$= 1.28 \text{ mA}$$

$$\therefore r_o \propto \frac{1}{I}$$

$$\text{and } I_y = 2 I_x$$

$$\therefore r_{\text{out}, m_1} = 2 r_{\text{out}, m_2}$$

$$\textcircled{15} \quad |I_{DS1}| = |I_{DS2}|,$$

$$\begin{aligned}\frac{1}{2}(200 \times 10^{-6})\left(\frac{10}{0.18}\right) (V_B - 0.4)^2(1 + 0.1 \times 0.9) \\ = \frac{1}{2}(100 \times 10^{-6})(1.8 - V_B - 0.4)^2(1 + 0.1 \times 0.9) \\ \times \left(\frac{30}{0.18}\right)\end{aligned}$$

$$2(V_B - 0.4)^2 = 3(1.4 - V_B)^2$$

$$\sqrt{\frac{2}{3}}(V_B - 0.4) = (1.4 - V_B)$$

$$1.816 V_B = 1.7264$$

$$V_B = 0.95 //$$

(16) a) For M_1 ,

$$I_{DS1} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{5}{0.18} \right) (V_B - 0.4)^2 (1 + 0.1 \times 0.9)$$

$$\therefore V_B \approx 0.806 V$$

b) There are 3 regions of operation:

For $V_x < V_B - V_{TH1}$, M_1 is in triode.

$$\text{and } |I_{DS2}| > |I_{DS1}|$$

For $|V_x - V_{DD}| > |V_B - V_{DD} - V_{TH2}|$, M_2 is in triode


$$\text{and } I_{DS1} > |I_{DS2}|$$

For $V_B - V_{TH2} < V_x$ and $|V_x - V_{DD}| < |V_B - V_{DD} - V_{TH2}|$

M_1 and M_2 are in saturation.

$$\text{and } I_{DS1} = |I_{DS2}| = 0.5 \text{ mA at } V_x = 0.9 V$$

In all cases, $I_x = I_{DS1} - |I_{DS2}|$

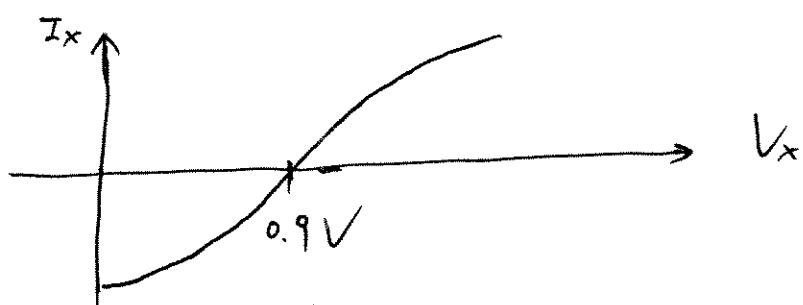

7.17 (a) Assume M_1 is operating in saturation.

$$I_D = 0.5 \text{ mA}$$
$$V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}}$$
$$= \boxed{0.573 \text{ V}}$$

$V_{DS} = V_{DD} - I_D R_D = 0.8 \text{ volt} > V_{GS} - V_{TH}$, verifying that M_1 is in saturation

(b)

$$A_v = -g_m R_D$$
$$= -\frac{2I_D}{V_{GS} - V_{TH}} R_D$$
$$= \boxed{-11.55}$$

7.18 (a) Assume M_1 is operating in saturation.

$$I_D = 0.25 \text{ mA}$$

$$\begin{aligned} V_{GS} &= V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \\ &= \boxed{0.55 \text{ V}} \end{aligned}$$

$V_{DS} = V_{DD} - I_D R_D = 1.3 \text{ V} > V_{GS} - V_{TH}$, verifying that M_1 is in saturation

(b)

$$V_{GS} = 0.55 \text{ V}$$

$V_{DS} > V_{GS} - V_{TH}$ (to ensure M_1 remains in saturation)

$$V_{DD} - I_D R_D > V_{GS} - V_{TH}$$

$$\begin{aligned} V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 R_D &> V_{GS} - V_{TH} \\ \frac{W}{L} &< \frac{2(V_{DD} - V_{GS} + V_{TH})}{\mu_n C_{ox} (V_{GS} - V_{TH})^2 R_D} \\ &= 366.67 \\ &= 3.3 \frac{20}{0.18} \end{aligned}$$

Thus, W/L can increase by a factor of $\boxed{3.3}$ while M_1 remains in saturation.

$$\begin{aligned} A_v &= -g_m R_D \\ &= -\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) R_D \\ A_{v,max} &= -\mu_n C_{ox} \left(\frac{W}{L} \right)_{max} (V_{GS} - V_{TH}) R_D \\ &= \boxed{-22} \end{aligned}$$

7.19

$$P = V_{DD}I_D < 1 \text{ mW}$$

$$I_D < 556 \mu\text{A}$$

$$A_v = -g_m R_D$$

$$= -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D R_D}$$

$$= -5$$

$$\frac{W}{L} < \frac{20}{0.18}$$

$$R_D > \boxed{1.006 \text{ k}\Omega}$$

7.20 (a)

$$\begin{aligned}I_{D1} &= I_{D2} = 0.5 \text{ mA} \\A_v &= -g_{m1} (r_{o1} \parallel r_{o2}) \\&= -\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} \left(\frac{1}{\lambda_1 I_{D1}} \parallel \frac{1}{\lambda_2 I_{D2}} \right) \\&= -10 \\\left(\frac{W}{L}\right)_1 &= \boxed{7.8125}\end{aligned}$$

(b)

$$\begin{aligned}V_{DD} - V_B &= V_{TH} + \sqrt{\frac{2 |I_{D2}|}{\mu_p C_{ox} \left(\frac{W}{L}\right)_2}} \\V_B &= \boxed{1.1 \text{ V}}\end{aligned}$$

$$(21) |A_v| = f_{m1} (r_{o1} // r_{o2})$$

$$f_{m1} = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{20}{0.18}\right) \times (0.001)}$$

(Since V_{ds1} is not given, assume
(if $\lambda_1 V_{ds1}$) has minimal effect on f_{m1})

$$= 6.67 \text{ mS.} \quad (S = \Omega^{-1})$$

$$\begin{aligned} r_{o1} &= \frac{1}{\lambda_1 \times I_{D1}} \\ &= \frac{1}{0.1 \times 1mA} \\ &= 10 k\Omega. \end{aligned}$$

$$r_{o2} = \infty$$

$$(\because \lambda_2 \ll \lambda_1)$$

$$\begin{aligned} \therefore |A_v| &= 6.67 \times 10^{-3} \times 10^3 \times 10 \\ &= 66.7 // \end{aligned}$$

- 7.22 (a) If I_{D1} and I_{D2} remain constant while W and L double, then $g_{m1} \propto \sqrt{(W/L)_1 I_{D1}}$ will not change (since it depends only on the ratio W/L), $r_{o1} \propto \frac{1}{I_{D1}}$ will not change, and $r_{o2} \propto \frac{1}{I_{D2}}$ will not change. Thus, $A_v = -g_{m1} (r_{o1} \parallel r_{o2})$ will not change.
- (b) If I_{D1} , I_{D2} , W , and L double, then $g_{m1} \propto \sqrt{(W/L)_1 I_{D1}}$ will increase by a factor of $\sqrt{2}$, $r_{o1} \propto \frac{1}{I_{D1}}$ will halve, and $r_{o2} \propto \frac{1}{I_{D2}}$ will halve. This means that $r_{o1} \parallel r_{o2}$ will halve as well, meaning $A_v = -g_{m1} (r_{o1} \parallel r_{o2})$ will decrease by a factor of $\sqrt{2}$.

(23). To get higher voltage gain,

(a) is preferred.

For the same dimensions of transistors
and same bias current,

(a) has a high " g_m " than (b).

$$\therefore g_{m1} > g_{m2}$$

$$(\text{since } M_n C_{ox} > M_p C_{ox})$$

while (R_{o1}/R_{o2}) is the same
for both cases.

$$(24) \quad Av = f_{m_2} (r_{o1} // r_{o2})$$

$$r_{o1} = \frac{1}{0.15 \times 0.5mA}$$

$$= 13.3 k\Omega.$$

$$r_{o2} = \frac{1}{0.05 \times 0.5mA}$$

$$= 40 k\Omega.$$

$$\therefore r_{o1} // r_{o2} = 10 k\Omega.$$

$$\therefore 15 = \left[\sqrt{2 \times (100 \times 10^{-6}) \left(\frac{w}{l} \right)_2 \cdot 0.5mA} \right] \cdot (10 k\Omega)$$

$$\left(\frac{w}{l} \right)_2 = 22.5 \cancel{\parallel}$$

(25) From Eg (7.57),

$$3 = \sqrt{\frac{20/0.18}{(w/L)_2}}$$

$$\therefore (w/L)_2 \approx 12.3 //$$

7.26 (a)

$$\begin{aligned}
 I_{D1} &= I_{D2} = 0.5 \text{ mA} \\
 V_{GS1} &= V_{TH} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} \\
 &= 0.7 \text{ V} \\
 V_{DS1} &= V_{GS1} - V_{TH} \text{ (in order of } M_1 \text{ to operate at the edge of saturation)} \\
 &= V_{DD} - V_{GS2} \\
 V_{GS2} &= V_{DD} - V_{GS1} + V_{TH} = V_{TH} + \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} \\
 \left(\frac{W}{L}\right)_2 &= \boxed{4.13}
 \end{aligned}$$

(b)

$$\begin{aligned}
 A_v &= -\frac{g_{m1}}{g_{m2}} \\
 &= -\frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}}{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_{D2}}} \\
 &= -\sqrt{\frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2}} \\
 &= \boxed{-3.667}
 \end{aligned}$$

- (c) Since $(W/L)_1$ is fixed, we must minimize $(W/L)_2$ in order to maximize the magnitude of the gain (based on the expression derived in part (b)). If we pick the size of M_2 so that M_1 operates at the edge of saturation, then if M_2 were to be any smaller, V_{GS2} would have to be larger (given the same I_{D2}), driving M_1 into triode. Thus, $(W/L)_2$ is its smallest possible value (without driving M_1 into saturation) when M_1 is at the edge of saturation, meaning the gain is largest in magnitude with this choice of $(W/L)_2$.

7.27 (a)

$$\begin{aligned}
A_v &= -\frac{g_{m1}}{g_{m2}} \\
&= -\frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}}{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_2 I_{D2}}} \\
&= -\sqrt{\frac{\left(\frac{W}{L}\right)_1}{\left(\frac{W}{L}\right)_2}} \\
&= -5 \\
\left(\frac{W}{L}\right)_1 &= \boxed{277.78}
\end{aligned}$$

(b)

$$\begin{aligned}
V_{DS1} &> V_{GS1} - V_{TH} \text{ (to ensure } M_1 \text{ is in saturation)} \\
V_{DD} - V_{GS2} &> V_{GS1} - V_{TH} \\
V_{DD} - V_{TH} - \sqrt{\frac{2I_{D2}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_2}} &> \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1}} \\
I_{D1} = I_{D2} &< \boxed{1.512 \text{ mA}}
\end{aligned}$$

7.28 For this problem, recall that looking into the drain of a transistor with a grounded gate and source we see a resistance of r_o , and looking into either terminal of a diode-connected transistor we see a resistance of $\frac{1}{g_m} \parallel r_o$.

(a)

$$A_v = \boxed{-g_{m1} \left(r_{o1} \parallel \frac{1}{g_{m2}} \parallel r_{o2} \right)}$$

(b)

$$A_v = \boxed{-g_{m1} \left(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m3}} \parallel r_{o3} \right)}$$

(c)

$$A_v = \boxed{-g_{m1} \left(r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m3}} \parallel r_{o3} \right)}$$


(d)

$$A_v = \boxed{-g_{m2} \left(r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{m3}} \parallel r_{o3} \right)}$$

(e)

$$A_v = \boxed{-g_{m2} \left(r_{o2} \parallel r_{o1} \parallel \frac{1}{g_{m3}} \parallel r_{o3} \right)}$$

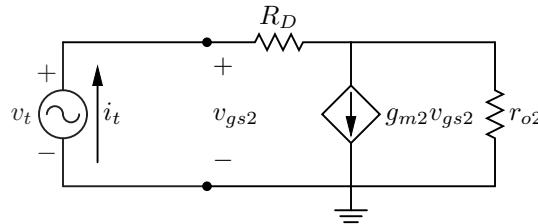(f) Let's draw a small-signal model to find the equivalent resistance seen looking up from the output.



$$i_t = g_{m2}v_{gs2} + \frac{v_t - i_t R_D}{r_{o2}}$$

$$v_{gs2} = v_t$$

$$i_t = g_{m2}v_t + \frac{v_t - i_t R_D}{r_{o2}}$$

$$i_t \left(1 + \frac{R_D}{r_{o2}} \right) = v_t \left(g_{m2} + \frac{1}{r_{o2}} \right)$$

$$\frac{v_t}{i_t} = \frac{1 + \frac{R_D}{r_{o2}}}{g_{m2} + \frac{1}{r_{o2}}} = \frac{r_{o2} + R_D}{1 + g_{m2}r_{o2}}$$

$$A_v = \boxed{-g_{m1} \left(r_{o1} \parallel \frac{r_{o2} + R_D}{1 + g_{m2}r_{o2}} \right)}$$

7.30 (a) Assume M_1 is operating in saturation.

$$I_D = 1 \text{ mA}$$

$$I_D R_S = 200 \text{ mV}$$

$$R_S = 200 \Omega$$

$$\begin{aligned} A_v &= -\frac{R_D}{\frac{1}{g_m} + R_S} \\ &= -\frac{R_D}{\frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} + R_S} \\ &= -4 \end{aligned}$$

$$\frac{W}{L} = \boxed{1000}$$

$$V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = 0.5 \text{ V}$$

$$V_{DS} = V_{DD} - I_D R_D - I_D R_S$$

$= 0.6 \text{ V} > V_{GS} - V_{TH}$, verifying that M_1 is in saturation

Yes, the transistor operates in saturation.

(b) Assume M_1 is operating in saturation.

$$\frac{W}{L} = \frac{50}{0.18}$$

$$R_S = 200 \Omega$$

$$\begin{aligned} A_v &= -\frac{R_D}{\frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} + R_S} \\ &= -4 \end{aligned}$$

$$R_D = \boxed{1.179 \text{ k}\Omega}$$


$$V_{GS} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} = 0.590 \text{ V}$$

$$V_{DS} = V_{DD} - I_D R_D - I_D R_S$$

$= 0.421 \text{ V} > V_{GS} - V_{TH}$, verifying that M_1 is in saturation

Yes, the transistor operates in saturation.

(31) The small signal model is:

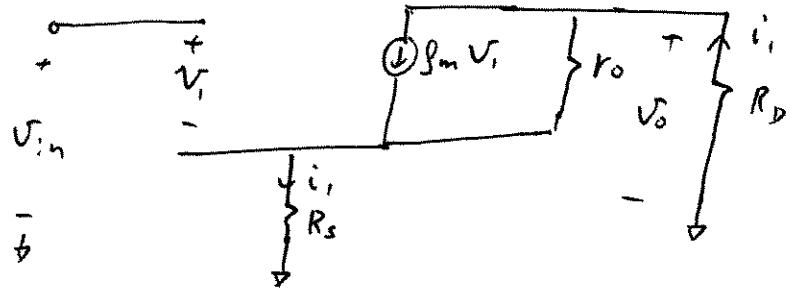

$$V_o = -i_1 R_D \quad \text{--- (1)}$$

$$i_1 = f_m V_i + \frac{V_o - V_i}{r_o}$$

$$= \frac{(f_m r_o - 1)V_i + V_o}{r_o}$$

$$i_1 \approx f_m V_i + \frac{V_o}{r_o}$$

$$\therefore -\frac{V_o}{R_D} = f_m V_i + \frac{V_o}{r_o} \quad \text{--- (2)}$$

$$V_{in} = V_i + i_1 R_s$$

$$\therefore V_i = V_{in} + \frac{V_o}{R_D} R_s \quad \text{--- (3)}$$

(2) combines with (3):


$$-\frac{V_o}{R_D} = f_m V_{in} + f_m V_o \frac{R_s}{R_D} + \frac{V_o}{r_o}$$

$$-\frac{V_o}{R_D} \left[\frac{1}{R_D} + f_m \frac{R_s}{R_D} + \frac{1}{r_o} \right] = f_m V_{in}$$

$$\therefore \text{Volt. gain} = \frac{V_o}{V_{in}} = - \left[\frac{f_m}{r_o + f_m R_s R_o + R_D} \right] (r_o R_D) //$$

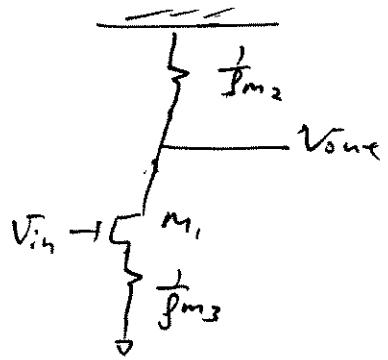(32). a) Equivalent circuit is:

$$\therefore A_v = - \frac{\frac{1}{g_{m_2}}}{\frac{1}{g_{m_1}} + \frac{1}{g_{m_3}}} //$$




b) Similar to Prob. 28(f),

Equivalent circuit is:

From Prob. 28(f),


$$Z_L = \frac{1}{g_{m_2}} \quad (\text{as } R_o \rightarrow \infty)$$
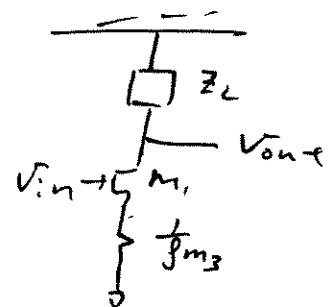
$$\therefore A_v = - \frac{\frac{1}{g_{m_2}}}{\frac{1}{g_{m_1}} + \frac{1}{g_{m_3}}} //$$



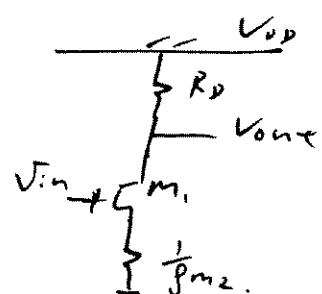
c) Equivalent circuit is:

$$\therefore A_v = - \frac{R_D}{\frac{1}{g_{m_1}} + \frac{1}{g_{m_2}}} //$$



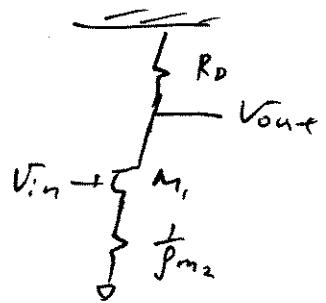
(d) Equivalent circuit is

$$A_v = - \frac{R_D}{\frac{1}{g_{m_1}} + \frac{1}{g_{m_2}}} //$$



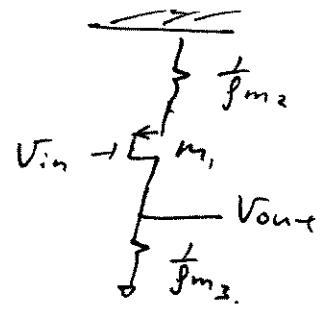(e) Equivalent circuit is

$$A_v = \frac{\frac{1}{g_{m_3}}}{\frac{1}{g_{m_1}} + \frac{1}{g_{m_2}}} //$$



(33) a) From Eq. (7.71),

$$R_{out} = (1 + f_{m_1} r_{o_1}) \cancel{\frac{f}{f_{m_2}}} + r_{o_1} //$$

b) From Eq. (7.71),

$$R_{out} = (1 + f_{m_1} r_{o_1}) \cancel{\frac{f}{f_{m_2}}} + r_{o_1} //$$

c) From Eq. (7.71),

$$R_{out} = (1 + f_{m_2} r_{o_2}) (r_{o_1} // \cancel{\frac{f}{f_{m_3}}}) + r_{o_2} //$$

d) From Eq. (7.71),

$$R_{out} = (1 + f_{m_1} r_{o_1}) (r_{o_2} // \cancel{\frac{f}{f_{m_3}}}) + r_{o_1} //$$

(34) To find $(\frac{w}{L})$

$$10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{w}{L} \right) (1 - 0.4)^2 \times \\ (1 + 0.1 V_{DS})$$

$$\text{where } V_{DS} = 1.8 - 1k\Omega \times 1mA \\ = 0.8V,$$

$$\therefore \left(\frac{w}{L} \right) \approx 25.7 //$$

$$\text{Voltage gain, } (A_v) = - f_m \cdot (r_{o1} // R_D)$$

$$f_m = \sqrt{2(200 \times 10^{-6}) / (25.7 \times 10^{-3}) \times (1 + 0.1 \times 0.8)} \\ = 3.33 \text{ mS.}$$

$$r_{o1} = \frac{1}{0.1 \times 10^{-3}} \\ = 10k\Omega.$$

$$\therefore A_v = (-3.33 \times 10^{-3}) / (10k\Omega // 1k\Omega) \\ = -3.03 //$$

(35) with $\lambda = 0$,

$$10^{-3} = \frac{1}{2} (200 \times 10^{-6}) \left(\frac{w}{c} \right) (1 - 0.4)^2$$

$$\therefore \left(\frac{w}{c} \right) \approx 27.8 //$$


$$Av = -f_m R_o$$

$$= -\sqrt{2(200 \times 10^{-6})(27.8) \times 10^{-3}} \times 1000$$

$$= -3.33 //$$

Without R_o , gain increases due mainly to increase in load resistance.

(36) The small-signal circuit is:

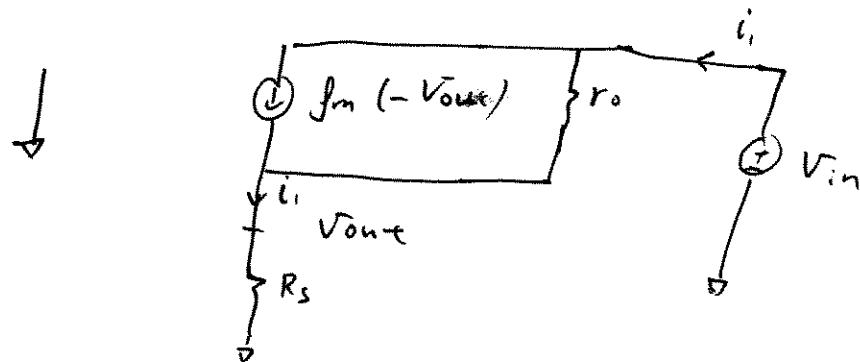

$$i_i = \frac{V_{out}}{R_s} \quad \text{--- (1)}$$

$$i_i = f_m (-V_{out}) + \frac{V_{in} - V_{out}}{r_o} \quad \text{--- (2)}$$

$$\therefore \frac{V_{out}}{R_s} = -f_m V_{out} + \frac{V_{in}}{r_o} - \frac{V_{out}}{r_o}$$

$$V_{out} \left(\frac{1}{R_s} + f_m + \frac{1}{r_o} \right) = \frac{V_{in}}{r_o}$$

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \frac{1}{r_o} \left(\frac{R_s r_o}{r_o + f_m r_o R_s + R_s} \right) \\ &= \frac{R_s}{f_m r_o R_s + r_o + R_s} \end{aligned}$$

Since $(f_m r_o R_s + r_o) > 0$, the voltage gain < 1 .

This is expected: Any variation in V_{in} causes minimal change in the bias current.

$\because V_{out}$ is determined largely by the amount of bias current ($\because V_{out}$ is set by V_{in})

\therefore There is almost no variation in V_{out} . (i.e. $\frac{V_{out}}{V_{in}} \ll 1$)

$$37) a) |Voltage gain| = f_m R_D$$

$$= 5$$

$$\therefore f_m = \frac{5}{500}$$

$$= 10 \text{ mS.}$$

$$= \sqrt{2(200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 10^{-3}}$$

$$\therefore \frac{W}{L} = 250 //$$

$$b) V_D = 1.8 - 500 \times 10^{-3}$$

$$= 1.3 \text{ V}$$

$$\text{To obtain } V_{DS} \geq V_{GS} - V_{TH} + 0.2,$$

$$V_D \geq V_G - 0.2$$

$$\therefore V_G \leq 1.5$$

$$\text{Also, } I_{R_1+R_2} = 0.1 \times 10^{-3} \text{ A.}$$

$$\therefore R_1 + R_2 = \frac{1.8}{0.1 \times 10^{-3}}$$

$$= 18 \text{ k}\Omega.$$

$$\text{choose } R_2 = 15 \text{ k}\Omega \quad \& \quad R_1 = 3 \text{ k}\Omega$$

c) With twice of (w/l), M_1 will go further away from triode. As (w/l) doubles, & I_{bias} is fixed by the current source, V_{ds} is forced to decrease (so M_1 will have same I_{DS}). Thus, $(V_{ds} - V_{T4})$ decreases, and V_{ds} can be allowed to drop more before M_1 goes into triode.

Gain will be increased by $\sqrt{2}$, because gain $\propto f_m$, and $f_m \propto \sqrt{w/l}$.

(38) a) $V_G = 1.8V$.

$$\therefore V_{D, \min} = 1.8 - 0.4 \quad (\text{for } M_1 \text{ stays in saturation}) \\ = 1.4V$$

$$\therefore R_{s, \max} = \frac{1.4V}{1mA} \\ = 1.4k\Omega //$$

b) |Voltage gain| = $f_m R_D$
= 5.

$$\therefore f_m = \frac{5}{R_D} \\ = 3.57 \text{ ms}^{-1}$$

$$= \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{W}{L}\right) \times 10^{-3}}$$

$$\therefore \left(\frac{W}{L}\right) = 31.9 //$$

(39) To get $R_{in} = 50\Omega$,

$$\frac{1}{f_m} = 50\Omega$$

$$\therefore f_m = 20 \text{ mS.}$$

$$\text{volt gain (Av)} = f_m R_D$$

$$= 4,$$

$$\therefore R_D = \frac{4}{0.02}$$

$$R_D = 200 \Omega //$$

$$\therefore f_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{w}{L}\right) \times 0.5 \times 10^{-3}}$$

$$\therefore \left(\frac{w}{L}\right) = 2000 //$$

7.42 (a)

$$R_{out} = R_D = 500 \Omega$$

$$V_G = V_{DD}$$

$V_D > V_G - V_{TH}$ (in order for M_1 to operate in saturation)

$$V_{DD} - I_D R_D > V_{DD} - V_{TH}$$

$$I_D < \boxed{0.8 \text{ mA}}$$

(b)

$$I_D = 0.8 \text{ mA}$$

$$\begin{aligned} R_{in} &= \frac{1}{g_m} \\ &= \frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} \\ &= 50 \Omega \end{aligned}$$

$$\frac{W}{L} = \boxed{1250}$$

(c)

$$A_v = g_m R_D$$

$$g_m = \frac{1}{50} \text{ S}$$

$$R_D = 500 \Omega$$

$$A_v = \boxed{10}$$

7.43 (a)

$$\begin{aligned}I_D &= I_1 = 1 \text{ mA} \\V_G &= V_{DD} \\V_D &= V_G - V_{TH} + 100 \text{ mV} \\V_{DD} - I_D R_D &= V_G - V_{TH} + 100 \text{ mV} \\R_D &= \boxed{300 \Omega}\end{aligned}$$

(b)


$$\begin{aligned}R_D &= 300 \Omega \\A_v &= g_m R_D \\&= \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D R_D} \\&= 5 \\\frac{W}{L} &= \boxed{694.4}\end{aligned}$$

7.44 For this problem, recall that looking into the drain of a transistor with a grounded gate and source we see a resistance of r_o , and looking into either terminal of a diode-connected transistor we see a resistance of $\frac{1}{g_m} \parallel r_o$.

(a) Referring to Eq. (7.109) with $R_D = \frac{1}{g_{m2}}$ and $g_m = g_{m1}$, we have

$$A_v = \boxed{\frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + R_S}}$$

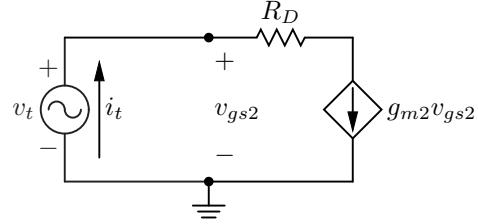(b) Let's draw a small-signal model to find the equivalent resistance seen looking up from the output.



$$i_t = g_{m2}v_{gs2}$$

$$v_{gs2} = v_t$$

$$i_t = g_{m2}v_t$$

$$\frac{v_t}{i_t} = \frac{1}{g_{m2}}$$

$$A_v = \boxed{\frac{g_{m1}}{g_{m2}}}$$

(c) Referring to Eq. (7.119) with $R_D = \frac{1}{g_{m2}}$, $R_3 = R_1$, and $g_m = g_{m1}$, we have

$$A_v = \boxed{\frac{R_1 \parallel \frac{1}{g_{m1}} g_{m1}}{R_S + R_1 \parallel \frac{1}{g_{m1}} g_{m2}}}$$

(d)

$$A_v = \boxed{g_{m1} \left(R_D + \frac{1}{g_{m2}} \parallel r_{o3} \right)}$$

(e)

$$A_v = \boxed{g_{m1} \left(R_D + \frac{1}{g_{m2}} \right)}$$

7.45 (a)

$$\begin{aligned}
 \frac{v_X}{v_{in}} &= -g_{m1} \left(R_{D1} \parallel \frac{1}{g_{m2}} \right) \\
 \frac{v_{out}}{v_X} &= g_{m2} R_{D2} \\
 \frac{v_{out}}{v_{in}} &= \frac{v_X}{v_{in}} \frac{v_{out}}{v_X} \\
 &= \boxed{-g_{m1}g_{m2}R_{D2} \left(R_{D1} \parallel \frac{1}{g_{m2}} \right)}
 \end{aligned}$$

(b)

$$\lim_{R_{D1} \rightarrow \infty} -g_{m1}g_{m2}R_{D2} \left(R_{D1} \parallel \frac{1}{g_{m2}} \right) = \boxed{-g_{m1}R_{D2}}$$

This makes sense because the common-source stage acts as a transconductance amplifier with a transconductance of g_{m1} . The common-gate stage acts as a current buffer with a current gain of 1. Thus, the current $g_{m1}v_{in}$ flows through R_{D2} , meaning $v_{out} = -g_{m1}v_{in}R_{D2}$, so that $\frac{v_{out}}{v_{in}} = -g_{m1}R_{D2}$.

This type of amplifier (with $R_{D1} = \infty$) is known as a cascode and will be studied in detail in Chapter 9.

7.40

$$I_D = 0.5 \text{ mA}$$

$$\begin{aligned} R_{in} &= \frac{1}{g_m} \\ &= \frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} \\ &= 50 \Omega \end{aligned}$$

$$\frac{W}{L} = \boxed{2000}$$

$V_D > V_G - V_{TH}$ (in order for M_1 to operate in saturation)


$$V_{DD} - I_D R_D > V_b - V_{TH}$$

$$R_D < 2.4 \text{ k}\Omega$$

Since $|A_v| \propto R_D$, we need to maximize R_D in order to maximize the gain. Thus, we should pick $R_D = \boxed{2.4 \text{ k}\Omega}$. This corresponds to a voltage gain of $A_v = -g_m R_D = -48$.


(41) Voltage gain (A_v) = $g_m R_{out}$,
 where g_m and R_{out} are the transconductance
 and output resistance of the circuit respectively.

To find g_m :

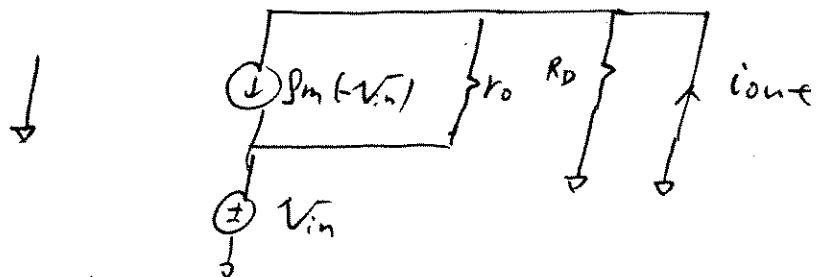

$$g_m = \frac{i_{out}}{V_{in}} = g_m + \frac{1}{r_o} \\ \approx g_m \quad (\because g_m r_o \gg 1)$$

To find R_{out} :

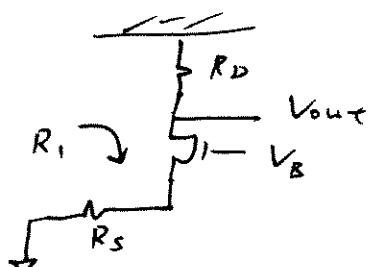

$$R_{out} = R_D // R_L \\ = R_D // [(1 + g_m r_o) R_s + r_o] \\ \text{(from Eq. (7.110))} \\ \approx R_D // (g_m r_o R_s + r_o) \quad (\because g_m r_o \gg 1) \\ = \frac{g_m r_o R_s R_D + r_o R_D}{R_D + g_m r_o R_s + r_o}$$

$$\therefore \text{Voltage gain} = f_m \left[\frac{f_m r_o R_D R_S + r_o R_D}{R_D + f_m r_o R_S + r_o} \right] \approx$$

7.42 (a)

$$R_{out} = R_D = 500 \Omega$$

$$V_G = V_{DD}$$

$V_D > V_G - V_{TH}$ (in order for M_1 to operate in saturation)

$$V_{DD} - I_D R_D > V_{DD} - V_{TH}$$

$$I_D < \boxed{0.8 \text{ mA}}$$

(b)

$$I_D = 0.8 \text{ mA}$$

$$\begin{aligned} R_{in} &= \frac{1}{g_m} \\ &= \frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} \\ &= 50 \Omega \end{aligned}$$

$$\frac{W}{L} = \boxed{1250}$$

(c)

$$A_v = g_m R_D$$

$$g_m = \frac{1}{50} \text{ S}$$

$$R_D = 500 \Omega$$

$$A_v = \boxed{10}$$

7.43 (a)

$$\begin{aligned}I_D &= I_1 = 1 \text{ mA} \\V_G &= V_{DD} \\V_D &= V_G - V_{TH} + 100 \text{ mV} \\V_{DD} - I_D R_D &= V_G - V_{TH} + 100 \text{ mV} \\R_D &= \boxed{300 \Omega}\end{aligned}$$

(b)


$$\begin{aligned}R_D &= 300 \Omega \\A_v &= g_m R_D \\&= \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D R_D} \\&= 5 \\\frac{W}{L} &= \boxed{694.4}\end{aligned}$$

7.44 For this problem, recall that looking into the drain of a transistor with a grounded gate and source we see a resistance of r_o , and looking into either terminal of a diode-connected transistor we see a resistance of $\frac{1}{g_m} \parallel r_o$.

(a) Referring to Eq. (7.109) with $R_D = \frac{1}{g_{m2}}$ and $g_m = g_{m1}$, we have

$$A_v = \boxed{\frac{\frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + R_S}}$$

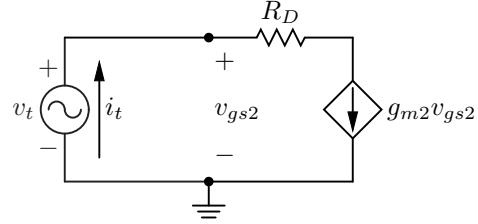(b) Let's draw a small-signal model to find the equivalent resistance seen looking up from the output.



$$i_t = g_{m2}v_{gs2}$$

$$v_{gs2} = v_t$$

$$i_t = g_{m2}v_t$$

$$\frac{v_t}{i_t} = \frac{1}{g_{m2}}$$

$$A_v = \boxed{\frac{g_{m1}}{g_{m2}}}$$

(c) Referring to Eq. (7.119) with $R_D = \frac{1}{g_{m2}}$, $R_3 = R_1$, and $g_m = g_{m1}$, we have

$$A_v = \boxed{\frac{R_1 \parallel \frac{1}{g_{m1}} g_{m1}}{R_S + R_1 \parallel \frac{1}{g_{m1}} g_{m2}}}$$

(d)

$$A_v = \boxed{g_{m1} \left(R_D + \frac{1}{g_{m2}} \parallel r_{o3} \right)}$$

(e)

$$A_v = \boxed{g_{m1} \left(R_D + \frac{1}{g_{m2}} \right)}$$

7.45 (a)

$$\begin{aligned}
 \frac{v_X}{v_{in}} &= -g_{m1} \left(R_{D1} \parallel \frac{1}{g_{m2}} \right) \\
 \frac{v_{out}}{v_X} &= g_{m2} R_{D2} \\
 \frac{v_{out}}{v_{in}} &= \frac{v_X}{v_{in}} \frac{v_{out}}{v_X} \\
 &= \boxed{-g_{m1}g_{m2}R_{D2} \left(R_{D1} \parallel \frac{1}{g_{m2}} \right)}
 \end{aligned}$$

(b)

$$\lim_{R_{D1} \rightarrow \infty} -g_{m1}g_{m2}R_{D2} \left(R_{D1} \parallel \frac{1}{g_{m2}} \right) = \boxed{-g_{m1}R_{D2}}$$

This makes sense because the common-source stage acts as a transconductance amplifier with a transconductance of g_{m1} . The common-gate stage acts as a current buffer with a current gain of 1. Thus, the current $g_{m1}v_{in}$ flows through R_{D2} , meaning $v_{out} = -g_{m1}v_{in}R_{D2}$, so that $\frac{v_{out}}{v_{in}} = -g_{m1}R_{D2}$.

This type of amplifier (with $R_{D1} = \infty$) is known as a cascode and will be studied in detail in Chapter 9.

$$(46) \quad \frac{V_x}{V_{in}} = \left(R_{D1} \parallel \frac{1}{f_{m2}} \right) f_{m1}$$


$$\frac{V_{out}}{V_x} = f_{m2} R_{D2}$$

$$\therefore \frac{V_{out}}{V_{in}} = f_{m1} f_{m2} R_{D2} \left(R_{D1} \parallel \frac{1}{f_{m2}} \right) \cancel{\parallel}$$

Similar to prob. (45), voltage gain approaches that of cascode stage as R_{D1} approaches infinity. The gain is $f_{m1} R_{D2}$.

(47) with $\lambda=0$, M_i appears as a diode-connected device.

i. the circuit becomes :

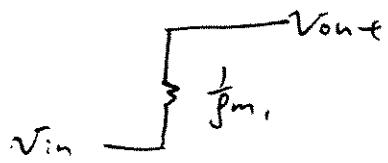


i.e. $\frac{V_{out}}{V_{in}} = \frac{1}{g_{m_i}}$

This is not a common-gate amplifier,
^(CG)

because the gate is not fixed. (ie. gate
is not at an "a.c. ground")

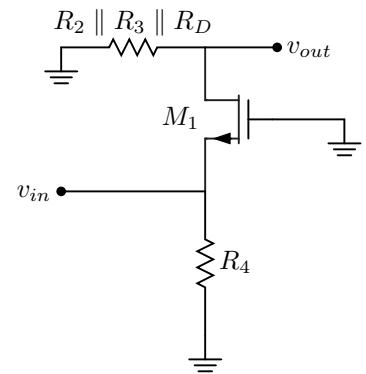7.48 For small-signal analysis, we can short the capacitors, producing the following equivalent circuit.



$$A_v = \boxed{g_m (R_2 \parallel R_3 \parallel R_D)}$$

7.49

$$V_{GS} = V_{DS}$$

$$V_{GS} = V_{DD} - I_D R_S = V_{DD} - \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{GS}) R_S$$

$$V_{GS} = V_{DS} = 0.7036 \text{ V}$$

$$I_D = 1.096 \text{ mA}$$

$$A_v = \frac{r_o \parallel R_S}{\frac{1}{g_m} + r_o \parallel R_S}$$

$$g_m = \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = 6.981 \text{ mS}$$

$$r_o = \frac{1}{\lambda I_D} = 9.121 \text{ k}\Omega$$

$$A_v = \boxed{0.8628}$$

7.50

$$\begin{aligned} A_v &= \frac{R_S}{\frac{1}{g_m} + R_S} \\ &= \frac{R_S}{\frac{1}{\mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})} + R_S} \\ &= 0.8 \end{aligned}$$

$$V_{GS} = 0.64 \text{ V}$$

$$\begin{aligned} I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 \\ &= 960 \text{ } \mu\text{A} \end{aligned}$$

$$\begin{aligned} V_G &= V_{GS} + V_S = V_{GS} + I_D R_S \\ &= \boxed{1.12 \text{ V}} \end{aligned}$$

(51)

$$A_v = \frac{R_s}{\frac{1}{f_m} + R_s}$$

$$= 0.8$$

$$0.8 = \frac{500}{\frac{1}{f_m} + 500}$$

$$\therefore f_m = 8 \text{ mS.}$$

$$\therefore I_{ds} = \frac{1}{2} \beta (V_{gs} - V_t)^2,$$

$$\text{where } \beta = \frac{w}{L} M_n C_{ox}$$

$$\text{and } f_m = \beta (V_{gs} - V_t).$$

$$\therefore I_{ds} = \frac{1}{2} f_m (V_{gs} - V_t)$$

$$= \frac{1}{2} f_m (1.8 - I_{ds}(500) - 0.4)$$

$$I_{ds} = 4 \times 10^{-3} (1.4 - 500 I_{ds})$$

$$\therefore I_{ds} = 1.87 \text{ mA.}$$

$$\therefore f_m = \sqrt{2(200 \times 10^{-6}) \frac{w}{L} \times 1.87 \times 10^{-3}}$$

$$\therefore \frac{w}{L} \approx 85.7 //$$

(52). To get $R_{out} = 100 \Omega$,

$$\frac{1}{f_m} = 100$$

$$\therefore f_m = 10 \text{ mS.}$$

$$\therefore I_{ds} = \frac{1}{2} \beta (V_{GS} - V_{TH})^2$$

$$\text{where } \beta = M_n C_o x \frac{w}{L}$$

$$\text{and } f_m = \beta (V_{GS} - V_{TH})$$

$$\therefore I_{ds} = \frac{1}{2} f_m (V_{GS} - V_{TH})$$

$$= \frac{1}{2} (10 \times 10^{-3})(0.9 - 0.4)$$

$$\therefore I_{ds} = 2.5 \text{ mA.}$$

$$\therefore f_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{w}{L} \right) (2.5 \times 10^{-3})}$$

$$\therefore \left(\frac{w}{L} \right) = 100 \quad \checkmark$$

(53) To get $R_{out} = 50\Omega$,

$$\frac{1}{f_m} = 50\Omega$$

$$\therefore f_m = 20 \text{ mS.}$$

$$\begin{aligned}\text{Power (P)} &= 1.8 \times I_{ds} \\ &= 2 \times 10^{-3} \text{ W.}\end{aligned}$$

$$\therefore I_{ds} = 1.11 \text{ mA.}$$

$$\therefore f_m = \sqrt{2 \times (200 \times 10^{-6}) / \left(\frac{W}{L}\right) (1.11 \text{ mA})}$$

$$\therefore \frac{W}{L} = 900 //$$

$$\textcircled{54} \quad A_v = \frac{R_L}{\frac{1}{f_m} + R_L}$$

$$\therefore 0.8 = \frac{50}{\frac{1}{f_m} + 50}$$

$$f_m = 80 \text{ mS}$$

$$\text{Power (P)} = 1.8 \times I_{DS}$$
$$= 3 \text{ mW}$$

$$\therefore I_{DS} = 1.67 \text{ mA}$$

$$f_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{w}{c}\right) (1.67 \times 10^{-3})}$$

$$\therefore \left(\frac{w}{c}\right) = \cancel{9600}$$

7.55 For this problem, recall that looking into the drain of a transistor with a grounded gate and source we see a resistance of r_o , and looking into either terminal of a diode-connected transistor we see a resistance of $\frac{1}{g_m} \parallel r_o$.

(a)

$$A_v = \boxed{\frac{r_{o1} \parallel (R_S + r_{o2})}{\frac{1}{g_{m1}} + r_{o1} \parallel (R_S + r_{o2})}}$$


(b) Looking down from the output we see an equivalent resistance of $r_{o2} + (1 + g_{m2}r_{o2}) R_S$ by Eq. (7.110).

$$A_v = \boxed{\frac{r_{o1} \parallel [r_{o2} + (1 + g_{m2}r_{o2}) R_S]}{\frac{1}{g_{m1}} + r_{o1} \parallel [r_{o2} + (1 + g_{m2}r_{o2}) R_S]}}$$

(c)

$$A_v = \boxed{\frac{r_{o1} \parallel \frac{1}{g_{m2}}}{\frac{1}{g_{m1}} + r_{o1} \parallel \frac{1}{g_{m2}}}}$$

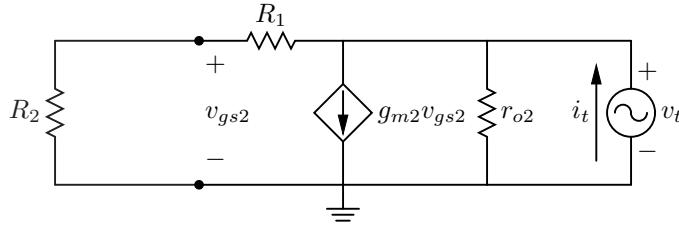(d) Let's draw a small-signal model to find the equivalent resistance seen looking down from the output.



$$i_t = \frac{v_t}{R_1 + R_2} + g_{m2}v_{gs2} + \frac{v_t}{r_{o2}}$$

$$v_{gs2} = \frac{R_2}{R_1 + R_2}v_t$$

$$i_t = \frac{v_t}{R_1 + R_2} + g_{m2}\frac{R_2}{R_1 + R_2}v_t + \frac{v_t}{r_{o2}}$$

$$i_t = v_t \left(\frac{1}{R_1 + R_2} + \frac{g_{m2}R_2}{R_1 + R_2} + \frac{1}{r_{o2}} \right)$$

$$\frac{v_t}{i_t} = (R_1 + R_2) \parallel \left(\frac{R_1 + R_2}{g_{m2}R_2} \right) \parallel r_{o2}$$

$$A_v = \boxed{\frac{r_{o1} \parallel (R_1 + R_2) \parallel \left(\frac{R_1 + R_2}{g_{m2}R_2} \right) \parallel r_{o2}}{\frac{1}{g_{m1}} + r_{o1} \parallel (R_1 + R_2) \parallel \left(\frac{R_1 + R_2}{g_{m2}R_2} \right) \parallel r_{o2}}}$$

(e)

$$A_v = \boxed{\frac{r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m1}}}{\frac{1}{g_{m2}} + r_{o2} \parallel r_{o3} \parallel \frac{1}{g_{m1}}}}$$

(f) Looking up from the output we see an equivalent resistance of $r_{o2} + (1 + g_{m2}r_{o2})r_{o3}$ by Eq. (7.110).

$$A_v = \boxed{\frac{r_{o1} \parallel [r_{o2} + (1 + g_{m2}r_{o2})r_{o3}]}{\frac{1}{g_{m1}} + r_{o1} \parallel [r_{o2} + (1 + g_{m2}r_{o2})r_{o3}]}}$$

$$(56) \quad \frac{V_x}{V_{in}} = \frac{\frac{1}{f_{m_2}}}{\frac{1}{f_{m_1}} + \frac{1}{f_{m_2}}}.$$

$$\frac{V_{out}}{V_x} = f_{m_2} R_D$$

$$\therefore \frac{V_{out}}{V_{in}} = \frac{R_D}{\frac{1}{f_{m_1}} + \frac{1}{f_{m_2}}} //$$

b) if $f_{m_1} = f_{m_2}$,

$$\frac{V_{out}}{V_{in}} = \frac{f_{m_1} R_D}{2} //$$

(52)

$$\therefore R_{out} = 1k\Omega.$$

$$\therefore R_D = 1k\Omega.$$

$$\therefore A_V = 5$$
$$= f_m, R_D$$

$$\therefore f_m, (1000) = 5$$
$$f_m = 5 \text{ mS.}$$

$\therefore M_1$ is 00 mV away from triode,

$$V_D = (V_a - V_{TH}) + 0.1.$$

$$V_D = (1.8 - 0.4) + 0.1$$

$$V_D = 1.5 \text{ V}$$

$$\therefore I_{DS} = \frac{1.8 - 1.5}{R_D} = \frac{0.3}{R_D}$$
$$= 0.3 \text{ mA}$$

$$\therefore f_m = \sqrt{2 \times (200 \times 10^{-6}) \left(\frac{w}{l}\right) I_{DS}}$$

$$\therefore \left(\frac{w}{l}\right) \approx 208$$

$$\therefore R_D = 1k\Omega, R_s = 10k\Omega, \left(\frac{w}{l}\right) = 208$$

7.58

$$P = V_{DD}I_D = 2 \text{ mW}$$

$$I_D = 1.11 \text{ mA}$$

$$R_D I_D = 1 \text{ V}$$

$$R_D = 900 \Omega$$

$$A_v = -g_m R_D$$

$$= -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D R_D}$$

$$= -5$$

$$\frac{W}{L} = \boxed{69.44}$$

(59)

$$|A_v| = f_m R_L$$

\therefore To achieve maximum gain, use maximum R_L .

i.e. set $R_D = 500 \Omega$.

For maximum f_m , use maximum I_{DS} .

(... while keeping M_i in saturation),

$$\text{i.e. } V_D \geq V_S - V_{TH}$$

$$1.8 - (I_{DS})(500) \geq 1.8 - 0.4 ,$$

$$\therefore I_{DS} \leq \frac{0.4}{500}$$

$$I_{DS, \max} = 0.8 \text{ mA.}$$

Note! Setting a large R_D in this case would force $I_{DS, \max}$ to be lower (in order to keep M_i in saturation).

But since $A_v \propto R_D$, while $A_v \propto \sqrt{I_{DS}}$, sacrificing I_{DS} to get higher R_D would yield a higher gain.

7.60 Let's let R_1 and R_2 consume exactly 5 % of the power budget (which means the branch containing R_D , M_1 , and R_S will consume 95 % of the power budget). Let's also assume $V_{ov} = V_{GS} - V_{TH} = 300$ mV exactly.

$$I_D V_{DD} = 0.95(2 \text{ mW})$$

$$I_D = 1.056 \text{ mA}$$

$$I_D R_S = 200 \text{ mV}$$

$$R_S = \boxed{189.5 \Omega}$$

$$V_{ov} = V_{GS} - V_{TH} = 300 \text{ mV}$$

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_{ov}^2$$

$$\frac{W}{L} = \boxed{117.3}$$

$$\begin{aligned} A_v &= -\frac{R_D}{\frac{1}{g_m} + R_S} \\ &= -\frac{R_D}{\frac{1}{2\mu_n C_{ox} \frac{W}{L} I_D} + R_S} \\ &= -4 \end{aligned}$$

$$R_D = \boxed{1.326 \text{ k}\Omega}$$

$$\frac{V_{DD}^2}{R_1 + R_2} = 0.05(2 \text{ mW})$$

$$R_1 + R_2 = \frac{V_{DD}^2}{0.1 \text{ mW}}$$

$$V_G = V_{GS} + I_D R_S = V_{ov} + V_{TH} + I_D R_S = 0.9 \text{ V}$$

$$\begin{aligned} V_G &= \frac{R_2}{R_1 + R_2} V_{DD} \\ &= \frac{R_2}{\frac{V_{DD}^2}{0.1 \text{ mW}}} = 0.9 \text{ V} \end{aligned}$$

$$R_2 = \boxed{29.16 \text{ k}\Omega}$$

$$R_1 = \boxed{3.24 \text{ k}\Omega}$$

7.61 Let's let R_1 and R_2 consume exactly 5 % of the power budget (which means the branch containing R_D , M_1 , and R_S will consume 95 % of the power budget).

$$R_D = 200 \Omega$$

$$I_D V_{DD} = 0.95(6 \text{ mW})$$

$$I_D = 3.167 \text{ mA}$$

$$I_D R_S = V_{ov} = V_{GS} - V_{TH}$$

$$R_S = \frac{V_{ov}}{I_D}$$

$$g_m = \frac{2I_D}{V_{ov}}$$

$$A_v = -\frac{R_D}{\frac{1}{g_m} + R_S}$$

$$= -\frac{R_D}{\frac{V_{ov}}{2I_D} + \frac{V_{ov}}{I_D}}$$

$$= -5$$

$$V_{ov} = 84.44 \text{ mV}$$

$$R_S = \boxed{26.67 \Omega}$$

$$\frac{W}{L} = \frac{2I_D}{\mu_n C_{ox} V_{ov}^2} = \boxed{4441}$$

$$\frac{V_{DD}^2}{R_1 + R_2} = 0.05(6 \text{ mW})$$

$$R_1 + R_2 = \frac{V_{DD}^2}{0.3 \text{ mW}}$$

$$V_G = V_{GS} + I_D R_S = V_{ov} + V_{TH} + I_D R_S = 0.5689 \text{ V}$$

$$V_G = \frac{R_2}{R_1 + R_2} V_{DD}$$

$$= \frac{R_2}{\frac{V_{DD}^2}{0.3 \text{ mW}}} = 0.5689 \text{ V}$$

$$R_2 = \boxed{6.144 \text{ k}\Omega}$$

$$R_1 = \boxed{4.656 \text{ k}\Omega}$$

7.62

$$\begin{aligned}
R_{in} &= R_1 = \boxed{20 \text{ k}\Omega} \\
P &= V_{DD} I_D = 2 \text{ mW} \\
I_D &= 1.11 \text{ mA} \\
V_{DS} &= V_{GS} - V_{TH} + 200 \text{ mV} \\
V_{DD} - I_D R_D &= V_{DD} - V_{TH} + 200 \text{ mV} \\
R_D &= 180 \text{ }\Omega \\
A_v &= -g_m R_D \\
&= -\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D R_D} \\
&= -6 \\
\frac{W}{L} &= \boxed{2500} \\
V_{GS} &= V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \frac{W}{L}}} \\
&= 0.467 \text{ V} \\
V_{GS} &= V_{DD} - I_D R_S \\
R_S &= \boxed{1.2 \text{ k}\Omega} \\
\frac{1}{2\pi f C_1} &\ll R_1 \\
\frac{1}{2\pi f C_1} &= \frac{1}{10} R_1 \\
f &= 1 \text{ MHz} \\
C_1 &= \boxed{79.6 \text{ pF}} \\
\frac{1}{2\pi f C_S} \parallel R_S &\ll \frac{1}{g_m} \\
\frac{1}{2\pi f C_S} &= \frac{1}{10} \frac{1}{g_m} \\
g_m &= \sqrt{2\mu_n C_{ox} \frac{W}{L} I_D} = 33.33 \text{ mS} \\
C_S &= \boxed{52.9 \text{ nF}}
\end{aligned}$$

(63). Power (P) = 2mW .

$$\therefore I_{DS1} = |I_{DS2}| = \frac{2 \text{mW}}{1.8V} = 1.11 \text{mA.}$$

$$R_{O1} = R_{O2} = \frac{1}{2I_{DS}} \\ = \frac{1}{0.1 \times 1.11 \times 10^{-3}} \\ = 9000 \Omega.$$

$$\text{fain (Av)} = f_m, (R_{O1} // R_{O2}) = 20,$$

$$f_m, (\frac{9000}{2}) = 20.$$

$$\therefore f_m, = 4.44 \text{ mS.}$$

$$\text{Set } V_{GS1} \text{ (i.e. } V_{out}) = 1.2V$$

(which is $< 1.5V$)

$$\therefore V_{IN} = V_{GS1} \leq 1.2 + V_{TH}$$

(for M_1 to stay in saturation)

$$\text{Set } V_{GS1} = 1.2V$$

$$\therefore f_m, = M_n C_{ox} \left(\frac{w}{l} \right), (V_{GS1} - V_{TH})$$

$$\left(\frac{w}{l} \right)_1 = 27.75$$

For M_2 , $\therefore M_2$ must be in saturation
for $V_{out} \leq 1.5V$.

$$\therefore V_{DD} - V_B \leq V_{DD} - 1.5V + V_{TH}$$

$$\therefore V_B \geq 1.1V$$

$$\text{Set } V_B = 1.2V$$

$$|I_{DS2}| = \frac{1}{2} M_p C_{ox} \left(\frac{W}{L}\right)_2 \left(|V_{GS2}| - V_{TH} \right)^2 \\ (1 + \lambda |V_{DS2}|)$$

$$1.11 \times 10^{-3} = \frac{1}{2} \times 100 \times 10^{-6} \left(\frac{W}{L}\right)_2 (0.6 - 0.2)^2 \\ (1 + 0.1 \times (1.8 - 1.5))$$

(assuming $V_{out} = 1.5V$)

$$\therefore \left(\frac{W}{L}\right)_2 \approx 135$$

$$\therefore \left(\frac{W}{L}\right)_1 = 27.75 \quad \left(\frac{W}{L}\right)_2 = 135$$

$$V_{IN} = 1.2 \quad V_b = 1.1$$

$$I_{DS1} = I_{DS2} = 1.11 \text{ mA}$$

7.64 (a)

$$A_v = \boxed{-g_{m1} (r_{o1} \parallel R_G \parallel r_{o2})}$$

(b)

$$\begin{aligned}
P &= V_{DD} I_{D1} = 3 \text{ mW} \\
I_{D1} &= |I_{D2}| = 1.67 \text{ mA} \\
|V_{GS2}| &= |V_{DS2}| = V_{DS} = \frac{V_{DD}}{2} \\
|I_{D2}| &= \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)_2 (|V_{GS2}| - |V_{TH}|)^2 (1 + \lambda_p |V_{DS2}|) \\
\left(\frac{W}{L} \right)_2 &= \boxed{113} \\
A_v &= -g_{m1} (r_{o1} \parallel R_G \parallel r_{o2}) \\
R_G &= 10 (r_{o1} \parallel r_{o2}) \\
r_{o1} &= \frac{1}{\lambda_n I_{D1}} = 6 \text{ k}\Omega \\
r_{o2} &= \frac{1}{\lambda_p |I_{D2}|} = 3 \text{ k}\Omega \\
R_G &= 10 (r_{o1} \parallel r_{o2}) = \boxed{20 \text{ k}\Omega} \\
A_v &= -\sqrt{2\mu_n C_{ox} \left(\frac{W}{L} \right)_1 I_{D1} (r_{o1} \parallel R_G \parallel r_{o2})} \\
&= -15 \\
\left(\frac{W}{L} \right)_1 &= \boxed{102.1} \\
V_{IN} &= V_{GS1} = V_{TH} + \sqrt{\frac{2I_D}{\mu_n C_{ox} \left(\frac{W}{L} \right)_1 (1 + \lambda_n V_{DS1})}} \\
&= \boxed{0.787 \text{ V}}
\end{aligned}$$

(65) a) Impedance looking into drain of M₂

$$= (1 + g_{m_2} r_{o_2}) / R_s + r_{o_2}$$

$$= 10 r_o.$$

Assume $g_{m_2} r_{o_2} \gg 1$,

$$\therefore g_{m_2} r_{o_2} R_s + r_{o_2} \approx 10 r_o.$$

$$\therefore r_{o_1} = r_{o_2} \quad (\lambda_1 = \lambda_2 \text{ and } |I_{DS1}| = |I_{DS2}|)$$

$$\therefore g_{m_2} R_s + 1 = 10$$

$$g_{m_2} R_s = 9 \quad \text{--- (1)}$$

Given $V_B = 1V$,

Set $|V_{GS2}| = 0.6V$, (i.e. $V_{GS2} - V_{T4} = 0.2V$)

$$\therefore V_{S2} = 1.6V$$

$$\therefore V_{Rs} = 1.8V - 1.6V = 0.2V$$

\therefore Power = 2 mW

$$I_{DS1} = |I_{DS2}| = \frac{2 \text{ mW}}{1.8V} = 1.11 \text{ mA.}$$

$$\therefore R_s = \frac{V_{Rs}}{1.11 \times 10^{-3}} \approx 180 \Omega //$$

$$\text{From (1), } g_{m_2} = \frac{9}{180} = 50 \text{ mS.}$$

$$\therefore g_{m_2} = \left(\frac{W}{L}\right)_2 (100 \times 10^{-6}) (V_{GS2} - V_{T4})$$

$$\therefore \left(\frac{W}{L}\right)_2 = 2500 //$$

$$b). \text{ Gain } (\text{Av}) = f_{m_1} (r_o // 10r_{o_1})$$

$$30 = f_{m_1} (0.909 r_o)$$

$$r_o = \frac{1}{0.1 \times 1.11 \times 10^{-3}}$$

$$= 900 \Omega$$

$$\therefore f_{m_1} = 3.66 \text{ mS.}$$

$$\therefore f_{m_1} = \sqrt{2(\mu_n C_s)(\frac{w}{l})} \times I_{DS_1}$$

$$\therefore \left(\frac{w}{l}\right)_1 \approx 30.2$$

7.66

$$P = V_{DD} I_{D1} = 1 \text{ mW}$$

$$I_{D1} = |I_{D2}| = 556 \mu\text{A}$$

$$V_{ov1} = V_{GS1} - V_{TH} = \sqrt{2I_D} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 = 200 \text{ mV}$$

$$\left(\frac{W}{L} \right)_1 = \boxed{138.9}$$

$$A_v = -\frac{g_{m1}}{g_{m2}}$$

$$= -\frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L} \right)_1 I_{D1}}}{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L} \right)_2 |I_{D2}|}}$$

$$= -\sqrt{\frac{\left(\frac{W}{L} \right)_1}{\left(\frac{W}{L} \right)_2}}$$

$$= -4$$

$$\left(\frac{W}{L} \right)_2 = \boxed{8.68}$$

$$V_{IN} = V_{GS1} = V_{ov1} + V_{TH} = \boxed{0.6 \text{ V}}$$

7.67

$$P = V_{DD}I_D = 3 \text{ mW}$$

$$I_D = I_1 = \boxed{1.67 \text{ mA}}$$

$$R_{in} = \frac{1}{g_m} = \frac{1}{\sqrt{2\mu_n C_{ox} \frac{W}{L} I_D}} = 50 \Omega$$

$$\frac{W}{L} = \boxed{600}$$

$$A_v = g_m R_D = \frac{1}{50 \Omega} R_D = 5$$

$$R_D = \boxed{250 \Omega}$$

7.68

$$P = V_{DD}I_D = 2 \text{ mW}$$

$$I_D = 1.11 \text{ mA}$$

$$V_D = V_G - V_{TH} + 100 \text{ mV}$$

$$V_{DD} - I_D R_D = V_G - V_{TH} + 100 \text{ mV}$$

$$V_G = V_{DD}$$

$$A_v = g_m R_D = \frac{2I_D}{V_{GS} - V_{TH}} R_D = 4$$

$$R_D = A_v \frac{V_{GS} - V_{TH}}{2I_D}$$

$$V_{DD} - I_D A_v \frac{V_{GS} - V_{TH}}{2I_D} = V_{DD} - V_{TH} + 100 \text{ mV}$$

$$V_{GS} = 0.55 \text{ V}$$

$$R_D = \boxed{270 \Omega}$$

$$V_S = V_{DD} - V_{GS} = I_D R_S$$

$$R_S = \boxed{1.125 \text{ k}\Omega}$$

$$\frac{W}{L} = \frac{2I_D}{\mu_n C_{ox} (V_{GS} - V_{TH})^2} = \boxed{493.8}$$

(69)

$$\text{Power} = 5 \text{ mW}$$

$$\therefore I_{DS} = \frac{5 \times 10^{-3}}{1.8} = 2.78 \text{ mA}$$

$$\text{gain (Av)} = \text{gm } R_D = 5$$

$$V_{G_1} = V_{out} = 1.8 - IR_D$$

$$V_{S_1} = I R_S$$

$$\text{Let } R_S = \frac{10}{\text{gm.}}$$

$$\therefore V_{S_1} = \frac{10 I}{\text{gm.}}$$

$$\therefore V_{BS_1} = 1.8 - IR_D - \frac{10 I}{\text{gm.}}$$

$$\therefore I_{DS} = \frac{1}{2} \text{ gm } (V_{GS} - V_{TH})$$

$$2.78 \times 10^{-3} = \frac{\text{gm}}{2} (1.8 - 2.78 \times 10^{-3} R_D - \frac{2.78 \times 10^{-2}}{\text{gm}})$$

$$= 0.9 \text{ gm} - 1.39 \times 10^{-3} \text{ gm } R_D - 1.39 \times 10^{-2}$$

$$\therefore \text{gm } R_D = \text{Av} = 5,$$

$$2.78 \times 10^{-3} = 0.9 \text{ gm} - 6.95 \times 10^{-3} - 1.39 \times 10^{-2}$$

$$\therefore \text{gm} \approx 26.3 \text{ ms}$$

$$\text{and } R_D = \frac{5}{26.3 \times 10^{-3}} \approx 190 \Omega //$$

$$R_S = \frac{10}{26.3 \times 10^{-3}} = 380 \Omega //$$

$$\therefore \text{gm} = \sqrt{2 \mu n C_{ox} \left(\frac{w}{l} \right) I_{DS}} \Rightarrow \left(\frac{w}{l} \right) \approx 622 //$$

$$(70) \quad \therefore R_s \approx \frac{10}{f_m}$$

$$\therefore R_{in} \approx \frac{1}{f_m} = 50 \Omega$$

$$\text{i.e. } f_m = 20 \text{ mS. //}$$

$$[\text{gain (Av)}] = \frac{f_m R_D}{1 + f_m R_s} = 4$$

$$f_m R_D = 4 + 4 f_m R_s$$

$$R_D = \frac{4 + 0.08 R_s}{0.02} = 200 + 4 R_s \quad (1)$$

$$\therefore R_s I_D + V_{GS} - V_{TH} + 0.25 = 1.8 - I_D R_D \quad (\text{given})$$

$$\text{and } I_D = \frac{1}{2} f_m (V_{GS} - V_{TH})$$

$$\text{i.e. } V_{GS} - V_{TH} = 100 I_D$$

$$\therefore R_s I_D + 100 I_D + 0.25 = 1.8 - I_D R_D$$

From (1):

$$R_s I_D + 100 I_D + 0.25 = 1.8 - 200 I_D - 4 I_D R_s$$

$$5 R_s I_D + 300 I_D = 1.55$$

$$\text{Set } R_s = \frac{10}{f_m} = 500 \Omega$$

$$\therefore 2500 I_D + 300 I_D = 1.55$$

$$\therefore I_D = 0.554 \text{ mA //}$$

$$\therefore I_D = \frac{1}{2} f_m (V_{GS} - V_{TH})$$

$$0.554 \times 10^{-3} = \frac{1}{2} \times 20 \times 10^{-3} (V_{GS} - 0.4)$$

$$\therefore V_{GS} = 0.455 V$$

To find $(\frac{w}{l})$:

$$f_m = \sqrt{2 (\frac{w}{l}) M_{max} I_{DS}}$$

$$\therefore (\frac{w}{l}) \approx 18.05$$

To find R_D :

$$\therefore R_D = 200 + 4R_S \quad (\text{from (1)})$$

$$R_D = 2200$$

To find R_1 and R_2 ,

$$\therefore R_1 + R_2 = 20 \text{ k}\Omega$$

$$\text{and } V_{GS} = V_G - I_D R_S = 0.455 \text{ V}$$

$$\text{i.e. } V_G = 0.732 \text{ V}$$

$$V_G = \frac{R_1}{R_1 + R_2} \times V_{DD}$$

$$\therefore R_1 = 8133 \Omega$$

$$R_2 = 11.9 \text{ k}\Omega.$$

$$\therefore R_1 = 8133 \Omega, R_2 = 11.9 \text{ k}\Omega, R_D = 2200 \Omega, R_S = 500 \Omega$$

$$(\frac{w}{l}) = 18.05 \quad I_{DS} = 0.554 \text{ mA.}$$

$$(71) \quad R_{in} = R_g = 10 k\Omega //$$

$$\text{Power} = 2 \text{mW}$$

$$\therefore I_{DS} = \frac{2 \text{mW}}{1.8V} = 1.11 \text{mA} //$$

$$Av = \frac{R_s}{\frac{f_m}{I_{DS}} + R_s} = 0.8$$

$$\therefore R_s = \frac{4}{f_m} \quad \text{--- (1)}$$

$$\because V_{out} = \frac{V_{DD}}{2} = I_{DS} R_s$$

$$I_{DS} R_s = 0.9 \quad \text{--- (2)}$$

$$\therefore V_G = 1.8V \text{ and } V_S = 0.9$$

$$\therefore V_{GS} = 0.8V$$

$$\text{From (2), } \because I_{DS} = 1.11 \text{mA}$$

$$R_s = \frac{0.9V}{1.11 \text{mA}} \approx 810 \Omega //$$

$$\text{From (1), } f_m = \frac{4}{810 \Omega} \approx 4.94 \text{ ms.}$$

$$\therefore f_m = \left(\frac{w}{l}\right) (n_c C_{ox}) (V_{GS} - V_{Tn})$$

$$\frac{w}{l} \approx 49.4 //$$

(72)

$$R_{in} = R_g = Z_0 k \tau$$

$$\therefore \text{Power} = 3 \text{mW}$$

$$\therefore I_{ds} = \frac{3 \text{mW}}{1.8 \text{V}} = 1.67 \text{mA}$$

$$V_{x, \text{at DC}} = I_{ds} R_s = 0.9 \text{V}$$

$$\therefore R_s = 540 \Omega$$

$$\text{Load impedance, } Z_L = R_L // \left(\frac{1}{jC_1} + R_L \right)$$

(at 100 MHz)

$$= 540 // \left(\frac{1}{2\pi \times 10^{-8} C_1} + 50 \right)$$

$$\text{Voltage gain (Av)} = \frac{Z_L}{f_m + Z_L}$$

$$f_m = \frac{2 I_{ds}}{V_{GS} - V_{TH}}$$


$$= \frac{2 \times 1.67 \times 10^{-3}}{(1.8 - 0.9) - 0.4}$$

$$= 6.67 \text{ ms.}$$

$$\therefore Av = \frac{Z_L}{f_m + Z_L} = 0.8$$

$$Z_L = 120 + Z_L (0.8)$$

$$\therefore Z_L = 150$$

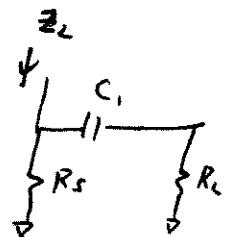

$$\begin{aligned}
 \therefore 150 &= 540 // \left(\frac{1}{2\pi \times 10^8 C_1} + 50 \right) \\
 &= 540 // \left[\frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1} \right] \\
 &= \frac{540 \times \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1}}{540 + \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1}} \\
 \therefore \frac{1 + 50(2\pi \times 10^8 C_1)}{2\pi \times 10^8 C_1} &\approx 208
 \end{aligned}$$

$$\therefore C_1 \approx 10.1 \text{ pF}$$

To find $(\frac{\omega}{L})$:

$$\therefore f_m = \left(\frac{\omega}{L}\right) M_n C_{ox} (V_{GS} - V_{TH})$$

$$\frac{\omega}{L} = 66.7$$

$$\therefore \frac{\omega}{L} = 66.7, C_1 = 10.1 \text{ pF}, R_s = 540 \Omega.$$

7.73

$$\begin{aligned}
P &= V_{DD} I_{D1} = 3 \text{ mW} \\
I_{D1} &= I_{D2} = 1.67 \text{ mA} \\
A_v &= \frac{r_{o1} \parallel r_{o2}}{\frac{1}{g_{m1}} + r_{o1} \parallel r_{o2}} \\
&= \frac{r_{o1} \parallel r_{o2}}{\frac{1}{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}} + r_{o1} \parallel r_{o2}} \\
&= 0.9 \\
r_{o1} &= r_{o2} = \frac{1}{\lambda I_{D1}} = 6 \text{ k}\Omega \\
\left(\frac{W}{L}\right)_1 &= \boxed{13.5}
\end{aligned}$$

Let $V_{ov2} = V_{GS2} - V_{TH} = 0.3 \text{ V}$. Let's assume that $V_{OUT} = V_{DS2} = V_{ov2}$.

$$\begin{aligned}
V_{GS2} &= V_b = V_{ov2} + V_{TH} = \boxed{0.7 \text{ V}} \\
\left(\frac{W}{L}\right)_2 &= \frac{2I_{D2}}{\mu_n C_{ox} (V_{GS2} - V_{TH})^2 (1 + \lambda V_{DS2})} \\
&= \boxed{161} \\
V_{GS1} &= V_{TH} + \sqrt{\frac{2I_{D1}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_1 (1 + \lambda V_{DS1})}} \\
V_{DS1} &= V_{DD} - V_{DS2} = 1.5 \text{ V} \\
V_{GS1} &= 1.44 \text{ V} \\
V_{IN} &= V_{GS1} + V_{DS2} = \boxed{1.74 \text{ V}}
\end{aligned}$$