

Answer key: ECE-2005

1		2	C	3	4	4	B	5	A	6	C	7	C
8	B	9	B	10	C	11	C	12	B	13	C	14	D
15	B	16	D	17	B	18	B	19		20	B	21	D
22	D	23	A	24	C	25	B	26	D	27	D	28	C
29	B	30	C	31	A	32	C	33	A	34	A	35	C
36	C	37	C	38	A	39	B	40	C	41	C	42	D
43	B	44	B	45	B	46	C	47	D	48	A	49	D
50	A	51	B	52	C	53	C	54	A	55	C	56	C
57	B	58	D	59	A	60	C	61	B	62	B	63	B
64	C	65	B	66		67	A	68	C	69	A	70	A
71	C	72	C	73	D	74	C	75	D	76	D	77	C
78	B	79	A	80	B	81		82	D,D	83	B,A	84	C,A
85	A,C												

Explanations:

1. (A) Direct question

2. ()

3. (D) $\frac{1}{2} \times \frac{1}{2}$ 4. (B) $D^2 - 5D + 6 = 0; (D - 2)(D - 3) = 0; D = 2, 3; y = e^{2x} + e^{3x}$ 5. (A) $u_e(t) = \frac{1}{2}; u_0(t) = \frac{1}{2} \text{sgn}(t) = \frac{1}{2} x(t)$
 $\therefore x(t) = \text{sgn}(t)$ 6. (C) First term is right handed sequence and second term is L.H. sequence.
Hence intersection of both ROCs7. (C) Characteristic equation is $s^2 + \frac{Rs}{L} + \frac{1}{LC} = 0$

for no oscillations,

$$b^2 - 4ac \geq 0$$

$$\frac{R^2}{L^2} \geq \frac{4}{LC} \Rightarrow R \geq 2\sqrt{\frac{L}{C}}$$



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} n & 0 \\ 0 & X \end{bmatrix}; V_1 = nV_2; I_1 = -XI_2$$

8. (B) $\frac{V_1}{V_2} = n = \frac{I_2}{I_1}$

$$\therefore X = \frac{1}{n} \quad [\text{neglecting -ve sign}]$$

9. (B) $w = \frac{1}{\sqrt{LC}} = \frac{\sqrt{400}}{\sqrt{10^{-6}}} = 20 \times 10^3; f = \frac{\omega}{2\pi} = \frac{10^4}{\pi}$

10. (C) Using MPT, $R_L = 100\Omega; P_{RL} = \frac{V^2}{4R_L} = \frac{100}{4 \times 100} = 0.25\omega$

11. (C)

12. (B) I_{CO} doubles for 10°C rise in temperature

13. (C)

14. (D)

15. (A) $10\text{K} \square 30\text{K}$

16. ()

17. (B)

18. (B)

19. (A) Let O/P of 1st mux be E,

$$\therefore \begin{bmatrix} B & \bar{E} \\ 0 & C \\ 1 & \bar{C} \end{bmatrix}$$

$$\therefore E = B\bar{C} + \bar{B}C$$

$$\text{Now } f = EA = A(B\bar{C} + \bar{B}C)$$

20. (B)

21. (D) $y(e^{j0}) = \sum_{n=0}^{\infty} y(n) = \sum_{n=0}^{\infty} \left(\frac{1}{2}\right)^{2n} = \sum_{n=0}^{\infty} \left(\frac{1}{4}\right)^n = \frac{1}{1 - \frac{1}{4}} = \frac{4}{3}$

22. (D)

23. (A) $\left(\frac{8}{\sqrt{2}}\right)^2 + \left(\frac{4}{\sqrt{2}}\right)^2 = \frac{8^2 + 4^2}{2} = \frac{64 + 16}{2} = 40$

24. (C)

25. (B) Eigen values of a linear system are same through representation of a system by state equation may be different

26. (D) Check with $\frac{1}{s + ST}$ @ $\omega=0$ and $\omega=\infty$

27. ()

28. (C)

$$\bar{H} = H_0 \sin(\omega t p \beta x + \phi) a_y$$

$$\omega = 5 \times 10^4, \beta = 0.004$$

$$V_p = \frac{\omega}{\beta} = \frac{5 \times 10^4}{0.004} = 1.25 \times 10^7 \text{ m/s.}$$

since \bar{H} is in +ve y , \bar{E} in z , propagation in -ve x dim

else \bar{H} would have been $H_0 \sin(\omega t - \beta x)$ for +ve x dim propagation

$$\therefore V_p = -1.25 \times 10^7 \text{ m/s.}$$

29. (B)

30. (C)

$$V_p \text{ in glass} = \frac{3 \times 10^8}{\eta} = \frac{3 \times 10^8}{1.5} = 2 \times 10^8 = f \lambda$$

$$\therefore \lambda = 2 \mu\text{m}$$

31. ()

32. (C) Eigen values are 4, -5.

To find eigen vector $(\lambda I - A)(x) = 0$

$$\begin{bmatrix} \lambda + 4 & -2 \\ -4 & \lambda - 3 \end{bmatrix} \begin{pmatrix} x_1 \\ x_2 \end{pmatrix} = 0$$

$$\text{for } \lambda = 4, 8x_1 = 2x_2, 4x_1 = x_2 \quad \begin{bmatrix} 1 \\ 4 \end{bmatrix} \text{ not in choice.}$$

$$\text{for } \lambda = -5, -x_1 = 2x_2 \begin{bmatrix} -1 \\ 1 \end{bmatrix} \text{ or } \begin{bmatrix} 2 \\ -1 \end{bmatrix} \rightarrow [C]$$

$$AA^{-1} = I$$

$$33. \quad (A) \quad A^{-1} = \frac{1}{6} \begin{bmatrix} 3 & 0.1 \\ 0 & 2 \end{bmatrix} = \begin{bmatrix} \frac{1}{2} & \frac{1}{60} \\ 0 & \frac{1}{3} \end{bmatrix}$$

$$a + b = \frac{1}{60} + \frac{20}{60} = \frac{21}{60} = \frac{7}{20}$$

34. (A) The integral is of Gaussian type with mean 0 and variance 4

$$\frac{1}{\sigma\sqrt{2\pi}} \int_{-\infty}^{\infty} e^{-\frac{(x-\mu)^2}{2\sigma^2}} dx = 1$$

Now if $\mu = 0$,

$$I = \frac{\text{area under } x(t)}{x} = 1$$

$$\text{Area} = \frac{2}{2\sqrt{2\pi}} \int_0^{\infty} e^{-\frac{x^2}{8}} dx = 1$$

$\therefore \text{Area} = I = 1$

35. (C) $\frac{d}{dx} e^{-x^2} = -2xe^{-x^2} \rightarrow \text{odd function}$

36. (C)

37. (A) $AA^T = \begin{bmatrix} 4 & 0 & 0 & 0 \\ 0 & 4 & 0 & 0 \\ 0 & 0 & 2 & 0 \\ 0 & 0 & 0 & 2 \end{bmatrix} = B; B^{-1} = \begin{bmatrix} \frac{1}{4} & 0 & 0 & 0 \\ 0 & \frac{1}{4} & 0 & 0 \\ 0 & 0 & \frac{1}{2} & 0 \\ 0 & 0 & 0 & \frac{1}{2} \end{bmatrix}$

38. (A) $10\angle 60^\circ - 5\angle 0^\circ = \frac{10\sqrt{3}}{2} \angle 90^\circ$

39. (B) $j(5+2+2+2 \times 10 - 2 \times 10) = j9$

40. ()

41. (C) $V_a = 5V; V_b = \frac{10 \times 1.1}{2.1} = 5.238$
 $V_{ab} = -0.238$

42. (D)

$$V_1 = h_{11}i_1 + h_{12}V_2$$

$$I_2 = h_{21}i_1 + h_{22}V_2$$

$$\text{for } V_2 = 0, h_{11} = 10\Omega$$

$$h_{21} = -1$$

$$\therefore i_2 = -i_1$$

43. (B) Differentiation ckt

44. (B) $\frac{\sigma_A}{\sigma_B} = \frac{n_A e \mu_b}{n_B e \mu_c} = \frac{\mu_b}{\mu_c} = \frac{1}{3}$

45. (B) $\frac{C_D}{A} = \frac{\epsilon}{w} = \frac{11.7 \times 8.85 \times 10^{-12}}{10 \times 10^{-6}} = 10\mu F$

46. (C) $I_E = I_0 \left(e^{\frac{V}{V_T}} - 1 \right)$

$$V = 0.7, V_T = 26 \text{ mV}, I_0 = 10^{-13} \text{ A}$$

$$I_E = 49 \text{ mA}$$

47. ()

48. (A)

49. (D)

50. (C) $V_{GS} = 2V, V_T = 1V$
 $V_{DS} = 4V; V_{DS} > V_{GS} - V_T$
51. (B) $20 - 0.7 = \frac{430 \times I_E}{51} + I_E$ (I_E is mA)
 $I_E = 2.04 \text{ mA}$
 $I_B = \frac{I_E}{1 + \beta} = 40 \mu A$
 $V_C = 20 - 2k \times \alpha \times I_E = 15.9 \approx 16V$
52. (A) $\frac{30 - 5.8}{1000} - 0.5m = 23.7mA$
53. (C) Q_3 is saturation.
 $\therefore I_B = \frac{0.75}{1} = 0.75mA$
54. (A) $(C + A)(\bar{A} + \bar{C})B$
55. (C) $9\mu \left(1 - \frac{V_0}{1}\right)^2 = 36\mu \left(1 - \frac{(5 - V_0)}{1}\right)^2$
 $1 - V_0 = 2(1 - 5 + V_0)$
 $1 - V_0 = -8 + 2V_0$
 $9 = 3V_0$
 $V_0 = 3$
56. (C) $J = 1 \quad K = X \quad Q_n$
i.e, $J = 1 \quad = 0 \quad = 1$
 $J = 1 \quad = 1 \quad \bar{Q}_n = 1$
57. (A) +ve edge triggered
 $Q_2 Q_1 Q_0$
0 1 1 $\therefore Q_1$ and Q_2 are getting 0 as clk pulse
0 1 0
58. (D) $A_9 \quad A_8 \quad (A_7 \dots A_0)$
(0 1 (X X) \rightarrow Chip 1
(1 0 X X) Chip 2
Choice (D) doesn't satisfy.
59. (A)
 $y(\omega) - x(\omega) \left[\frac{1}{2} e^{-j\omega(t_d - T)} + \frac{1}{2} e^{-j\omega(t_d + T)} + e^{-j\omega t_d} \right]$
 $= e^{-j\omega t_d} [1 + \cos \omega T]$
60. (C)

61. (B) $\frac{Y(\omega)}{X(\omega)} = Ae^{-jn_o\omega_o} = H(\omega) = |H(\omega)| \angle H(\omega)$
 $\therefore \angle H(\omega) = -n_o\omega_o + 2\pi k$

periodic with 2π .

62. (B) $x(at) \leftrightarrow \frac{1}{|a|} \times \left(\frac{f}{a}\right)$
 $a = \frac{1}{3}$

\therefore only choice satisfying is B.

63. (B) Number of net encirclement should be zero.

64. (C)

65. ()

66. (A) Type 1 system has an error for ramp i/p

$$K_v = \lim_{s \rightarrow 0} G(s)H(s) = \text{zero frequency gain}$$

$$= \frac{1}{0.05} = 20$$

67. ()

68. (C) The breakaway and break-in points are -1, 3

69. (C) Accumulation mode in n MOS

70. (C) Both f_m and Δf get multiplied by 2

$$BW = 2(10 + 180) = 380$$

71. (C)

$$h(t) = x(T-t)$$

$$y(t) = R_{xx}(t-T)$$

72. (A)

73. ()

74. (C)

$$\int_0^4 p(V) = 1 \Rightarrow k = \frac{1}{2} \quad \frac{k}{4} \frac{4^2}{2} = 1 \quad k = \frac{1}{2}$$

$$\int_0^4 \frac{k}{4} v dv = 1$$

$$\text{Mean square} = \int_0^4 v^2 p(v) = \frac{k}{4} \int_0^4 V^3 dv = \frac{k}{4} \frac{V^4}{4} = \frac{1}{2 \times 4 \times 4} 4^4 = \frac{4^2}{2} = 8$$

75. (D) $\lambda = \frac{2b}{2} = b$

76. (D) $z_0^2 = z_{sc} \times z_{oc} \Rightarrow z_{sc} = 7.69 - j11.54\Omega$

77. (B) $z_i = 2M$
 $z_o = 20k \square 2k = \frac{20}{11}k$
78. ()
79. (A) $I_D = 10 \left(1 - \frac{2}{8}\right)^2 = 5.625$
80. (B) $g_m = g_{mo} \left(1 - \frac{V_{DS}}{V_p}\right) = \frac{2 \times 10}{8} \left(1 - \frac{1}{4}\right) = 1.875mS$
 $\mu = -g_m (r_d \square R_D) = -3.41$
81. (A) (C) 0100 Lx1 SP, 00FF
 0103 Lx1 H, 0701 H 01
 0106 MVI A, 20 L 07
 0108 SUB M
 A = A - ((H) (L))
 = 20 - 20 = 0
- (B) (C) 00 or 40 = 40 + 20 = 60
82. (A) ()
 (B) ()
83. (A) (B) Area of region 1 = $\frac{1}{3}$
- $$\frac{2a}{4} = \frac{1}{3} \Rightarrow a = \frac{2}{3}$$
- (B) ()
84. (A) (B) $\frac{V_{\max}}{V_{\min}} = \frac{4}{1} = \frac{1+|r|}{1-|r|} = \frac{1+|5|}{1-|5|}$
- (B) (C)
- $$|r| = \frac{3}{5} = 0.6$$
- $$r = \frac{Z_R - Z_O}{Z_R + Z_O} = 0.6$$
- $$Z_R = 200$$
85. (A) (A) shift then scale
 (B) (C)